



Brac University

Faculty : AQT

CSE250 Circuits and Electronics

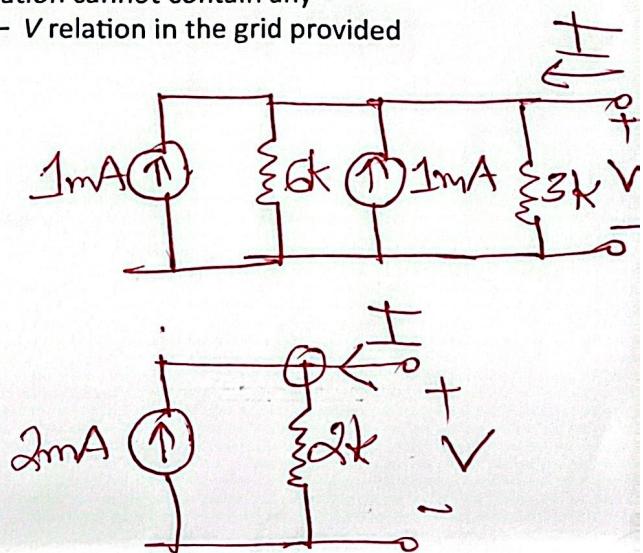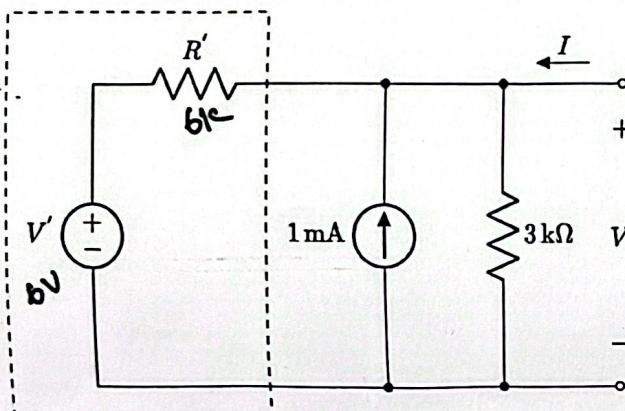
Question 1 of 2 [10 marks]

Derive a Current-Voltage Relationship from *Circuit 2*. The $I - V$ equation cannot contain any variables other than I and V pointed out in the diagram. Plot the $I - V$ relation in the grid provided above.



$$\begin{aligned} \text{KCL: } & 2 + I = \frac{V}{2} \\ \Rightarrow & I = \frac{V}{2} - 2 \end{aligned}$$

(6)

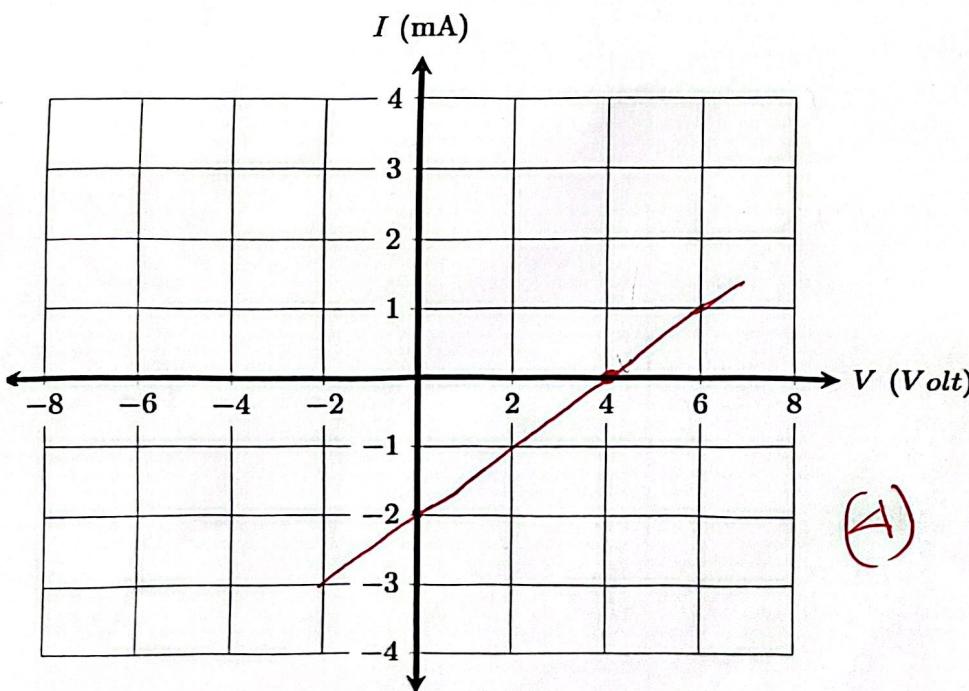

Question 2 of 4

[10 marks]

When a voltage $V = 5V$ is applied between terminals a and b of a linear two terminal circuit 'X', the circuit draws a current $I = 2A$ as shown in Figure 1 below. When the terminals are shorted, 3A current flows as shown in Figure 2.

(a) [2 marks] Derive a relationship between I and V.

(b) [2 marks] Draw the relationship found in (a) on the grid provided below.

(c) [6 marks] If the circuit in Figure 1 is an alternative version of the circuit 'X', determine the voltage V' and the resistance R' .

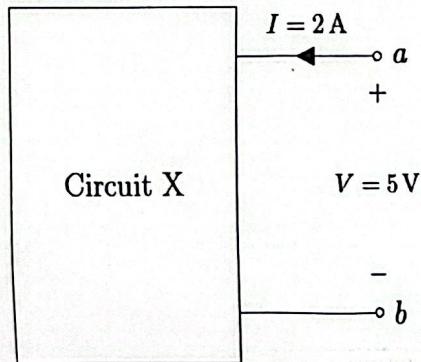


Figure 1

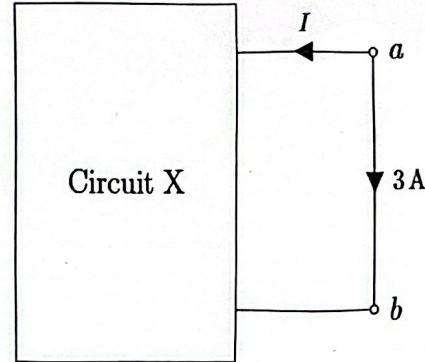


Figure 2

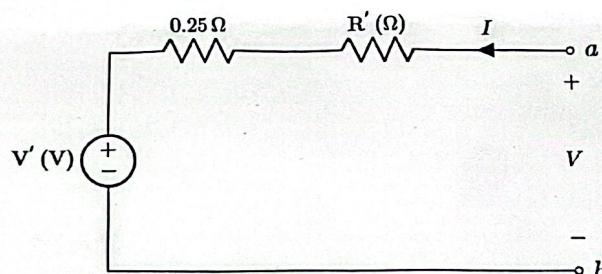


Figure 3

$$R = \frac{V}{I}$$

Equivalent R ,

$$0.25 + R' = 1$$

$$\therefore R' = 0.75$$

$$V' = 3$$

$$(V, I)$$

$$(5, 2), (0, -3)$$

$$y - y_1 = \frac{x - x_1}{x_2 - x_1}$$

$$y_2 - y_1 = \frac{x - 5}{0 - 5}$$

$$\Rightarrow y - 2 = \frac{x - 5}{0 - 5}$$


$$\Rightarrow y - 2 = x - 5$$

$$\Rightarrow y = x - 3$$

$$\therefore I = V - 3$$

$$m = 1$$


$$R = 1\Omega$$

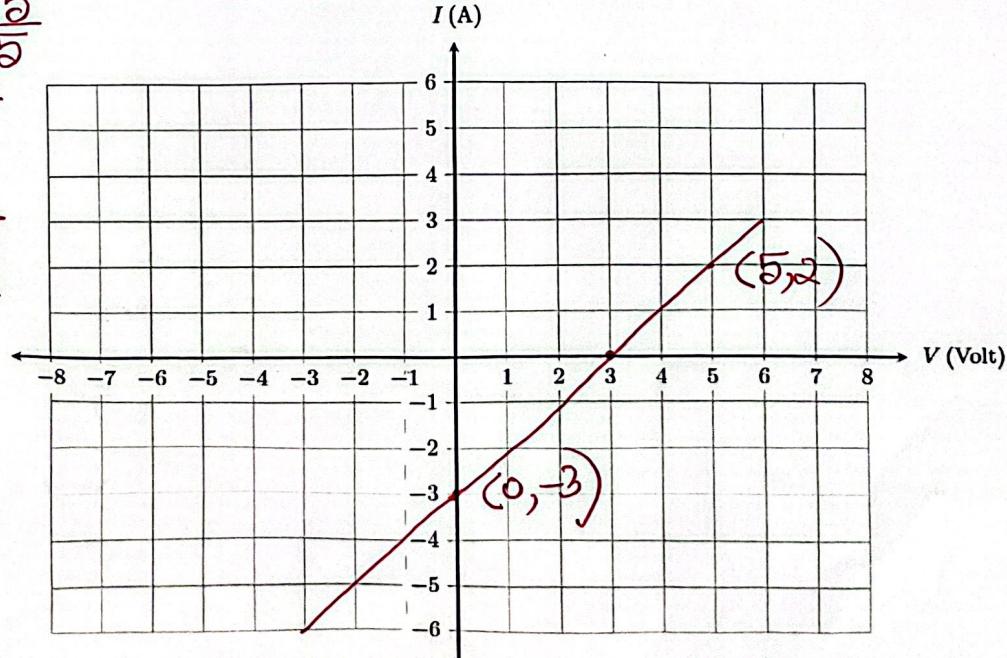

(a) Obtain the Thevenin Equivalent circuit at terminals a-b. (12 marks)

(b) Determine the value of R_L that will draw Maximum Power from the rest of the circuit. (3 marks)

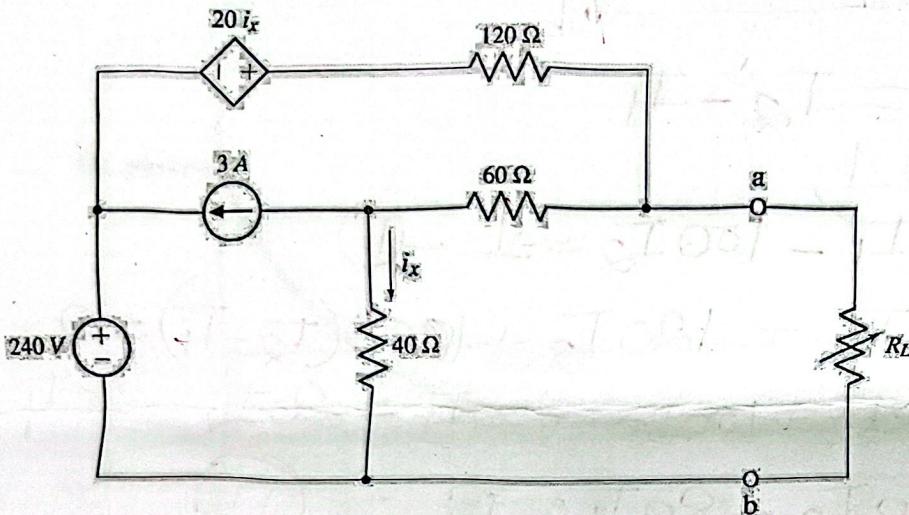(c) Determine that value of the Maximum Power. (5 marks)




$$R_L = 60\Omega$$

$$V_{Th} = 30V$$

$$P_{max} = 3.75W$$

(a)

$$\frac{V_{Th}}{(4)}$$

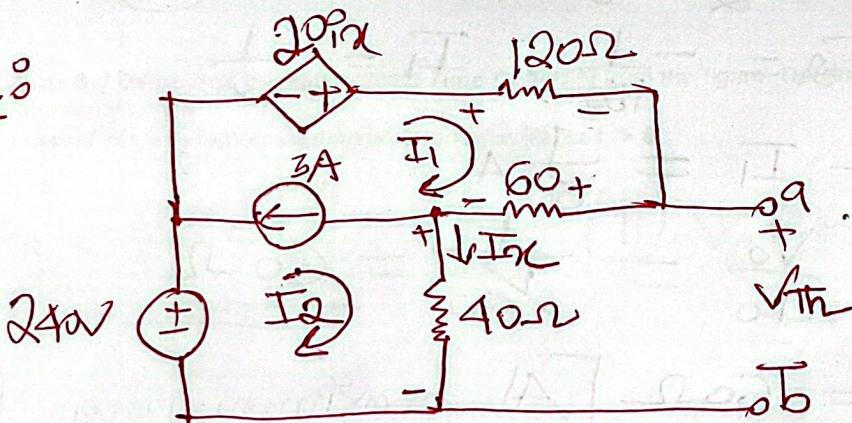

$$\cancel{V_{40}} = I_2 \times 40$$

Supermesh relations,

$$I_1 - I_2 = 3 \quad \textcircled{1}$$

$$I_2 = I_x$$

xVL at open loop,
+ V_{Th} + V_{40} + V_{60} = 0

$$V_{Th} = I_x \times 40 + I_x$$

$$= I_2 \times 40$$

$$= \cancel{\frac{3}{2}} \times 40$$

$$+ \cancel{\frac{1}{2} \times 60 \times 3}$$

$$= \underline{\underline{30V}}$$

xVL at outer loop,

$$-240 - 20I_x + 120I_1 + 60I_1 + 40I_2 = 0$$


$$\Rightarrow -20I_2 + 120I_1 + 60I_1 + 40I_2 = 240$$

$$\Rightarrow 180I_1 + 20I_2 = 240 \quad \textcircled{1}$$


$$I_1 = \cancel{-3.1A}, I_2 = \cancel{-\frac{3}{2}A}$$

R_{Th} (A)

Universal Method

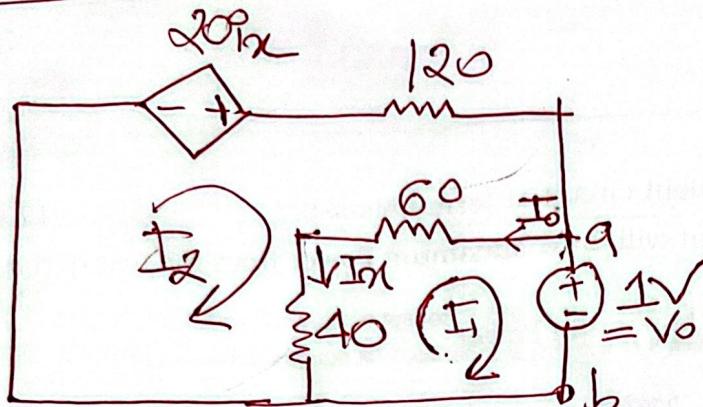

(A) Thévenin Circuit

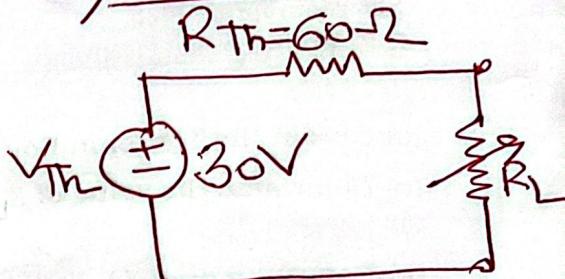

$$I_x = I_2 - I_1$$

KVL @ 1,

$$100I_1 - 100I_2 = -1 \quad \textcircled{I}$$

KVL @ 2

$$20I_x + 120I_2 + 1000(I_2 - I_1) = 0$$

$$\Rightarrow 120I_2 + 100I_2 - 100I_1 = 20I_2 - 20I_1$$

$$\Rightarrow 200I_2 - 80I_1 = 0 \quad \textcircled{II}$$

$$I_2 = -\frac{1}{150} \quad I_1 = -\frac{1}{60}$$

$$I_0 = -I_1 = \frac{1}{60} \text{ A}$$

$$R = \frac{V_o}{I_0} = \frac{1}{\frac{1}{60}} = \underline{\underline{60 \Omega}}$$

$$(b) R_L = 60 \Omega \quad [\text{At maximum power, } R_L = R_{Th}]$$

$$(c) P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(30)^2}{4 \times 60} = \underline{\underline{3.75 \text{ W}}} \quad (5)$$

Solution

ID:	Name:
-----	-------




Brac University
 Semester: Spring 2025
 Course Code: CSE250
 Circuits And Electronics
 Faculty: AQT

■ Question 1

[5 marks]

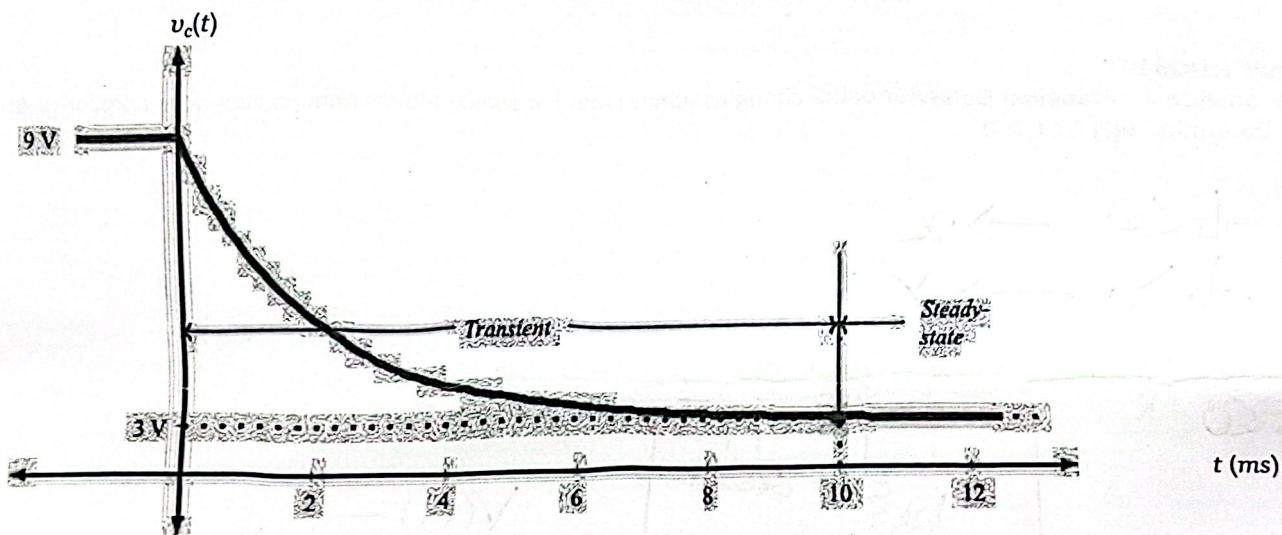The $v_c(t)$ vs t plot below shows the voltage response of a capacitor (C) in a series RC circuit to a sudden change in the DC voltage applied through an equivalent resistance of $2 \text{ k}\Omega$.



- (i) [3 marks] Determine the approximate Time Constant from the figure. Determine C with appropriate units.
 (ii) [2 mark] Write a mathematical expression of $v_c(t)$ for $t > 0$

(i)

$$R_{\text{eq}} = 2 \text{ k}\Omega$$

$$5\tau = 10 \text{ ms}$$

$$\therefore \tau = 2 \text{ ms}$$

$$\tau = RC$$

$$\Rightarrow 2 \times 10^{-3} = 2 \times 10^3 \times C$$


$$\Rightarrow C = \frac{2 \times 10^{-3}}{2 \times 10^3}$$

$$\therefore C = 1 \mu\text{F}$$

$$\begin{aligned}
 \text{(ii)} \quad v_c(t) &= v(\infty) + [v(0) - v(\infty)] e^{-\frac{t}{\tau}} \\
 &= 3 + [9 - 3] e^{-\frac{t}{2}} \\
 &= 3 + 6e^{-\frac{t}{2}}
 \end{aligned}$$

■ Question 2

[8 marks]

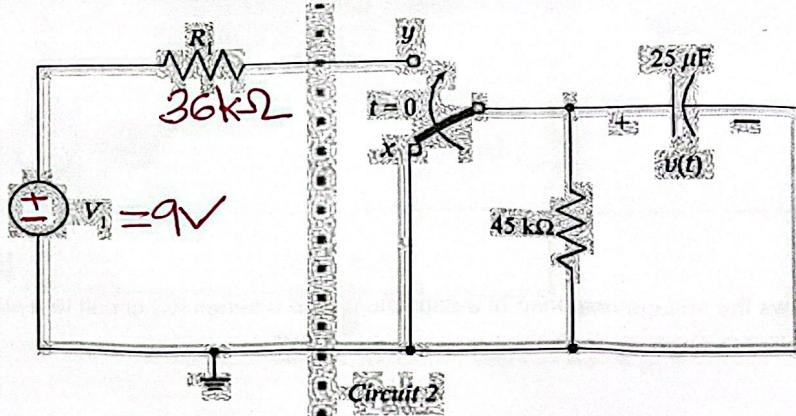


$$V_1 = 9V, R_1 = 36\text{ k}\Omega$$

Now, analyze the Transient Behavior of the circuit assuming that the switch moves from position **x** to position **y** at $t = 0$. Determine $v(t)$ for $t > 0$.

$$\begin{aligned} t < 0 &\rightarrow x \\ t > 0 &\rightarrow y \end{aligned}$$


$$t < 0$$

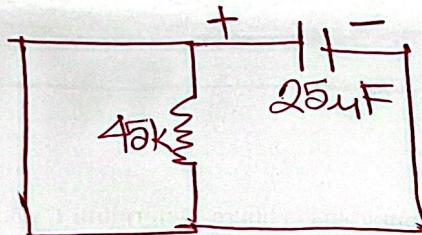

$$v(0) = 0V$$

source free

$$t > 0$$

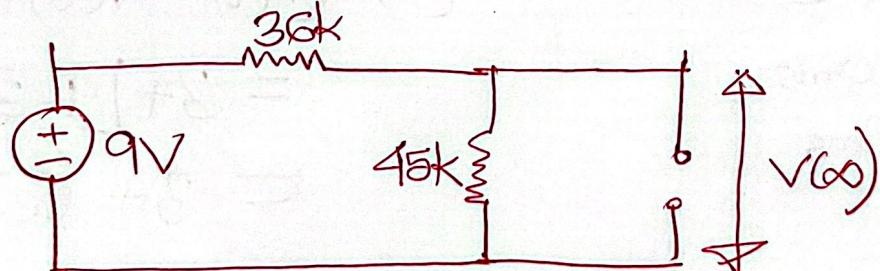

$$v(\infty) = \frac{45}{45+36} \times 9V = 5V$$

$$\gamma, t > 0$$


$$\begin{aligned} \tau &= RC \\ &= 20 \times 10^3 \times 25 \times 10^{-6} \\ &= 0.5s \end{aligned}$$

$$\begin{aligned} R_{eq} &= 36 || 45 \\ &= 20\text{ k}\Omega \end{aligned}$$

$$\begin{aligned}v(t) &= v(\infty) + [v(0) - v(\infty)] e^{-\frac{t}{0.5}} \\&= 5 + [0 - 5] e^{-\frac{t}{0.5}} \\&= 5 - 5e^{-2t} \quad (\checkmark), \quad t > 0\end{aligned}$$


■ Question 3

[7 marks]

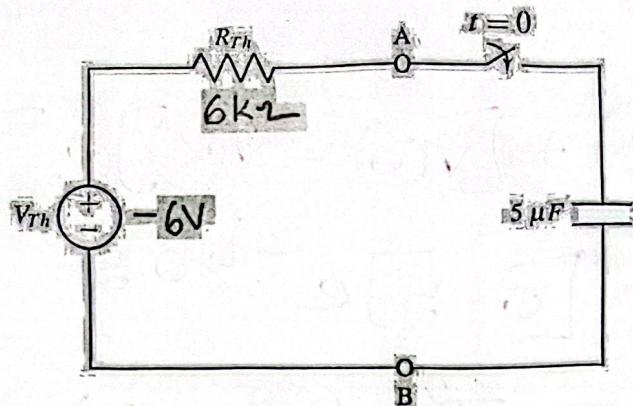


Perform transient analysis to determine $v(0)$, $v(\infty)$, and $v(t)$ for $t > 0$.

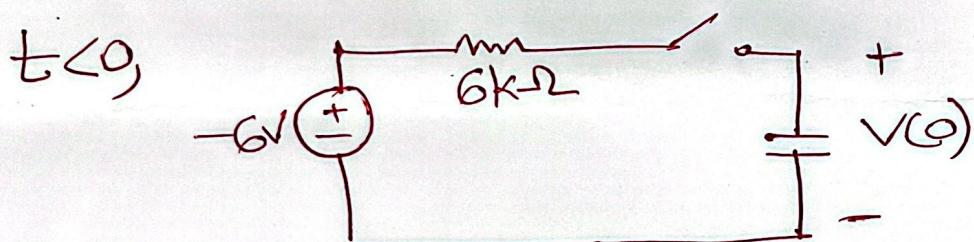$t < 0$ Switch open
 $t > 0$ Switch closed



$$v(0) = 0V$$

Capacitor disconnected

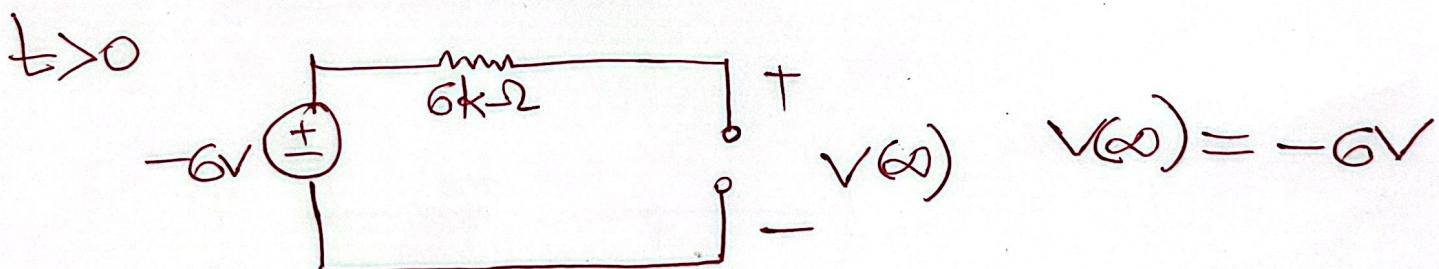

$$v(\infty) = -6V$$

$$\gamma, t > 0$$

$$\gamma = RC$$

$$= 6000 \times 5 \times 10^{-6}$$

$$= 30ms = 0.03s$$

$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-\frac{t}{RC}}$$

$$= -6 + [0 + 6] e^{-\frac{t}{0.03}}$$

$$= -6 + \frac{6}{0.03} e^{-t/0.03}, \quad t > 0 \quad (t \rightarrow ms)$$

Solution

ID:

Name:




Brac University
Semester: Spring 2025
Course Code: CSE250
Circuits and Electronics
Faculty: AQT

Quiz 5

■ Question 1 of 2

[CO3] [16 marks]

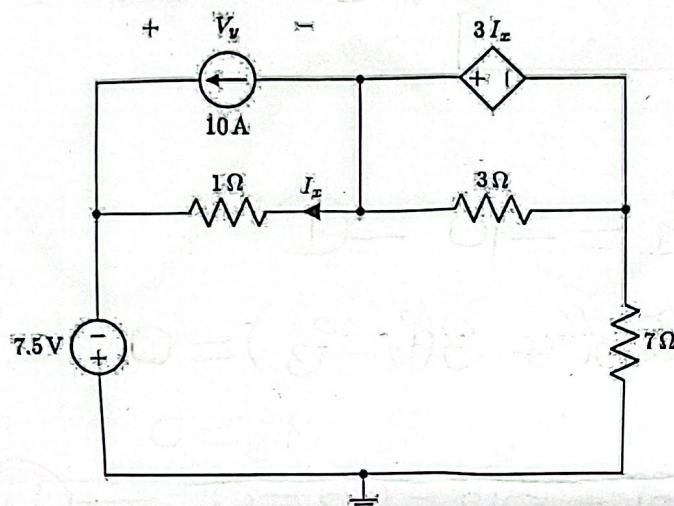

From the above circuit, answer the following questions-


(a) [9 marks] Find V_y using Superposition principle.

After applying Superposition principle you may use any analysis technique you prefer (Nodal, Mesh, Src Tx etc.).

(b) [9 marks] Find the power consumed/supplied by the current source (with proper ± sign and unit).

(a)

Keeping 7.5V active,

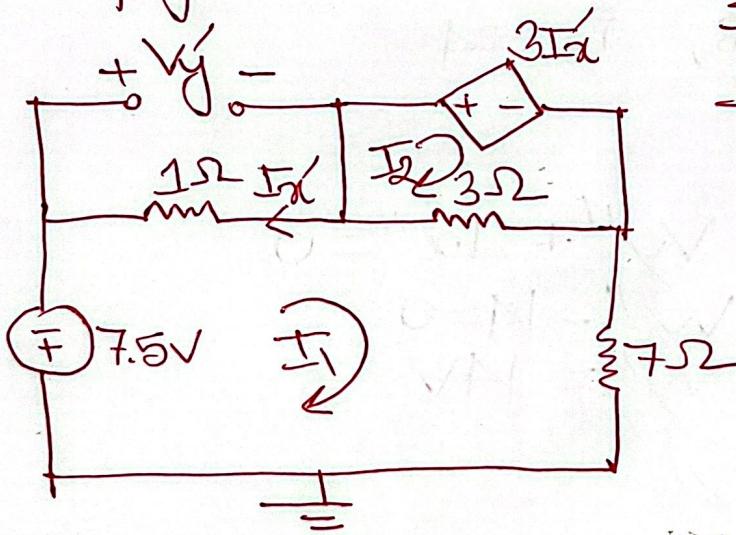


$$I_1 = -I_{x'}$$

$$\begin{aligned} \text{Mesh 1} \quad & 7.5 + I_1 + 3(I_1 - I_2) + 7I_1 = 0 \\ \Rightarrow & 11I_1 - 3I_2 = -7.5 \quad \text{--- (1)} \\ \text{Mesh 2} \quad & 3(I_2 - I_1) + 3I_{x'} = 0 \\ \Rightarrow & 3I_2 - 3I_1 - 3I_{x'} = 0 \\ \Rightarrow & -6I_1 + 3I_2 = 0 \quad \text{--- (11)} \\ I_1 = & -1.5A, I_2 = -3A \end{aligned}$$

$$\begin{aligned} V_y' = & -I_{x'} \times 1 = +I_1 = 1.5V \\ = & -1.5V \end{aligned}$$

keeping 10A active

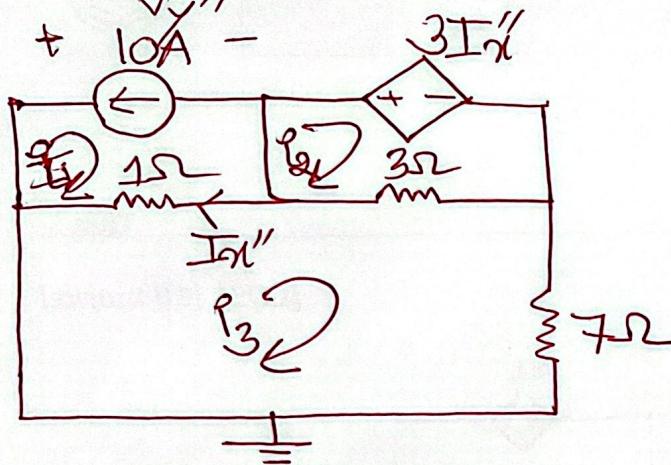

$$(b) \text{Power} = VI$$

$$P_{10A} = V_y \times 10A$$

$$= 12.5 \times 10$$

$$= -125W$$

(Supplying)

$$I_{in}'' = I_1 - I_3$$

$$\text{Mesh 1: } I_1 = -10 \quad \textcircled{1}$$

$$\text{Mesh 2: } 3I_{in}'' + 3(I_2 - I_3) = 0$$

$$\Rightarrow 3I_1 - 3I_3 + 3I_2 - 3I_3 = 0$$

$$\Rightarrow 3I_1 + 3I_2 - 6I_3 = 0 \quad \textcircled{11}$$

$$\text{Mesh 3: } I_3 - I_1 + 3(I_3 - I_2) + 7I_3 = 0$$

$$\Rightarrow -I_1 - I_1 - 3I_2 + 11I_3 = 0 \quad \textcircled{111}$$

$$I_1 = -10, I_2 = 18, I_3 = 4$$

$$I_{in}'' = -14A$$

$$\text{KVL in loop 1: } V_y''' + I_{in}'' = 0$$

$$\Rightarrow V_y''' - 14 = 0$$

$$\therefore V_y''' = 14V$$


$$\begin{aligned} V_y &= V_y' + V_y'' \\ &= -1.5V + 14V \\ &= \underline{\underline{12.5V}} \end{aligned}$$

■ Question 2 of 2

[8 marks]

Two ac voltage waveforms $v_1(t)$ and $v_2(t)$ from a circuit are plotted below as a function of time t .

$v_1(t), v_2(t)$ (Volt)

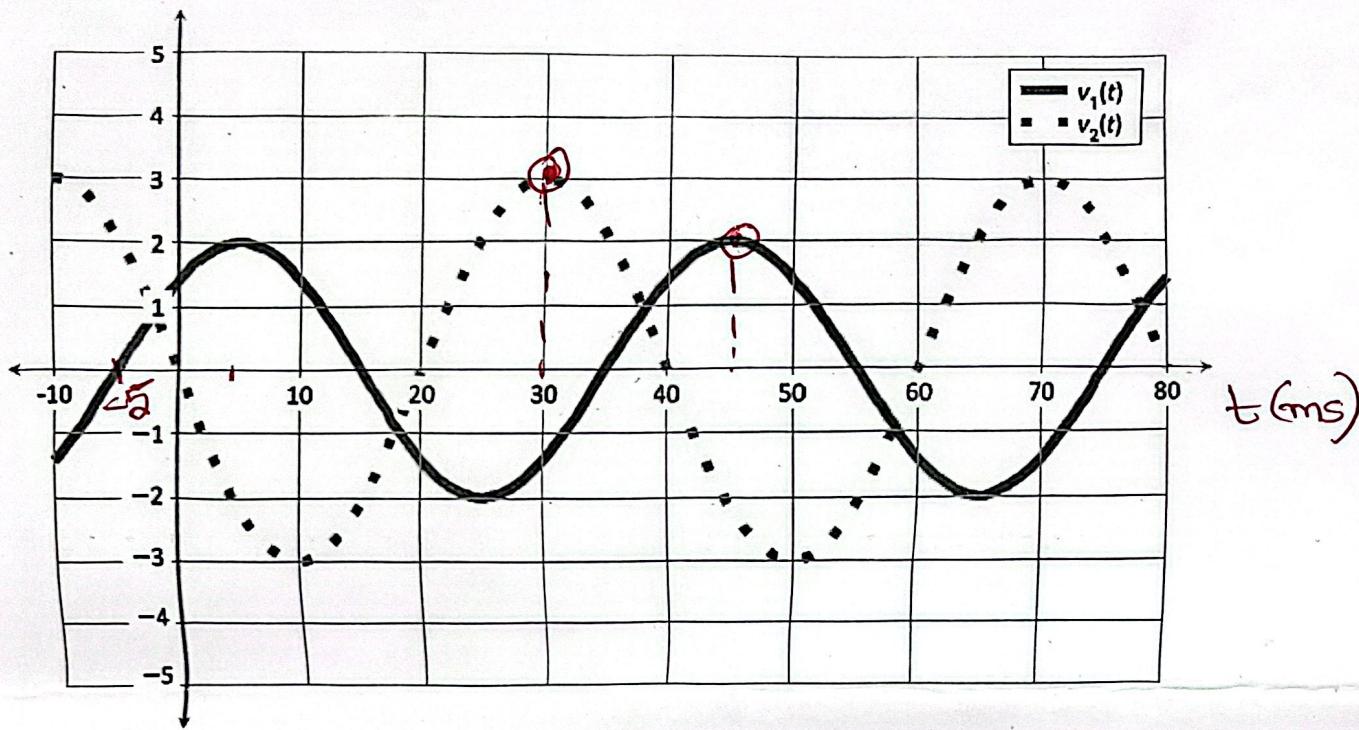

(a) [4 marks] Determine the phase difference between the two and specify which one is leading.

(b) [4 marks] Write analytical expressions for both $v_1(t)$ and $v_2(t)$. From the expressions, verify the fact found in (a).

$$(a) \Delta t = 45 - 30 = 15 \text{ ms}$$

$$T = 40 \text{ ms}$$

$$\Delta\phi = \frac{\Delta t}{T} \times 360^\circ = \frac{15}{40} \times 360^\circ = 135^\circ$$

$$\frac{20}{40} \times 360^\circ = 180^\circ$$

$v_2(t)$ is leading

$$v_2(t) = 3 \sin\left(\frac{2\pi}{40}t - 180^\circ\right)$$

$$(b) v_1(t) = 2 \sin\left(\frac{2\pi}{40}t + 45^\circ\right)$$

$$\phi = \frac{5}{40} \times 360^\circ = 45^\circ$$

$$v_2(t) = -3 \sin\left(\frac{2\pi}{40}t\right) \\ = 3 \sin\left(\frac{2\pi}{40}t - 180^\circ\right)$$