

# Department of Computer Science and Engineering (CSE) BRAC University

Fall 2023

CSE250 - Circuits and Electronics

## SUPERPOSITION PRINCIPLE




*PURBAYAN DAS, LECTURER  
Department of Computer Science and Engineering (CSE)  
BRAC University*

# Linearity property

- **Linearity** is the property of an element describing a linear relationship between cause and effect. The property is a combination of both the **homogeneity** (scaling) property and the **additivity** property.
- **Homogeneity property**  
For a resistor, for example, Ohm's law relates the input  $i$  to the output  $v$  as  $v = iR$ . If the current is increased by a constant  $k$ , then the voltage increases correspondingly by  $k$ ; that is,  $kv = (ki)R$ .
- **Additivity property**  
If applying  $v_1$  &  $v_2$  separately to a resistor gives rise to currents  $i_1$  &  $i_2$  respectively, then applying  $(v_1 + v_2)$  should give rise to the current  $(i_1 + i_2)$ .
- A **linearity circuit** is one whose output is linearly related (or directly proportional) to its input.

# Course Outline: broad themes

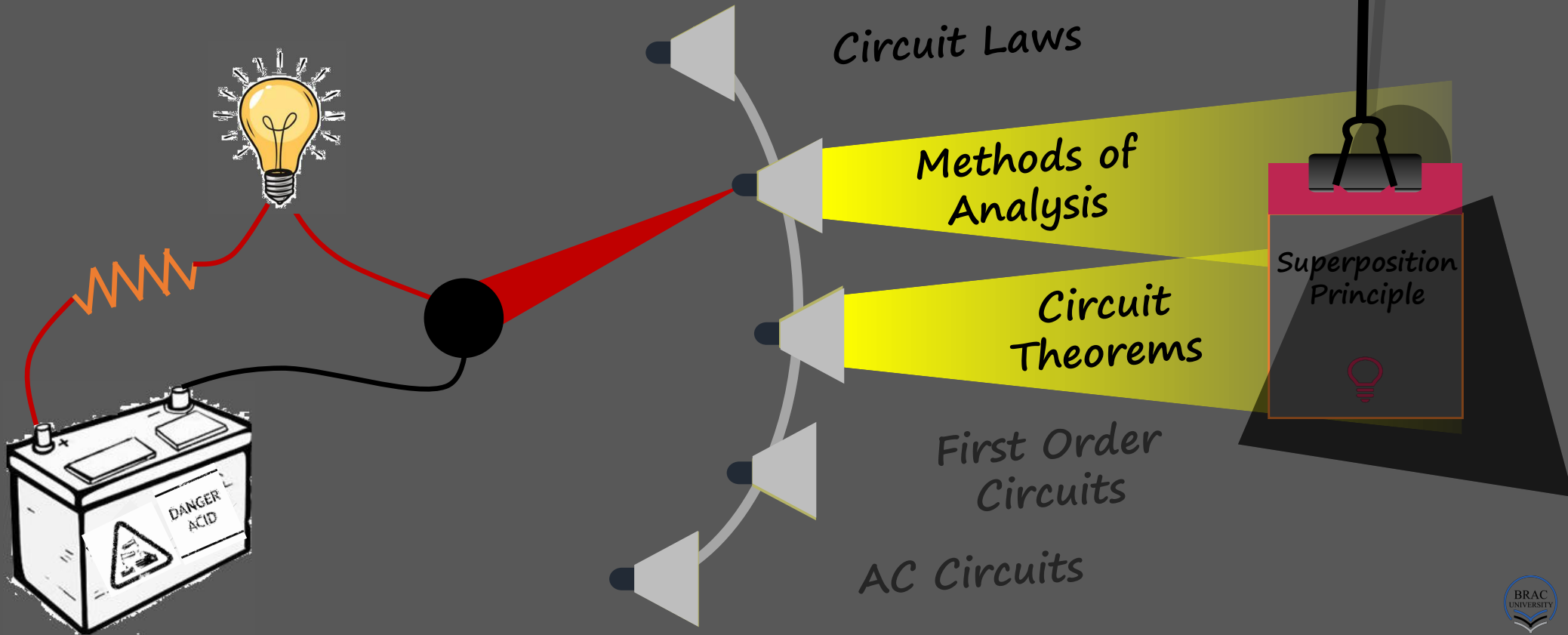

# Superposition Principle

- The *superposition principle* states that the voltage across (or current through) an element in a linear circuit is the algebraic sum of the voltages across (or currents through) that element due to each independent source acting alone.
- Keep in mind that superposition is based on linearity. For this reason, it is not applicable to the effect on power due to each source.

$$P_{Total}^2 \neq P_1^2 + P_2^2 + \dots + P_N^2$$




- If the power value is needed, the current through (or voltage across) the element must be calculated first using superposition.

## Steps to Apply Superposition Principle:

1. Turn off all independent sources except one source. Find the output (voltage or current) due to that active source using the techniques covered in Chapters 2 and 3.
2. Repeat step 1 for each of the other independent sources.
3. Find the total contribution by adding algebraically all the contributions due to the independent sources.

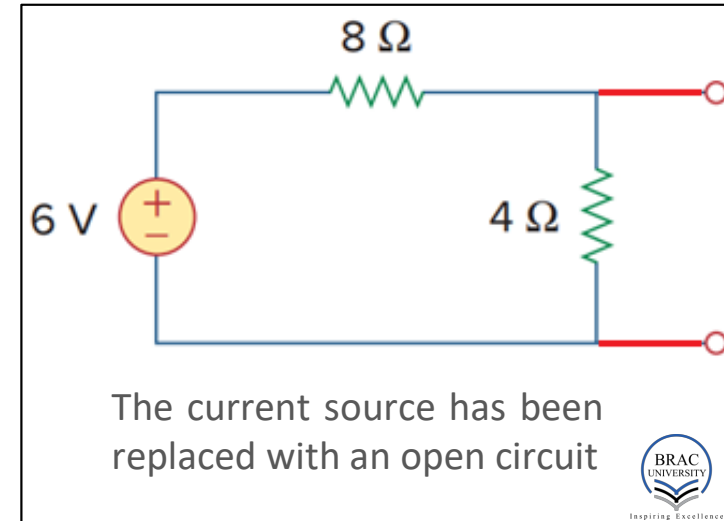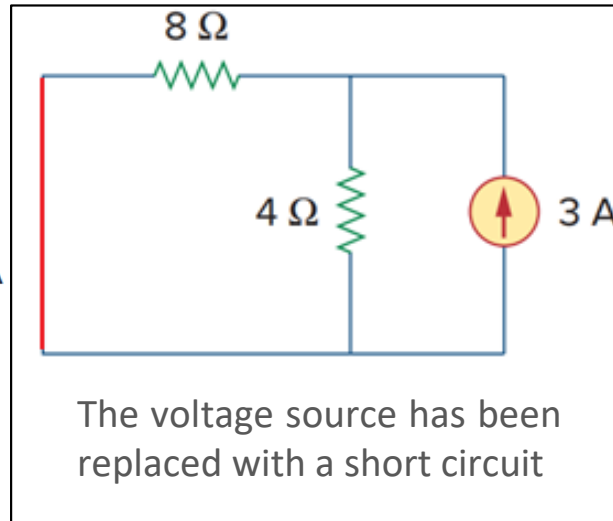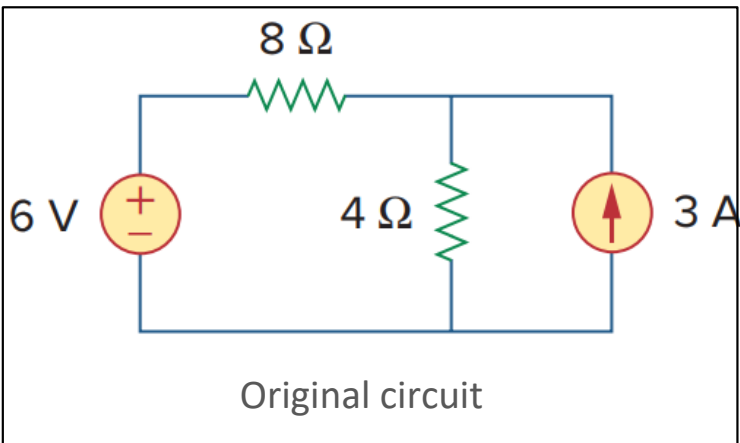
# Equivalence with inactive I/V sources

- In superposition principle, we consider one independent source at a time while all other independent sources are turned off. This implies that we replace every voltage source by  $0\text{ V}$  (or a short circuit), and every current source by  $0\text{ A}$  (or an open circuit).
- Dependent sources are left intact because they are controlled by circuit variables.


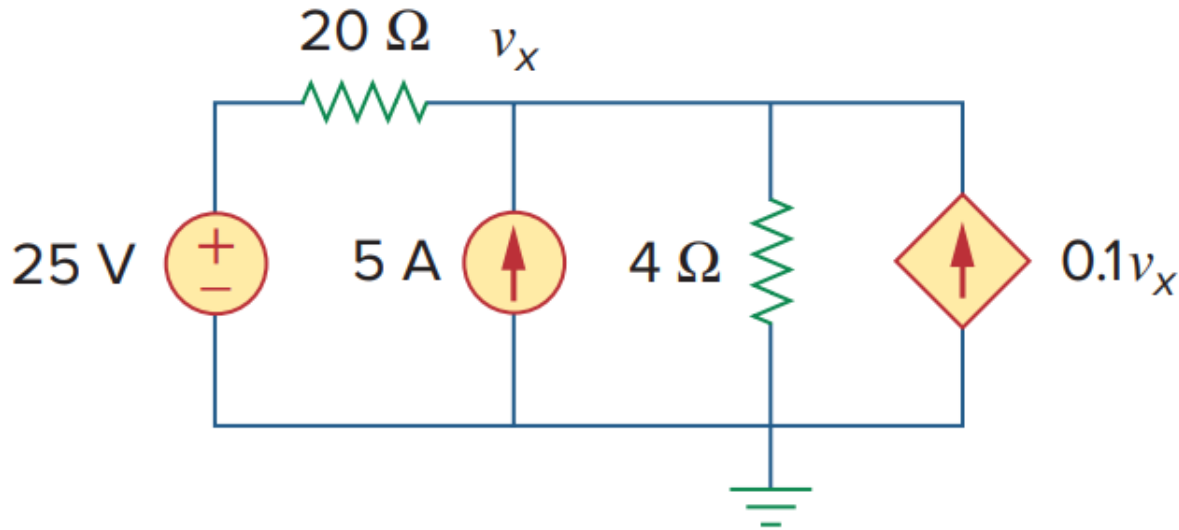
# Example 1


- Use Superposition Principle to find  $v_x$ .



There are two independent and one dependent sources. The principle requires us to determine the individual contributions of the two independent sources to the node voltage  $v_x$ . If  $v'_x$  and  $v''_x$  are the contributions from the 25 V voltage source and 5 A current source respectively, then

$$v_x = v'_x + v''_x.$$

# Example 1: 25 V source is active

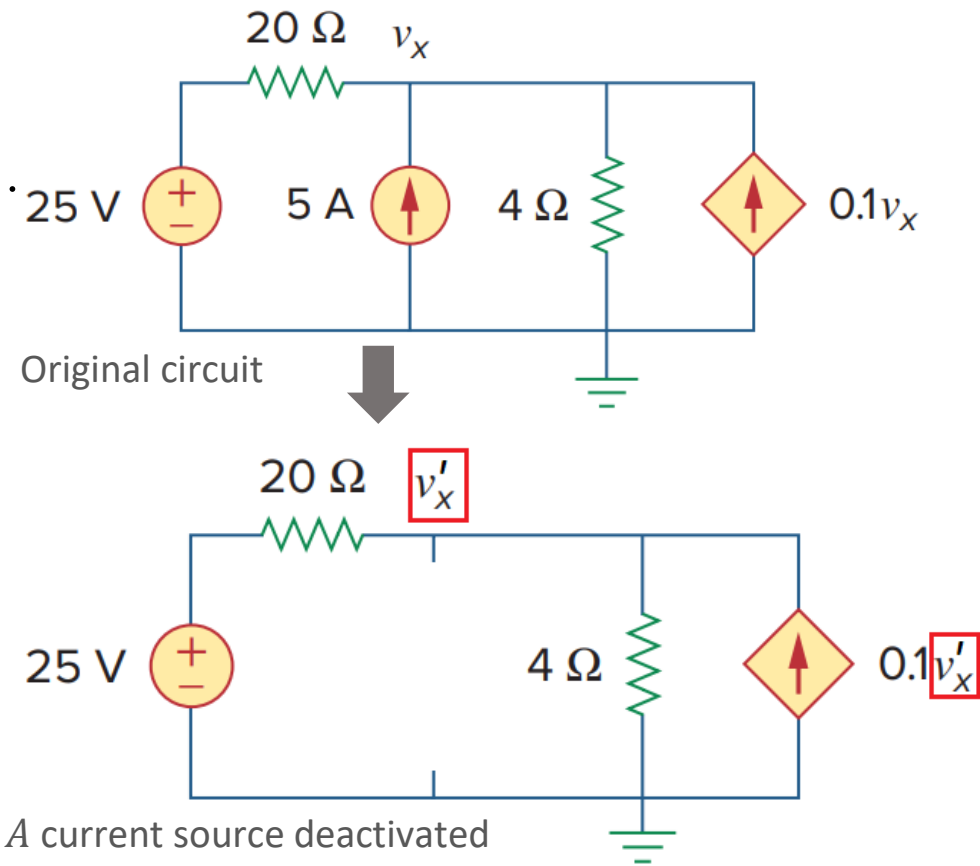



- The 5 A current source has been replaced by an open circuit. The notation  $v_x$  is replaced by  $v'_x$ .
- Different circuit solving techniques (nodal analysis or mesh analysis or source transformation or voltage division) can be applied to solve for  $v'_x$ . Nodal analysis may be the easiest one.

- KCL at the node  $v'_x$ ,

$$\frac{v'_x - 25}{20} + \frac{v'_x}{4} = 0.1v'_x$$

Simplification yields,  $v'_x = 6.25 \text{ V}$

# Example 1: 5 A source is active

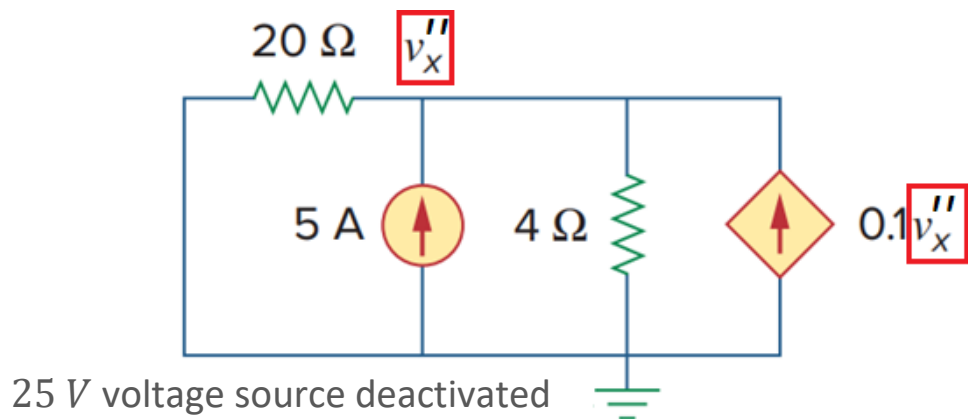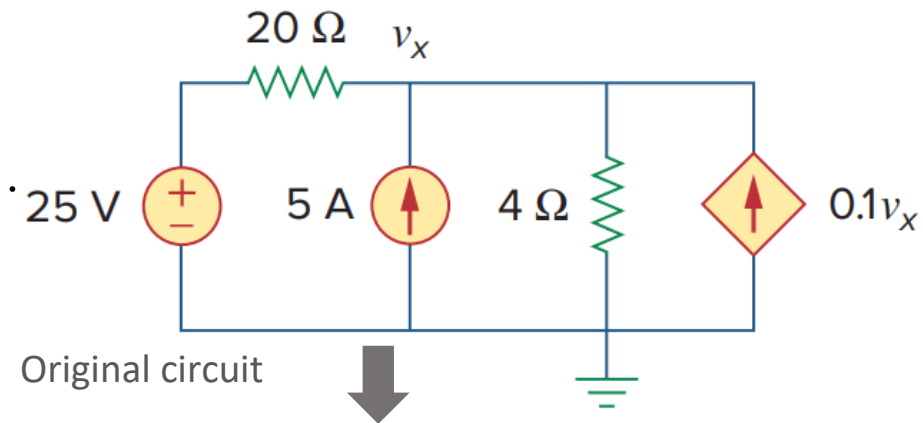

➤ The 25 V voltage source has been replaced by a short circuit. The notation  $v_x$  is replaced by  $v_x''$ .

➤ KCL at the node  $v_x''$ ,

$$\frac{v_x''}{20} + \frac{v_x''}{4} = 5 + 0.1v_x''$$

Simplification yields,  $v_x'' = 25 \text{ V}$

So, according to the Superposition Principle,


$$v_x = v_x' + v_x''$$

$$\Rightarrow v_x = 6.25 + 25 = 31.25 \text{ V}$$


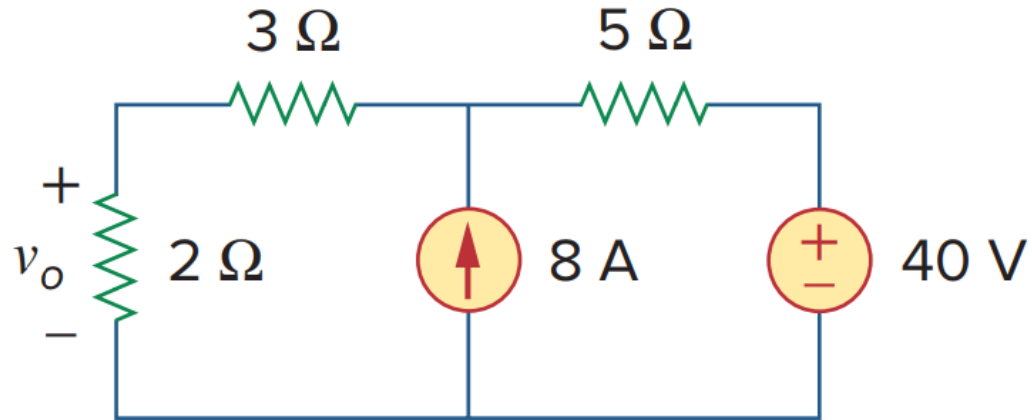
# Problem 1


- Using the Superposition Theorem, find  $v_o$ .



Ans:  $v_o = 16\ \text{V}$


When 8A is active:
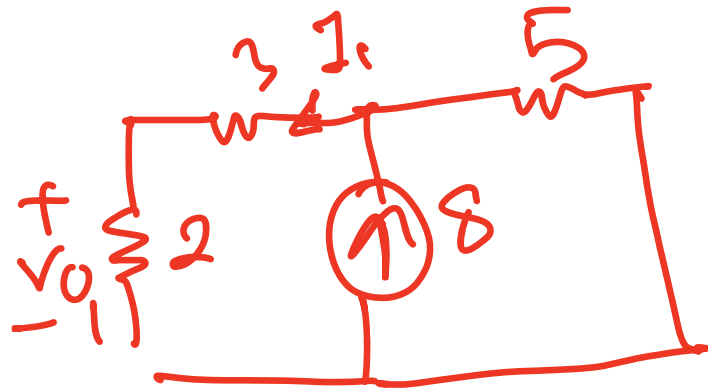
$$I_1 = \frac{5^{-1}}{5^{-1} + 5^{-1}} \times 8 = 4$$



$$V_{01} = 4 \times 2 = 8$$

When 40V is active:

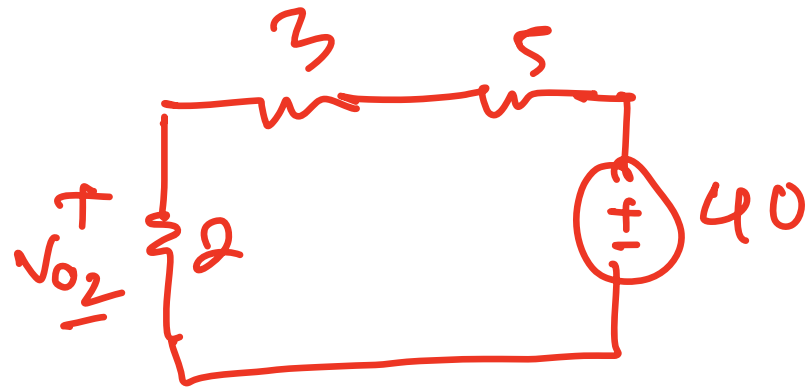


$$V_{02} = \frac{2}{2+3+5} \times 40 = \frac{2}{10} \times 40 = 8V$$

$$\therefore V_0 = V_{01} + V_{02} = 16V$$

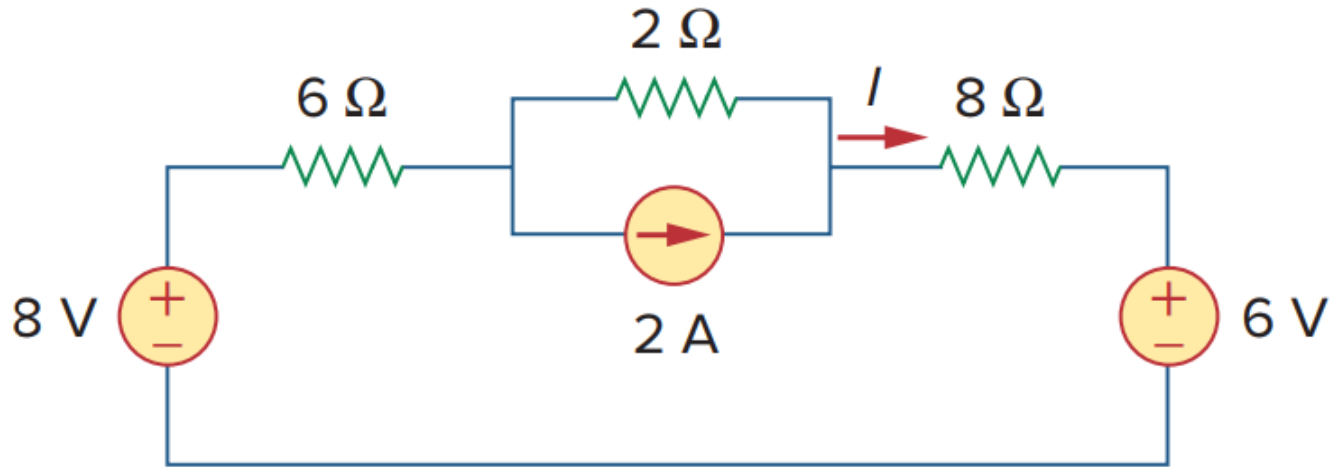
# Problem 2

- Find  $I$  in the circuit using the Superposition Principle.




Ans:  $i_0 = 0.375\text{ A}$

When 8V is active:

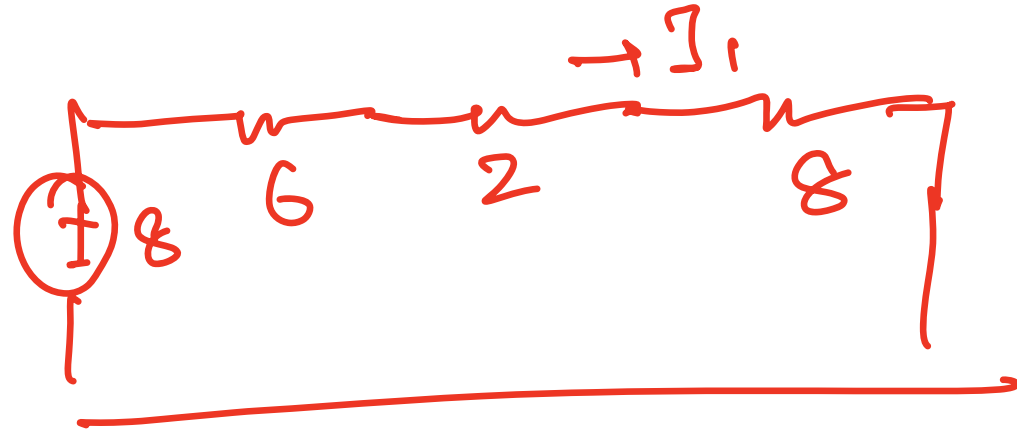


$$\therefore I_1 = \frac{8}{6+2+8}$$
$$= \frac{1}{2} \text{ A}$$

When 6V is active:

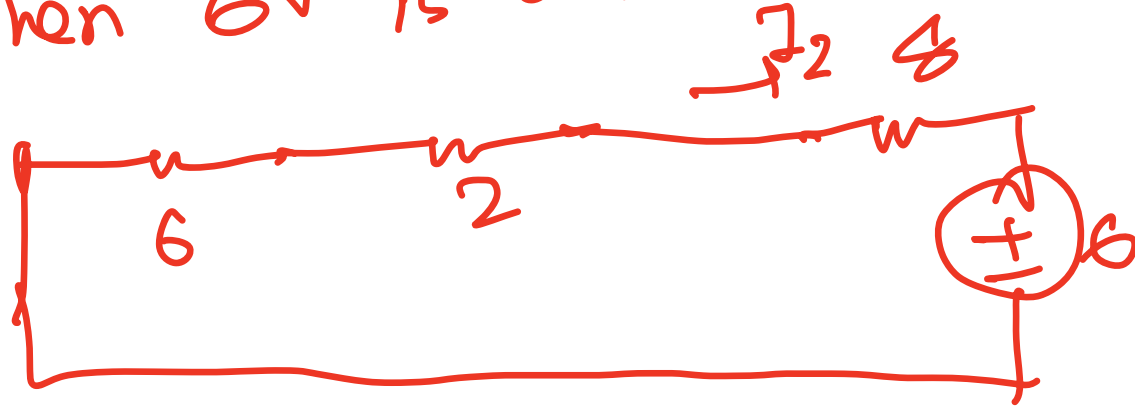

$$I_2 = \frac{-6}{8+8} \text{ A}$$
$$= -0.375 \text{ A}$$

When 2A is active:

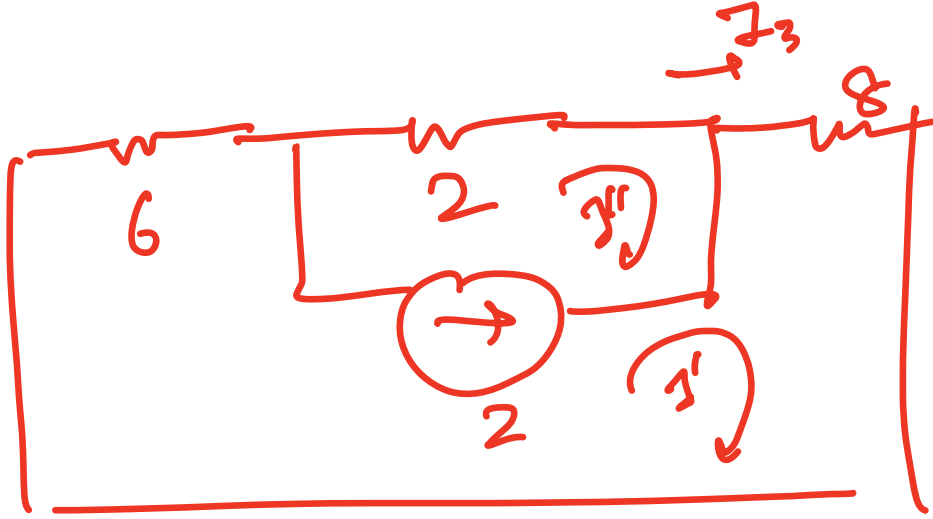

$$\therefore I_0 = I_1 + I_2 + I_3$$

$$\Rightarrow 0.375A$$

→

$$I' - I'' = 2$$

$$(6+8)I' + 2I'' = 0$$

$$14I' + 2 \cdot (I' - 2) = 0$$


$$14I' + 2I' - 4 = 0$$

$$I' = \frac{4}{16}$$

$$\therefore I_3 = \frac{4}{16}$$


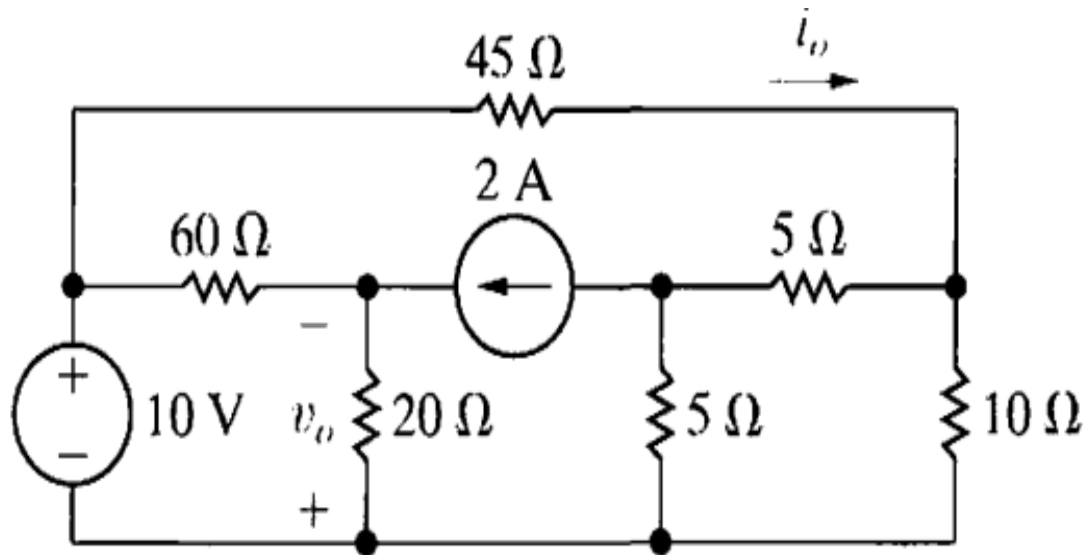
# Problem 3

- Use Superposition Principle to solve for  $i_0$  and  $v_0$ .



Ans:  $i_0 = 0.2 + 0.1 = 0.3 \text{ A}$ ;  $v_0 = -2.5 - 30 \text{ V} = -32.5 \text{ V}$

when 10V active:

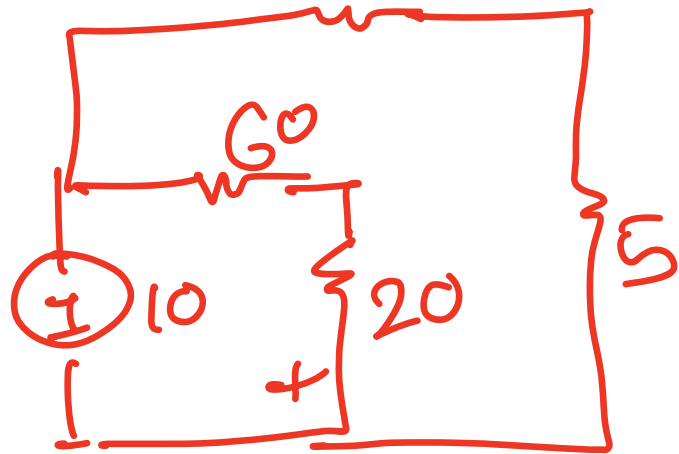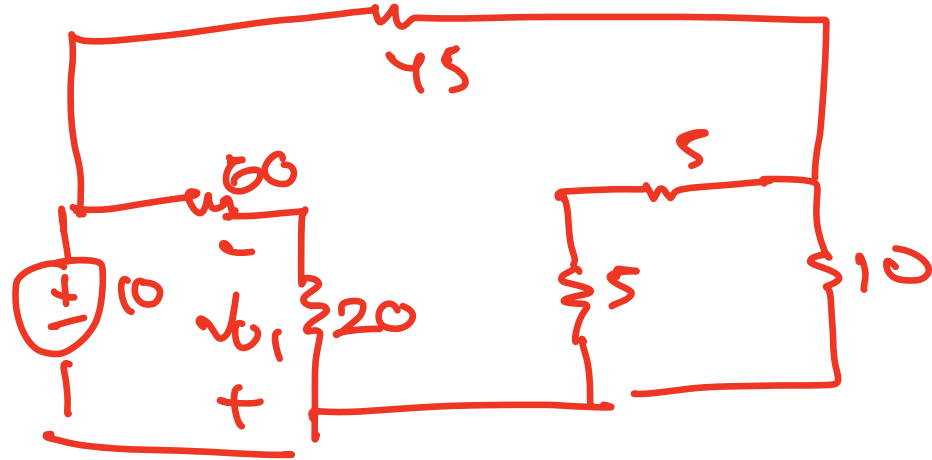

$$\therefore V_{o1} = -\frac{20}{60+20} \times 10$$


$$= -2.5V$$

$$i_{o1} = \frac{10}{50}$$

$$= 0.2A$$



When 2A active:

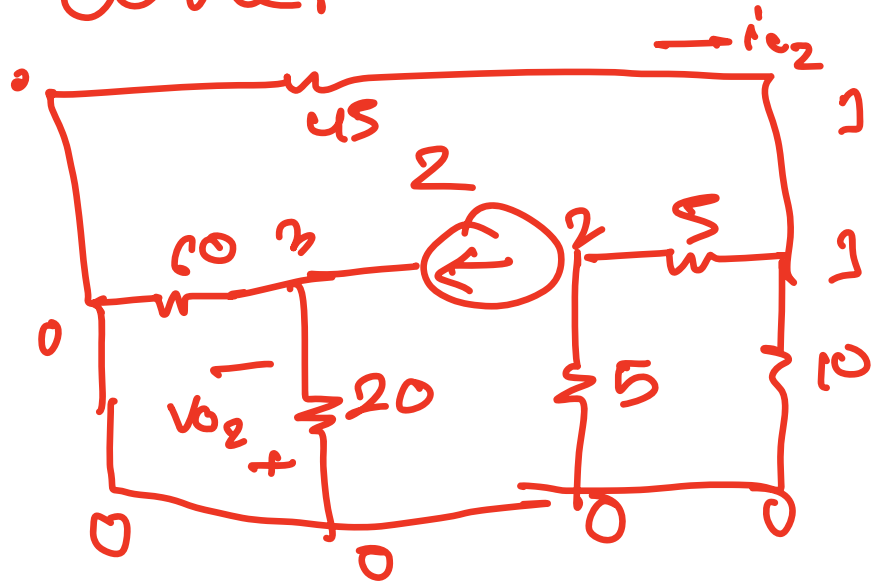


$$\text{So, } V_{02} = -2 \times 15 = -30$$

$$\text{So, } V_0 = V_{01} + V_{02} = -30 - 2 \times 5$$

$$\hat{i}_0 = \hat{i}_{01} + \hat{i}_{02} = 0.1 + 0.2$$

20 || 60 and 45 || 10

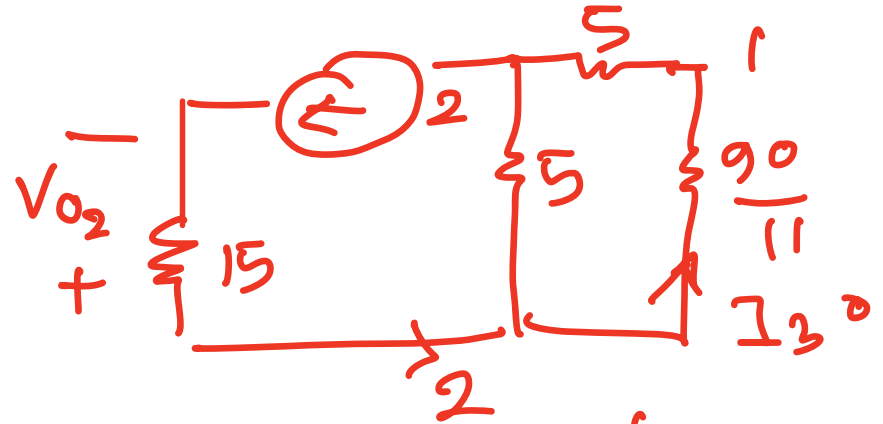


$$I_3 = \frac{(5 + 90/11)^{-1}}{(5 + 90/11)^{-1} + 5^{-1}} \times 2$$

$$i_{02} = \frac{I_3 \times 90/11}{45} = 0.1A$$


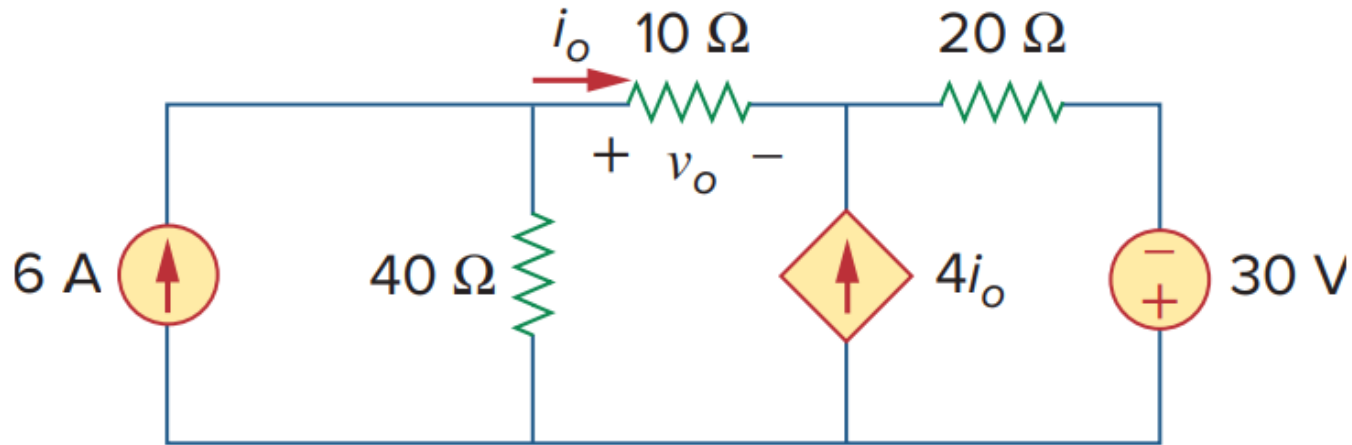
# Problem 4

- Use the Superposition Principle to find  $i_o$  and  $v_o$ .



Ans:  $i_o = 1.8 \text{ A}$ ;  $v_o = 18 \text{ V}$

6A active:

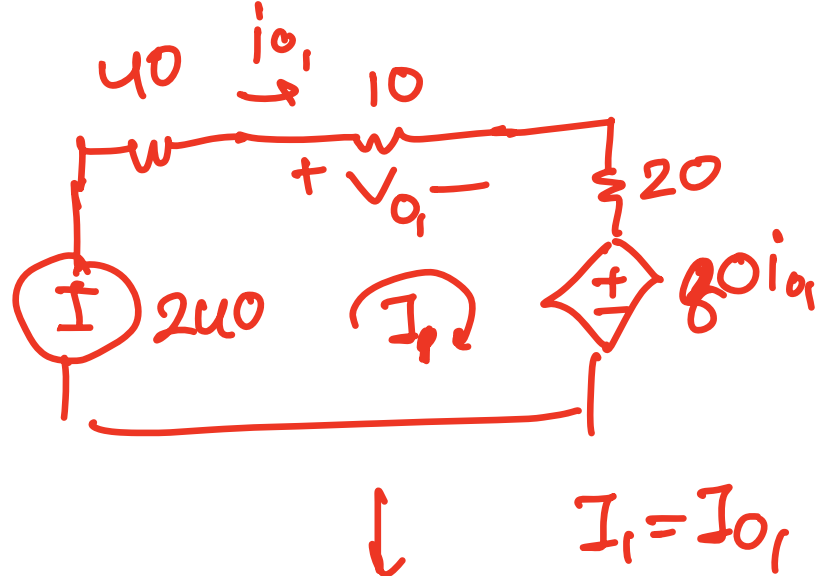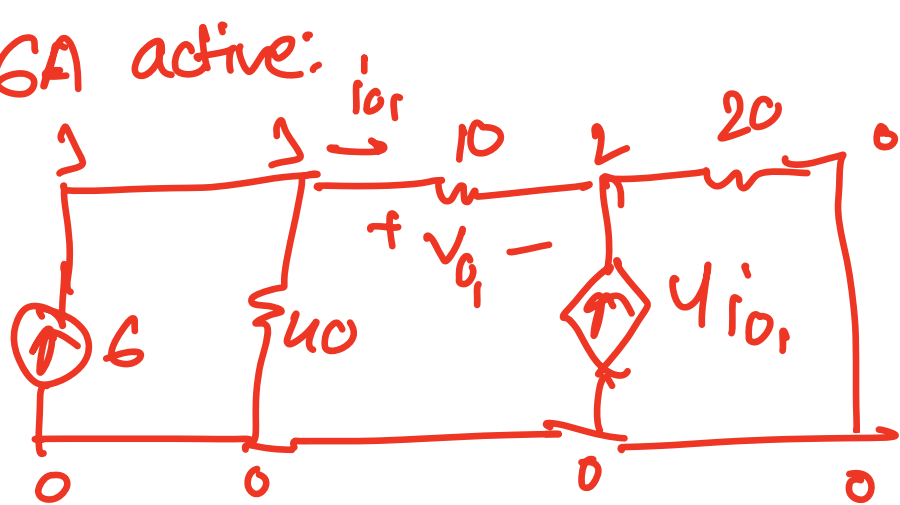


$$-240 + (40 + 10 + 20)I_1 + 80I_1 = 0$$

$$\therefore I_1 = 1.6 \text{ A}$$

$$V_{o1} = 10 \times 1.6 = 16 \text{ V}$$



When 30V active:

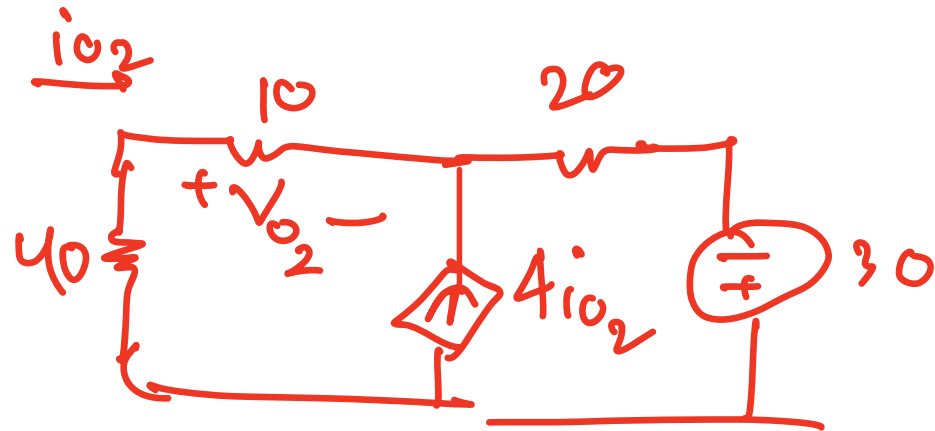

$$i_{o2} = - \frac{50^{-1}}{50^{-1} + 20^{-1}} \times (4i_{o2} - 3/2)$$

$$i_{o2} + \frac{50^{-1}}{50^{-1} + 20^{-1}} \times (4i_{o2} - 3/2) = 0$$
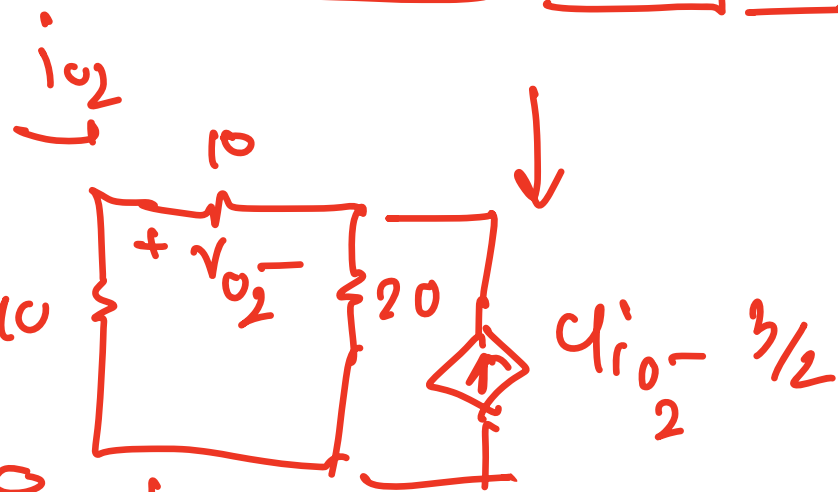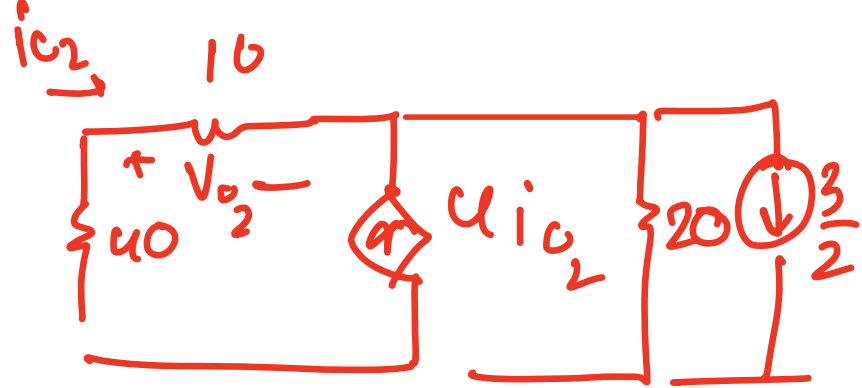
$$\therefore i_{o2} = 0.2A \quad \text{So, } V_{o2} = 2V$$




$$\text{So, } i_{o2} = 1.6 + 0.2 = 1.8$$

$$V_o = 16 + 2 = 18$$

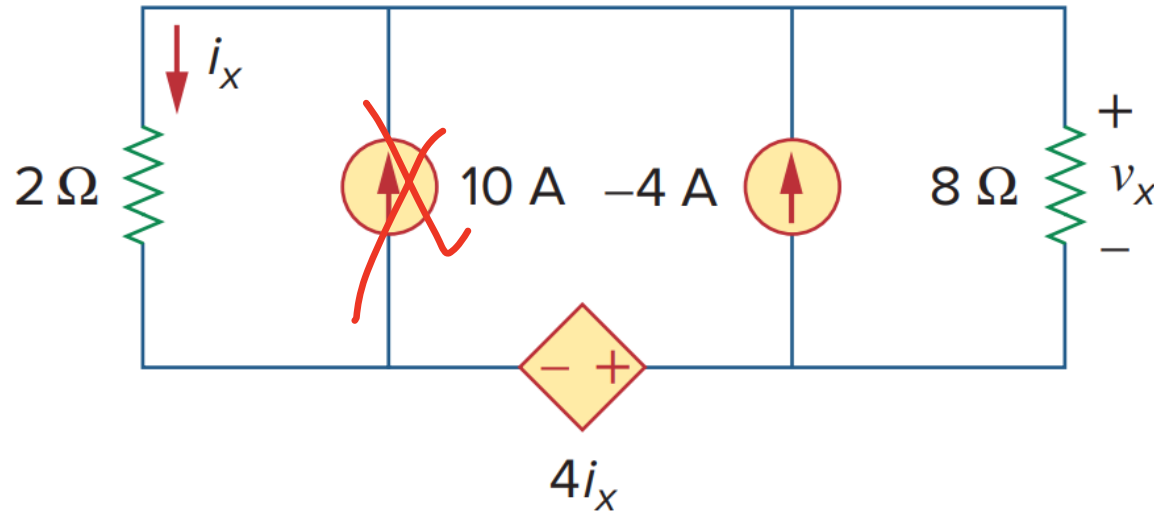
# Problem 5

- Use Superposition Principle to solve for  $v_x$ .



Ans:  $v_x = -16\text{ V}$

10A active:

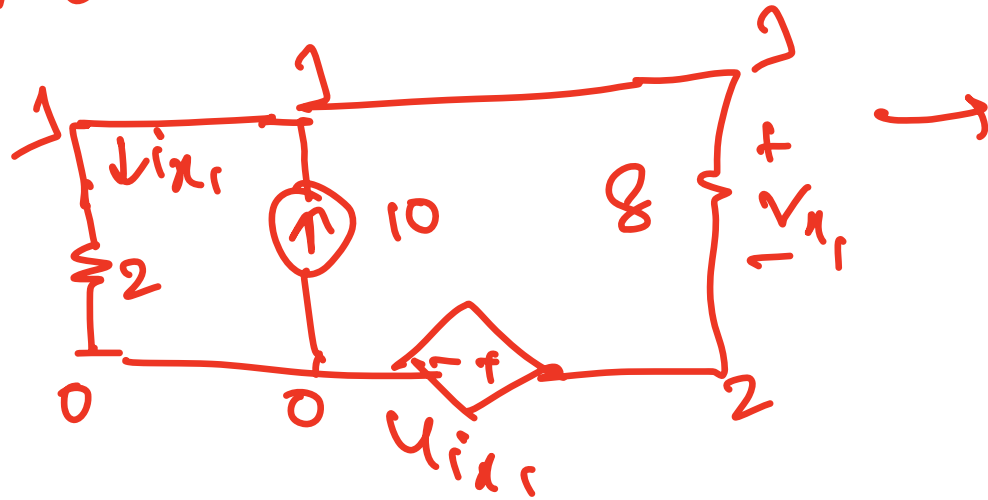

$$i_{x1} = v_1/2$$

$$v_2 = 4i_{x1}$$

$$v_2 = 4 \cdot \frac{v_1}{2} \Rightarrow 2v_1 - v_2 = 0 \quad \text{--- (1)}$$

At node 1:


$$v_1 \left( \frac{1}{2} + \frac{1}{8} \right) - \frac{v_2}{8} = 10$$

$$\frac{5}{8}v_1 - \frac{v_2}{8} = 10$$

$$v_1 = 80/3$$

$$v_2 = 160/3$$

$$v_{x1} = -80/3$$

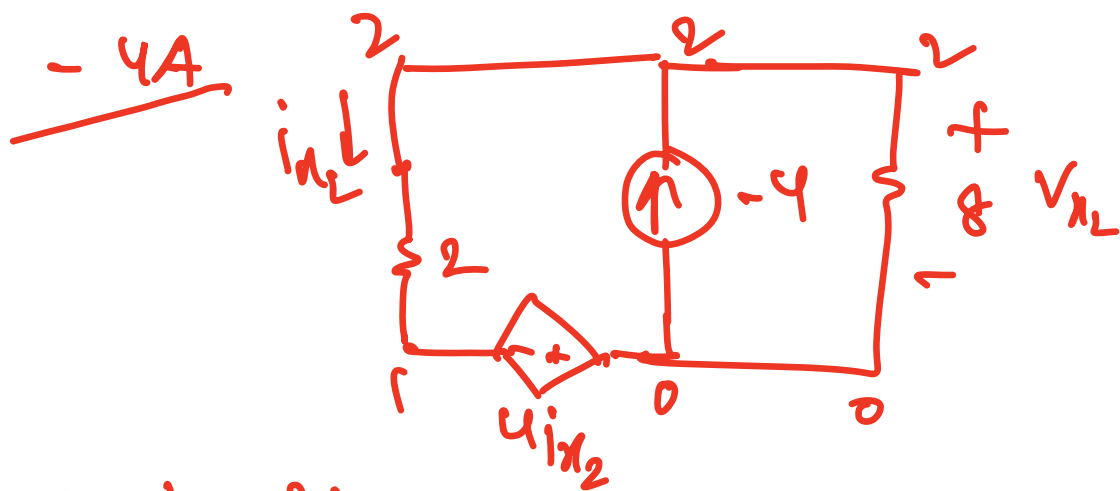

node 2:

$$V_2 \left( \frac{1}{2} + \frac{1}{2} \right) - \frac{V_1}{2} = -4$$

$$V_{x2} = V_2 = \frac{32}{3}$$

S.,  $V_x = \frac{32}{3} - \frac{80}{3} = -16V$

$$i_{x2} = \frac{V_2 - V_1}{2}$$

$$V_0 - V_1 = 4i_{x2}$$

$$-V_1 = 4 \cdot \frac{V_2 - V_1}{2}$$

$$-V_1 = 2V_2 - 2V_1$$

$$V_1 - 2V_2 = 0 \quad \text{--- (1)}$$

# Practice Problems

- Additional recommended practice problems: [here](#)
- Other suggested problems from the text book: [here](#)



Thank you for your attention

# Course Outline: broad themes

