

ID:

Name:

**Brac University**

Semester: Spring 2023

Course Code: CSE250

Circuits And Electronics

Set

A

Assessment: *Final*

Duration: 2 hours

Date: May 2, 2023

Full Marks (incl. bonus 5): 55

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ At the end of the exam, both the **answer script** and the **question paper** must be returned to invigilator.
- ✓ All **3 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Symbols have their usual meanings.

■ Question 1 of 3 [CO2 CO3 CO4] [20 marks]

Consider the following circuit with open terminals **a** and **b**. Currently, no load is connected to the terminals.


(a)

$$R_L = R_{Th} = 4\Omega$$

(b)

$$V_{Th} = 3V$$

$$P_{max} = 0.5625 W$$

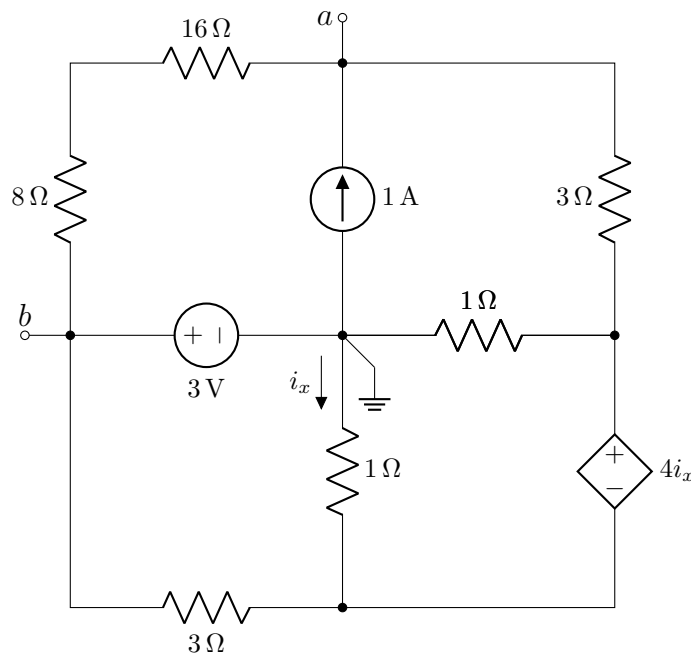


(a) [12 marks] Determine the value of R_L that will draw the **Maximum Power** from the circuit.

(b) [8 marks] Determine the value of the **Maximum Power**.


■ Question 2 of 3 [CO4 CO5] [20 marks]

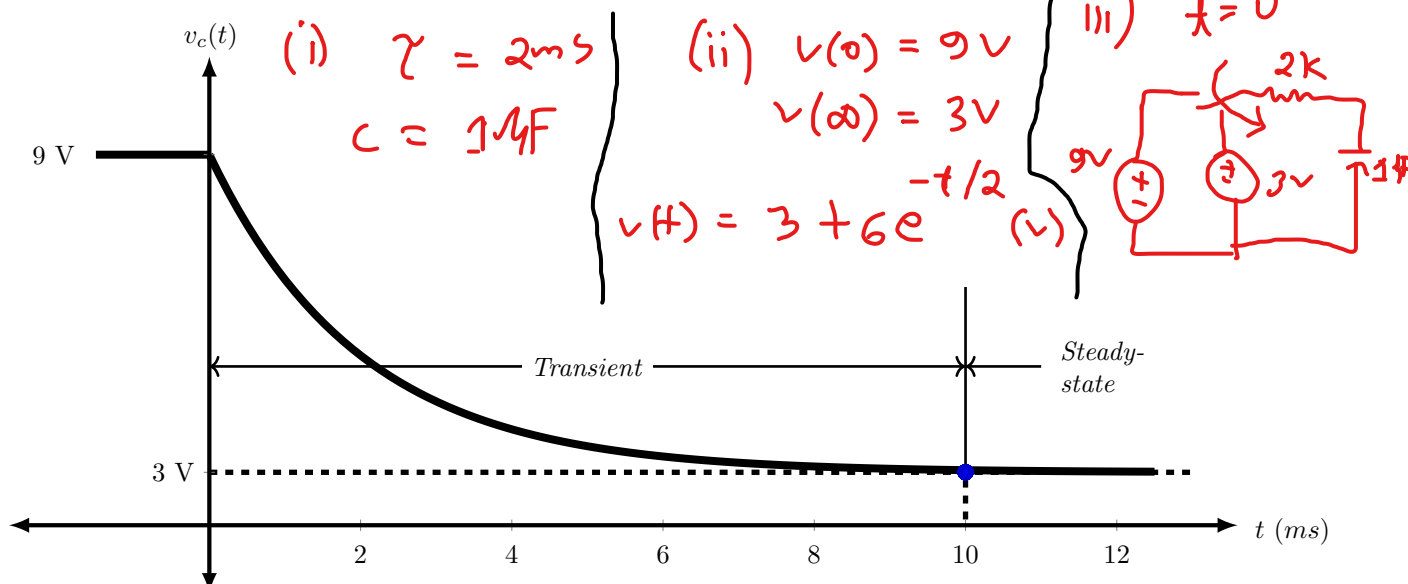(a) The $v_c(t)$ vs t plot below shows the voltage response of a capacitor (C) in a series RC circuit to a sudden change in the DC voltage applied through an equivalent resistance of $2 k\Omega$.



- (i) [2 marks] Determine the approximate **Time Constant** from the figure. Determine C with appropriate unit.
- (ii) [1 mark] Write a mathematical expression of $v_c(t)$ for $t > 0$.
- (iii) [2 marks] Predict and draw a circuit with appropriate switching mechanism that can generate the voltage response as shown in the plot.

(b) Consider the following circuits.

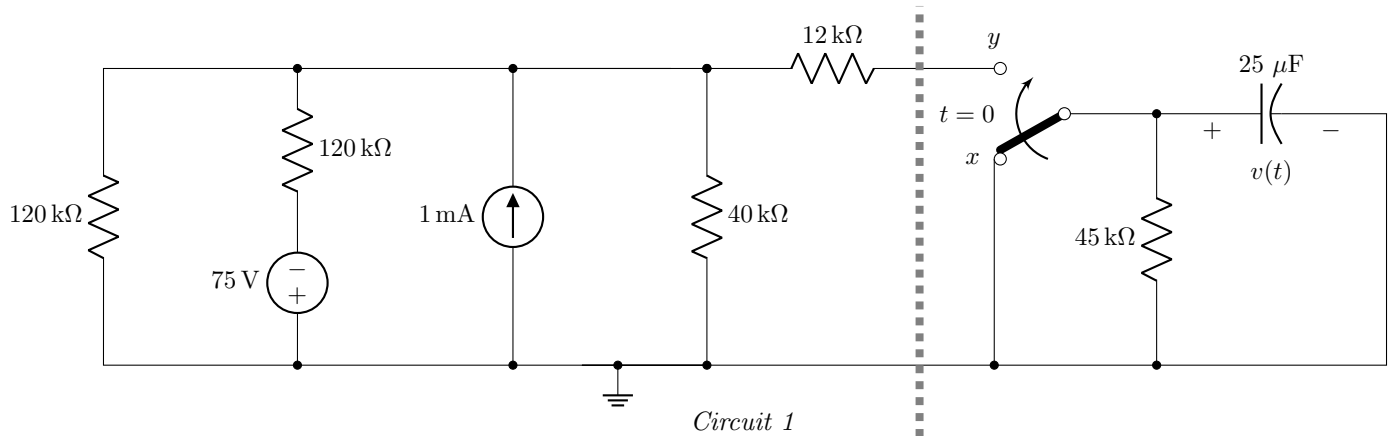


(i) $V_1 = 9V$

$R_1 = 36\Omega$

ii) $v(0) = 0$

$v(\infty) = 5V$

$\tau = 0.5s$

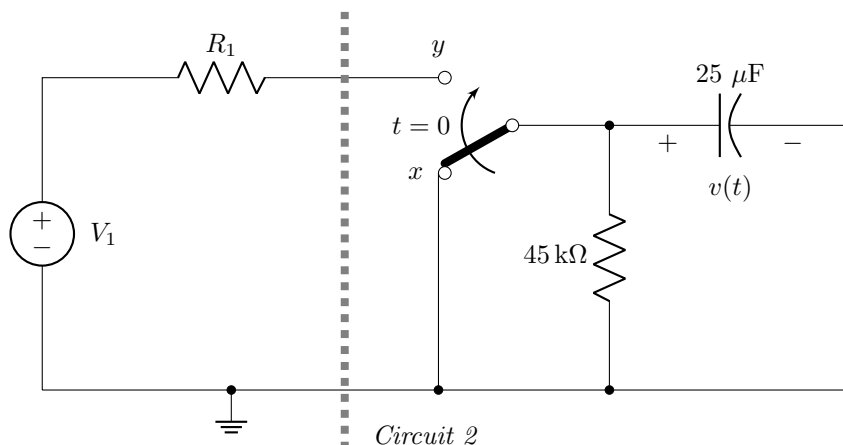


$v(t) = 5 - 5e^{-2t} (V), t > 0$

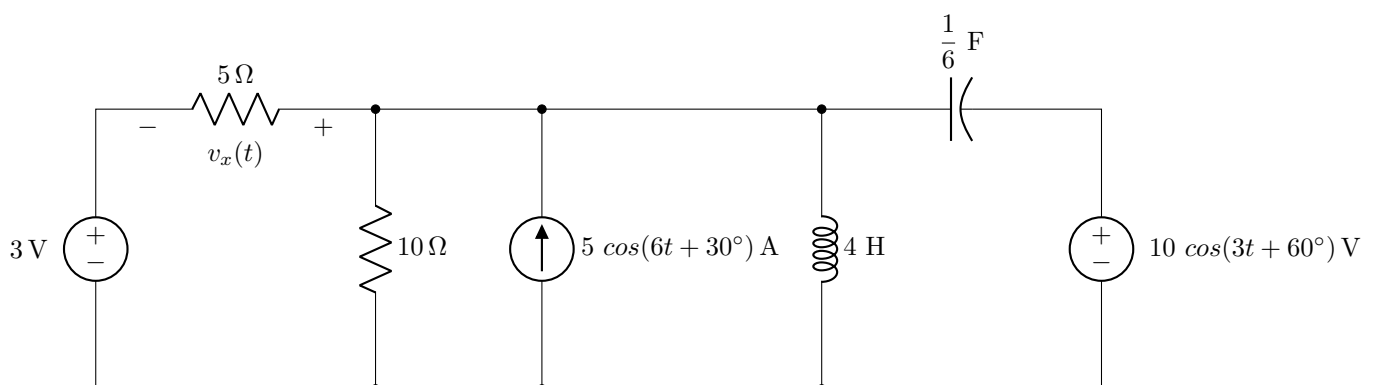- (i) [7 marks] Reduce the left portion with respect to the dashed gray line of *Circuit 1* so that it takes the form of *Circuit 2* as shown. Write down the values of V_1 and R_1 .
- (ii) [8 marks] Now, analyze the **Transient Behavior** of the circuit assuming that the switch moves from position x to position y at $t = 0$. Determine $v(t)$ for $t > 0$.

■ Question 3 of 3 [CO4 CO6] [15 marks]

Determine $v_x(t)$ in the circuit shown below.



$v_x(t) = -3 + 4.61 \cos(6t + 103.96^\circ) + 9.74 \cos(3t + 95.75^\circ)$