
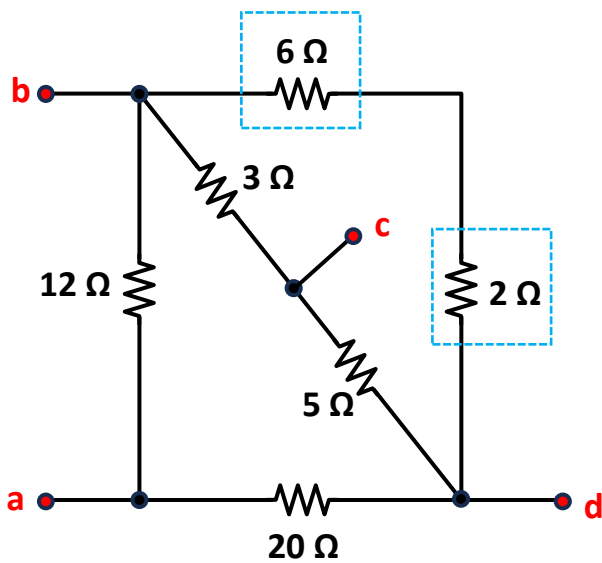



Equivalent resistance between a and b

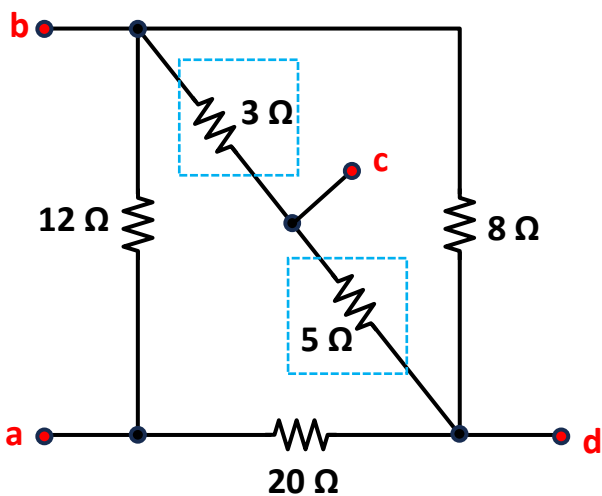


$6\ \Omega$ and $2\ \Omega$ are in series



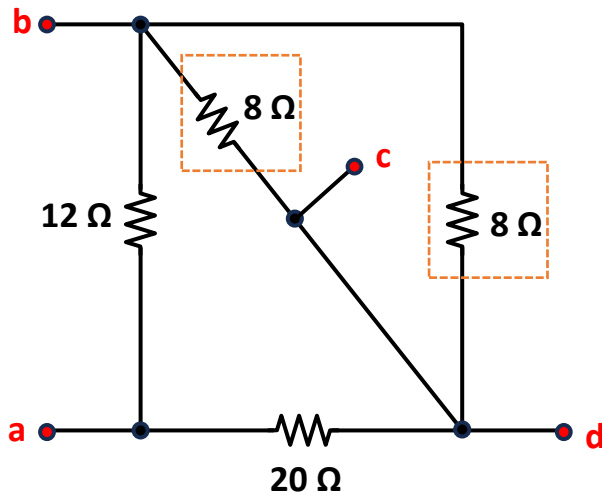
$3\ \Omega$ and $5\ \Omega$ are in series,



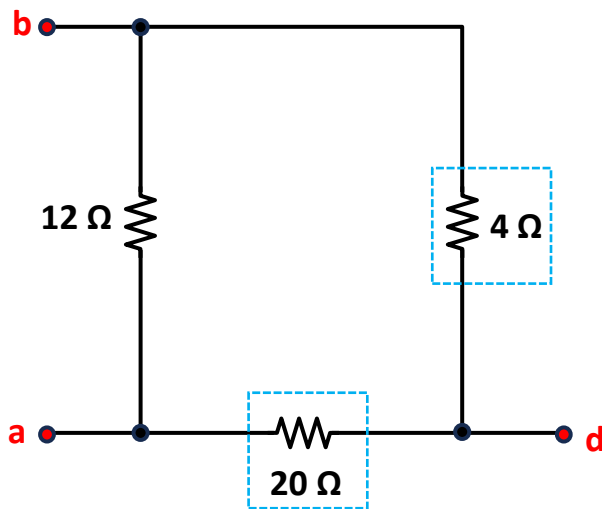
$8\ \Omega$ and $8\ \Omega$ are in parallel



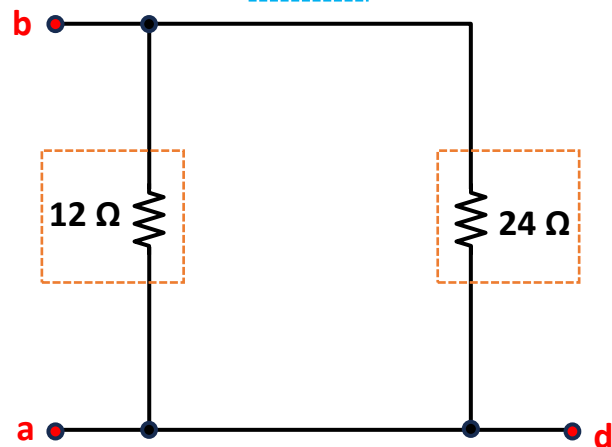
$4\ \Omega$ and $20\ \Omega$ are in series



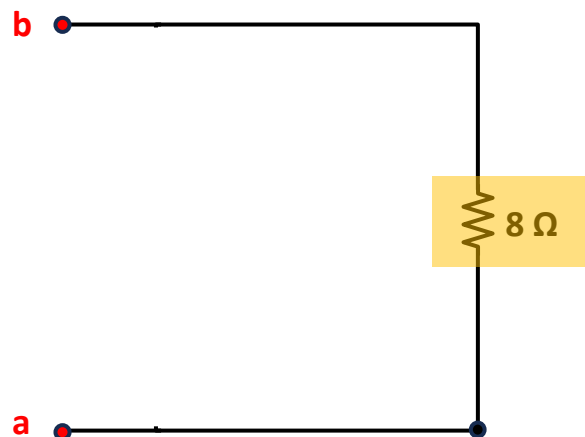
$12\ \Omega$ and $24\ \Omega$ are in parallel



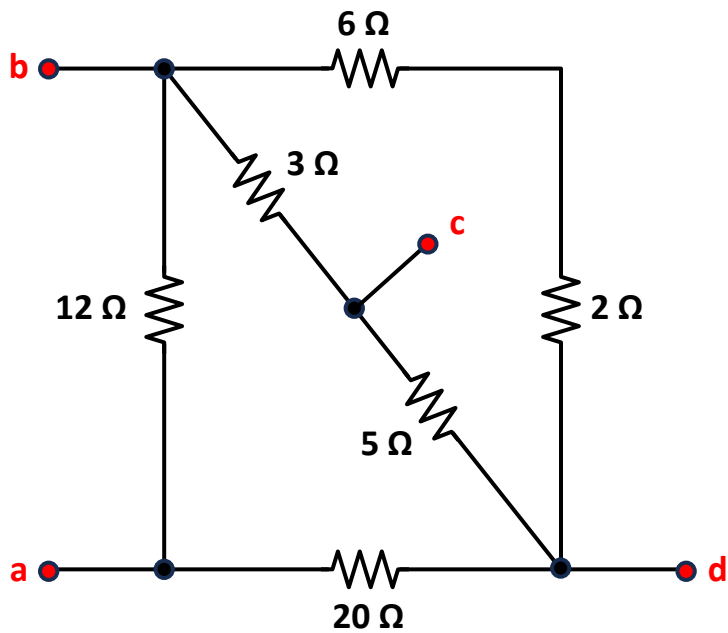
Equivalent resistance between **a** and **b** is $8\ \Omega$




Equivalent resistance between a and d

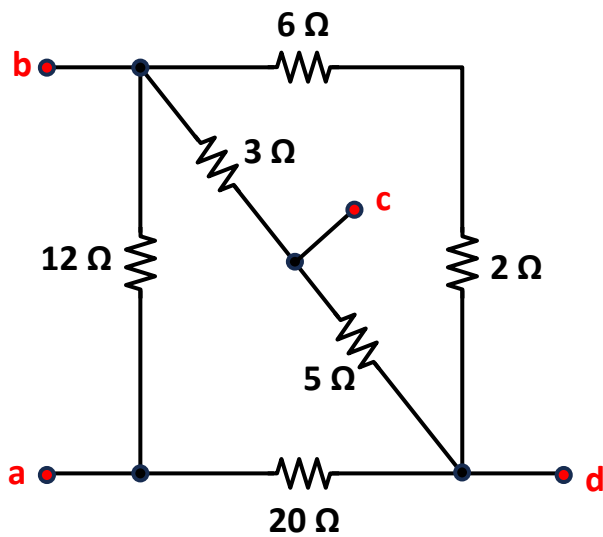


Let us rotate the circuit 90°
Clockwise

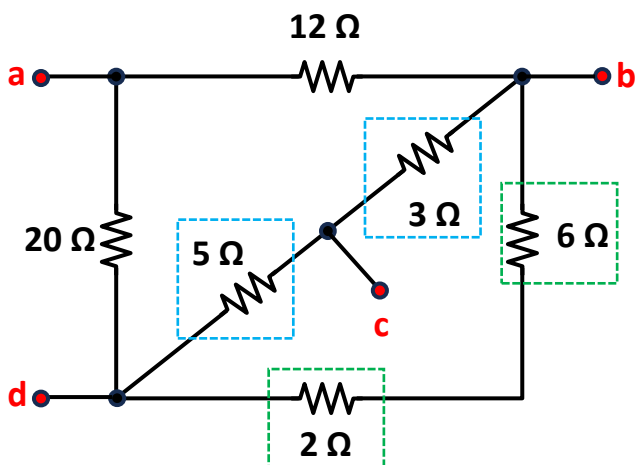

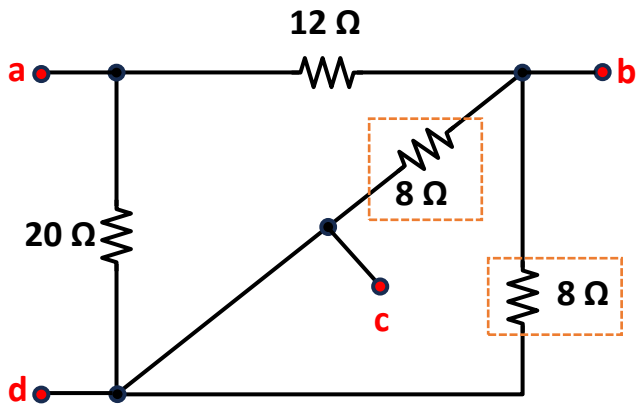
$5\ \Omega$ and $3\ \Omega$ are in series
 $6\ \Omega$ and $2\ \Omega$ are in series




8 Ω and 8 Ω are in parallel,

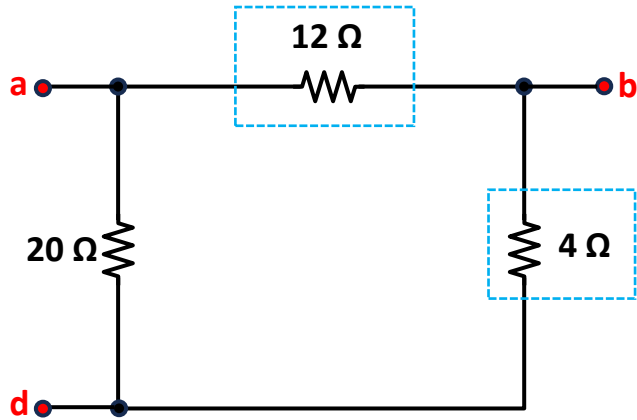


12 Ω and 4 Ω are in series

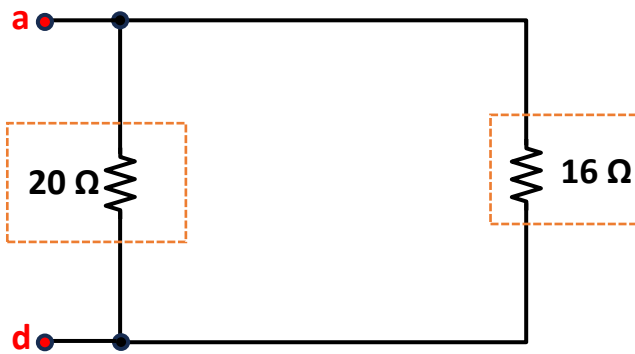


16 Ω and 20 Ω are in parallel

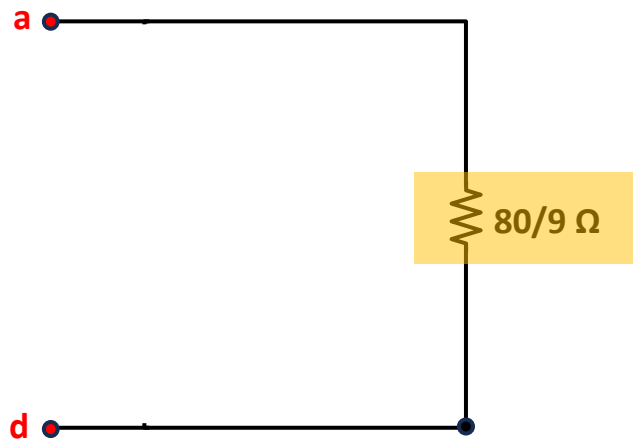


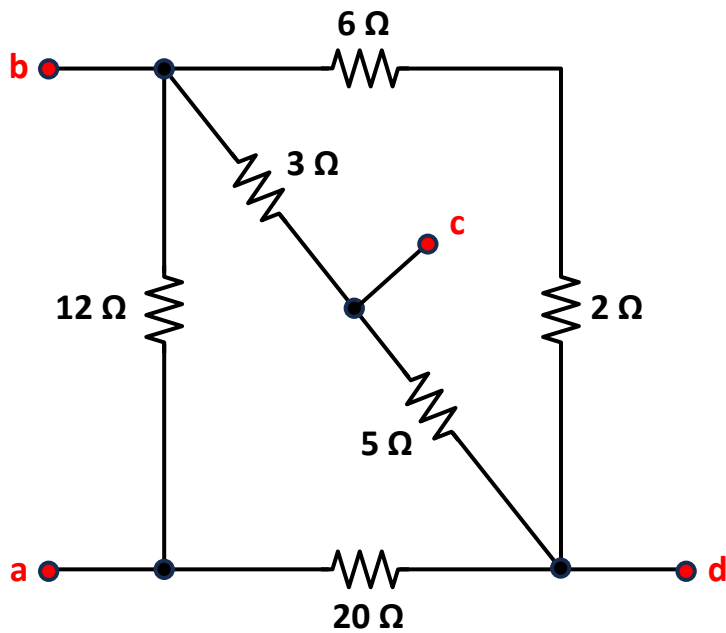
Equivalent resistance between a and d is $\frac{80}{9} \Omega$






Equivalent resistance between b and d

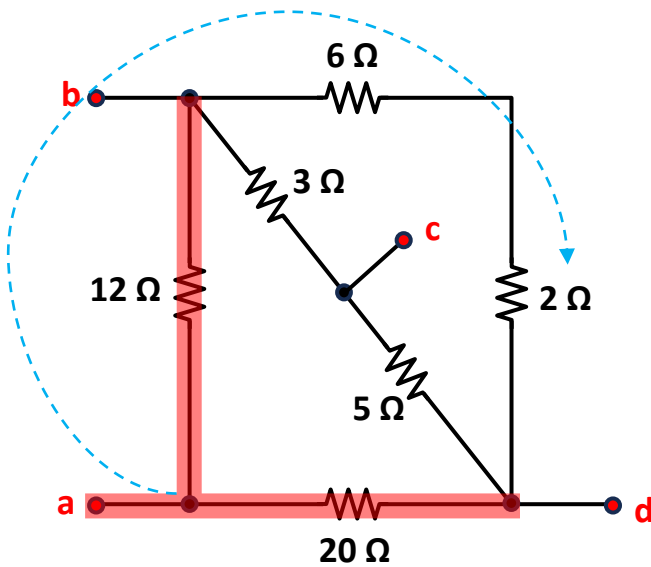

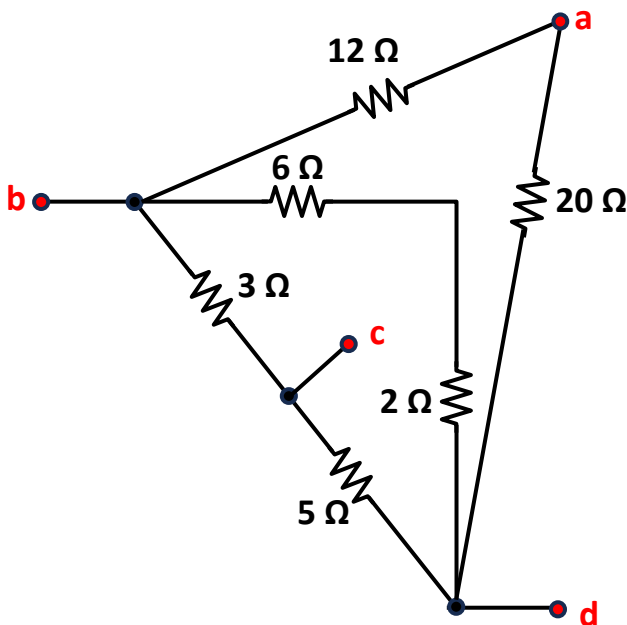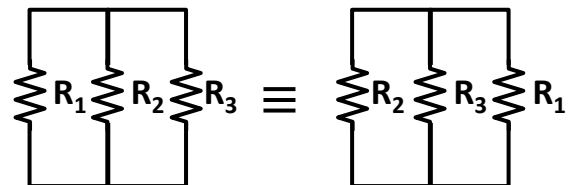
Let us bring the red portion in right side of b and d node. It does not change anything about the circuit



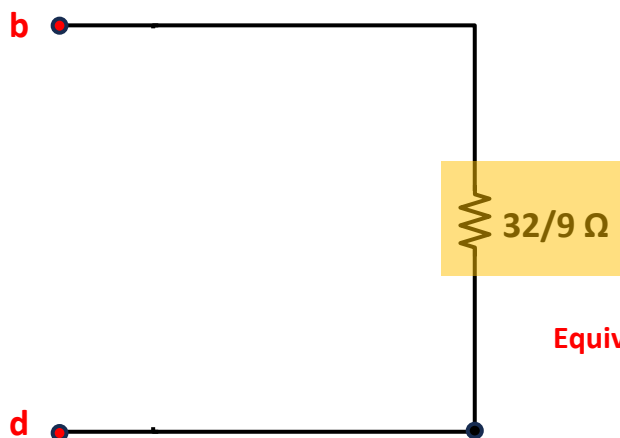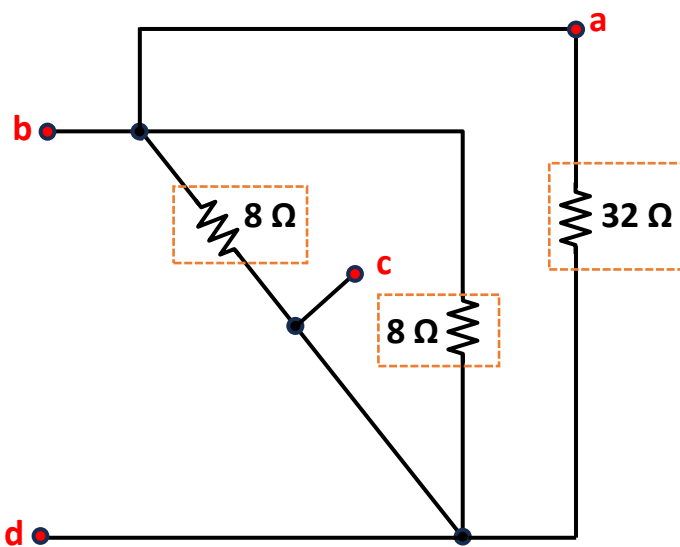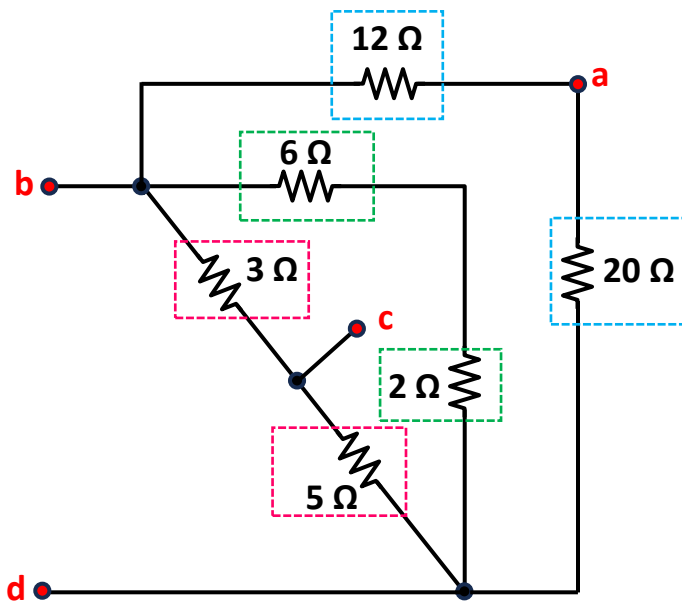
Let us just make the circuit visually better.




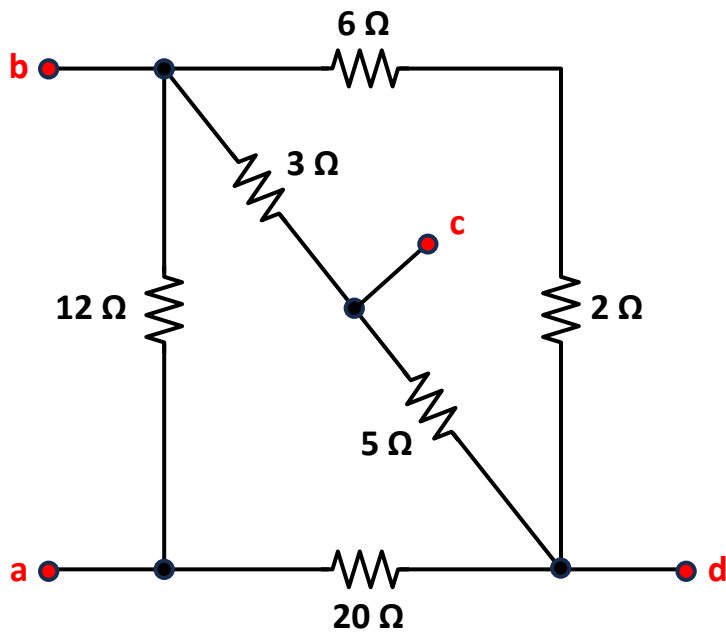
Equivalent resistance between a and d is 32/9 Ω




Equivalent resistance between b and c

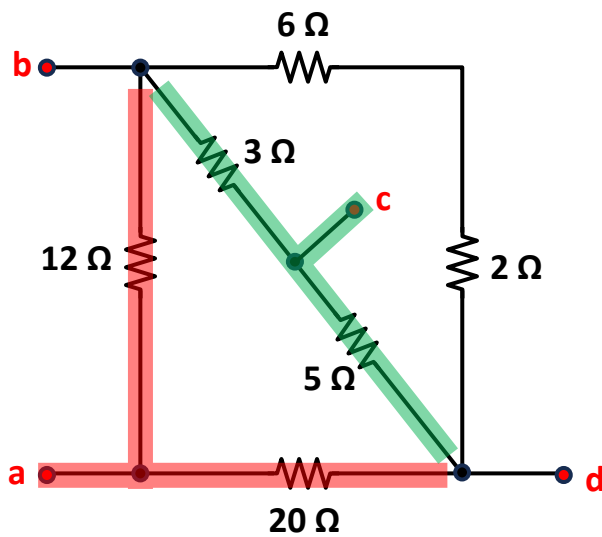

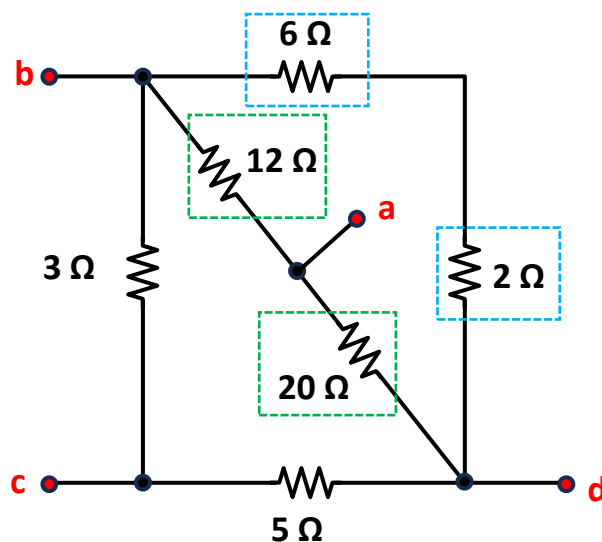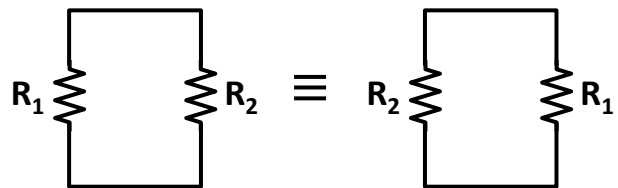
Let us exchange the position of the green portion and red portion. As the common nodes (b and d) are same. So exchanging their position will not effect the circuit



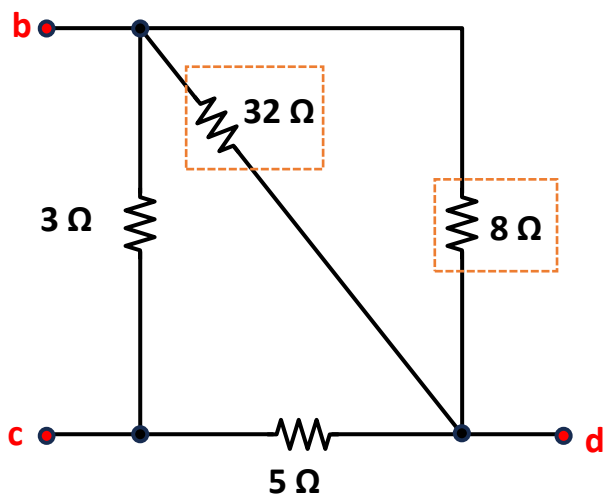
6 Ω and 2 Ω are in series
12 Ω and 20 Ω are in series



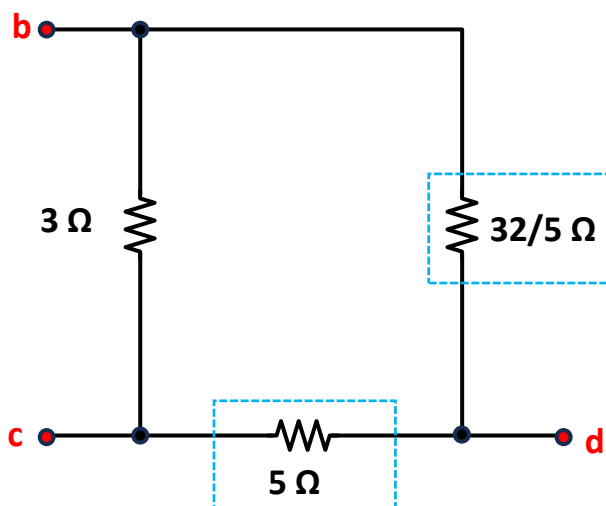
$32\ \Omega$ and $8\ \Omega$ are in parallel



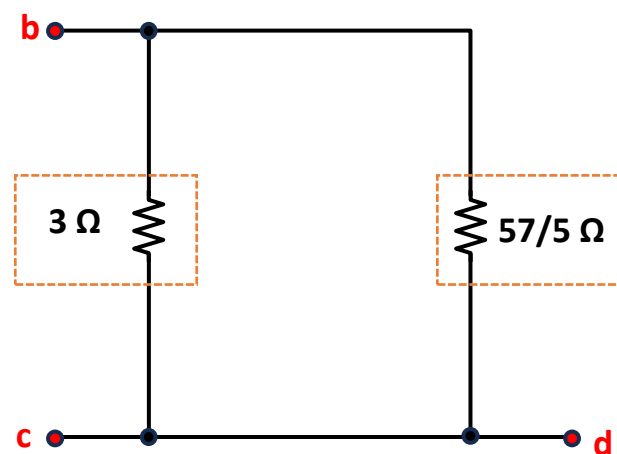$32/5\ \Omega$ and $5\ \Omega$ are in series



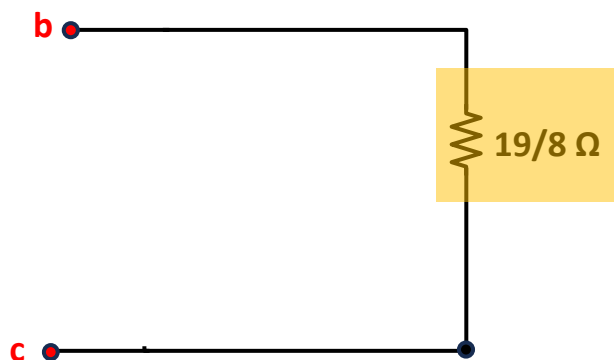$57/5\ \Omega$ and $3\ \Omega$ are in parallel



Equivalent resistance between b and c is $19/8\ \Omega$