

ID:

Name:

Set: 2

Brac University

Semester: Summer 2022

Course No: CSE250

Course Title: CIRCUITS AND ELECTRONICS


Date: September 09, 2022

Final Exam


Full marks: 50 (+5 Bonus)

Duration: 2 hours

Question 1 of 3 [20 marks]

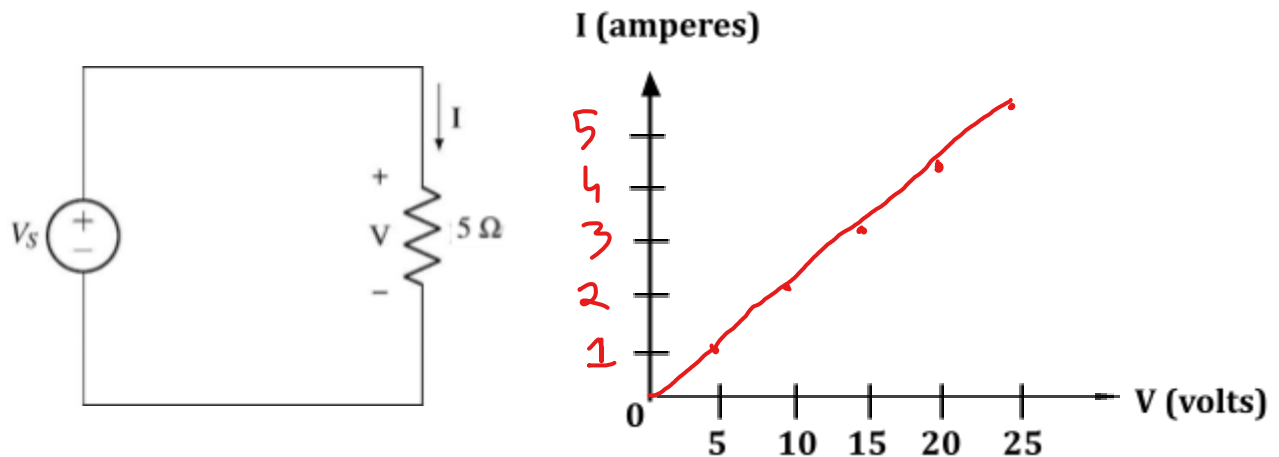

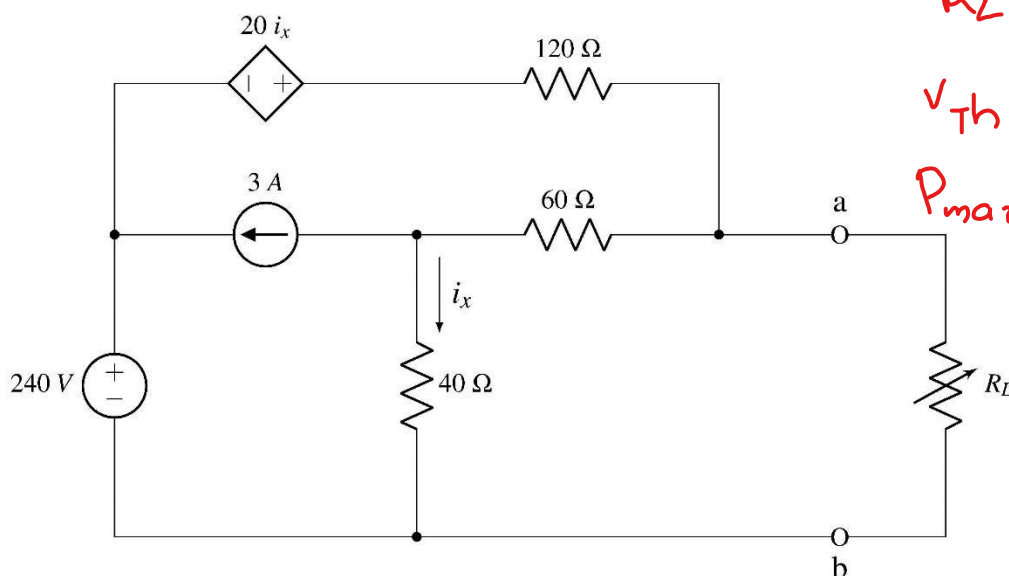- **Draw the I-V characteristics** of the $5\ \Omega$ resistor shown in the circuit above. Please redraw the plot template given above on your script. You must label the axes with appropriate values.
(2 marks) [CO1]



$$R_L = 60\ \Omega$$



$$V_{Th} = 30\text{ V}$$

$$P_{max} = 3.75\text{ W}$$

- **Determine** the value of R_L that will draw **Maximum Power** from the rest of the circuit.
(10 marks) [CO3, CO4]
- **Determine** that value of the **Maximum Power**.
(8 marks) [CO2, CO4]

Set: 2

Question 2 of 3 [20 marks]

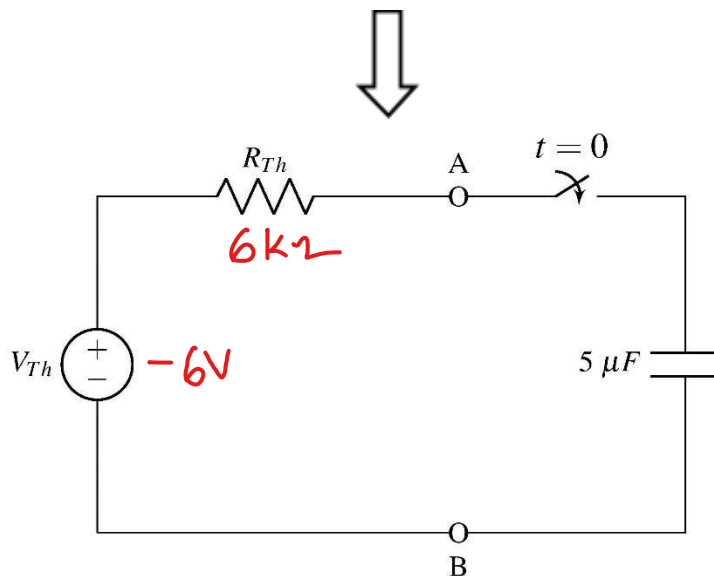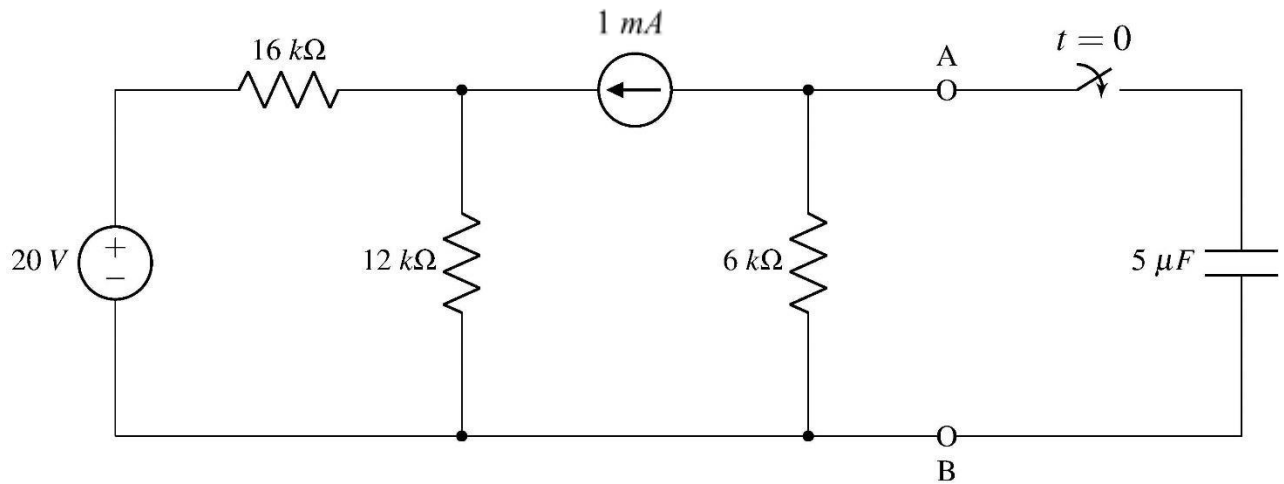

- **Reduce** the first circuit so that it takes the form of the 2nd circuit as shown above. [Hint: Use Thevenin's principle]
(8 marks) [CO4]
- **Perform** transient analysis to determine $v(0)$, $v(\infty)$, and $v(t)$ for $t > 0$. Also, determine the **current through the capacitor** at $t = 0.5 \text{ ms}$.
(9 marks) [CO5]

$$v(0) = 0 \text{ V}$$

$$v(\infty) = -6 \text{ V}$$

$$\tau = 30 \text{ ms}$$

$$v(t) = -6 + 6e^{-t/30}, \quad t > 0$$


$t \rightarrow \text{ms}$

Set: 2

$$\tau = 10 \text{ ms}$$


$$C = 54 \text{ F} - t/10, t > 0 \text{ ms}$$

$$v(t) = 6 - 6e^{-t/10}$$

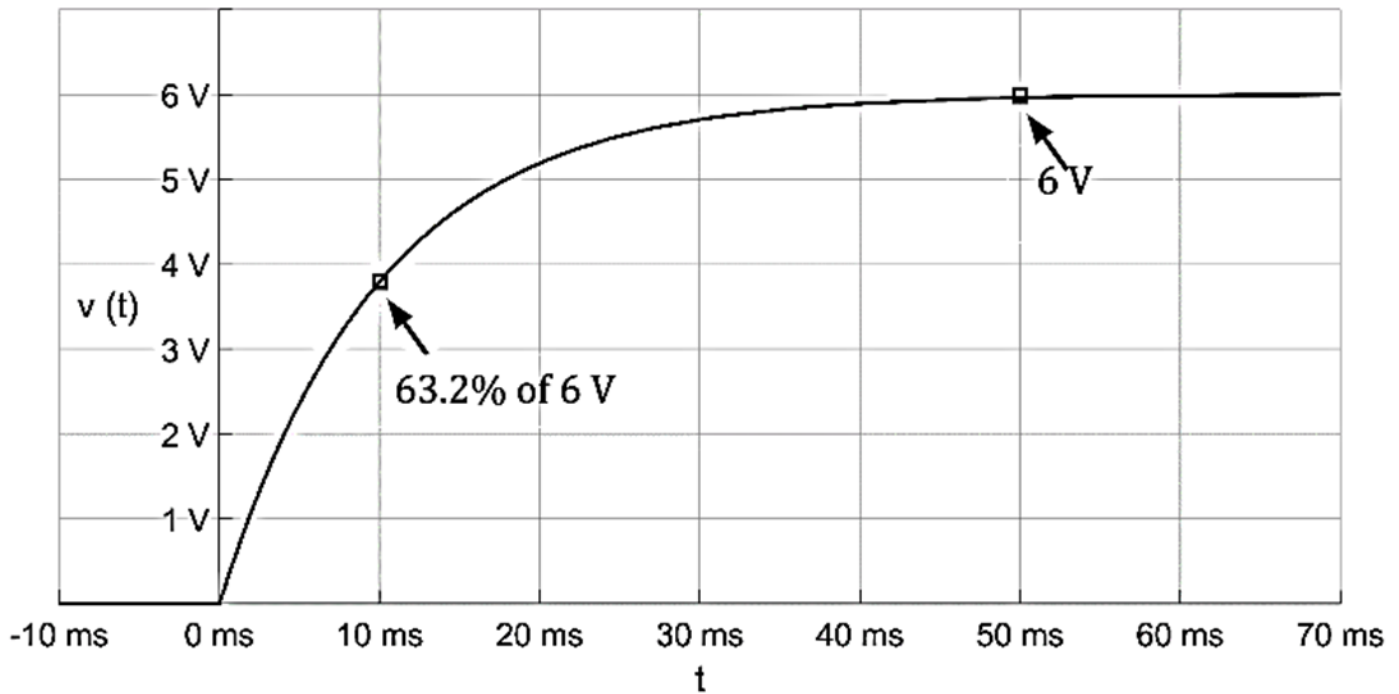

- The figure above shows the voltage response of a series RC circuit to a sudden DC voltage applied through an equivalent resistance of $2 \text{ k}\Omega$. **Determine** the approximate **time constant** from the figure. Also, **determine** the value of the **capacitor** used in the RC circuit and find the **expression** for $v(t)$ as only a function of t . [Hint: Time constant is the time required for the capacitor voltage to reach to 63.2% of its final value from an initially discharged state]
(3 marks) [CO5]

Question 3 of 3 [15 marks]

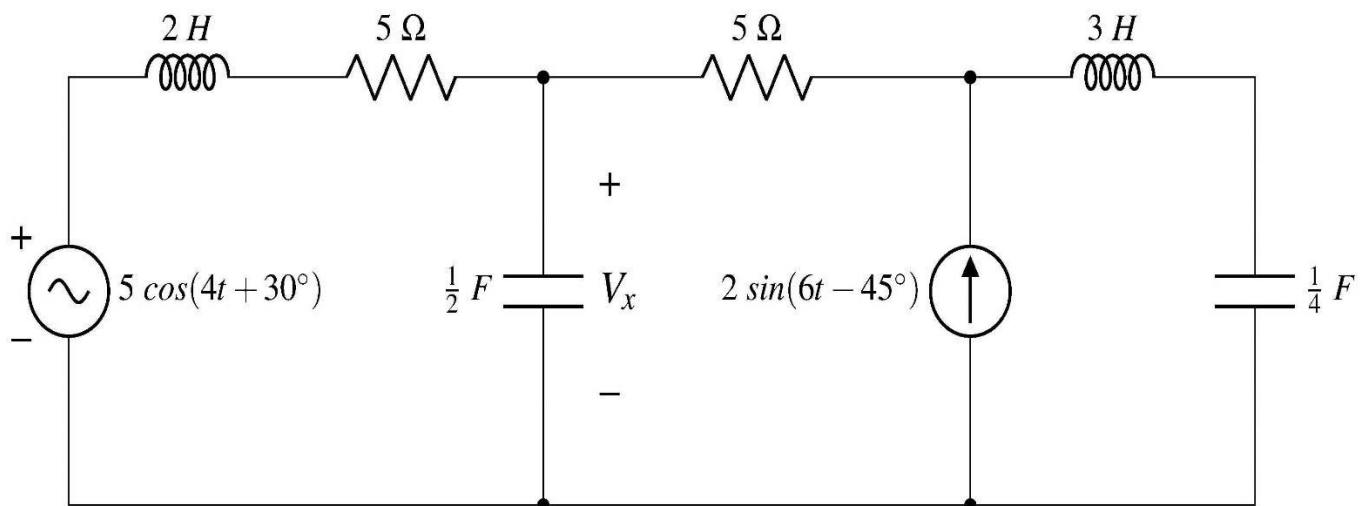

- Determine** the voltage v_x . [Hint: Use Superposition principle]
(15 marks) [CO4, CO6]

$$v_x(t) = 0.29 \cos(4t - 115.17^\circ) + 0.67 \sin(6t - 118.01^\circ) \text{ (V)}$$