

# Department of Computer Science and Engineering (CSE) BRAC University

Fall 2023

CSE250 - Circuits and Electronics

## SOURCE TRANSFORMATION




*KANIZ FATEMA SUPTI, ADJUNCT LECTURER  
Department of Computer Science and Engineering (CSE)  
BRAC University*

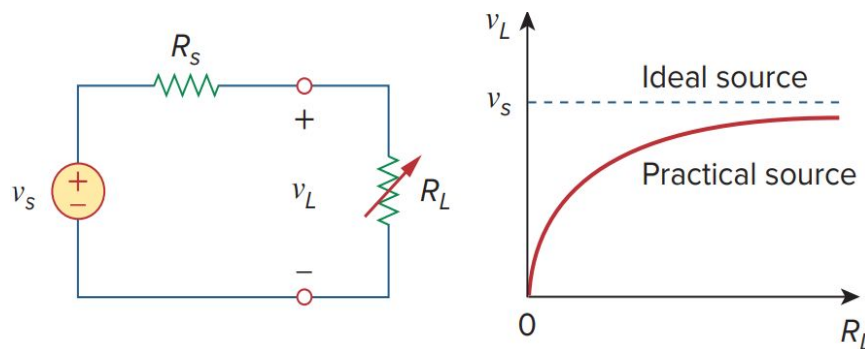
# Ideal and non-ideal sources

- An *ideal voltage source* provides a constant voltage irrespective of the current drawn by the load, while an *ideal current source* supplies a constant current regardless of the load voltage.
- Practical* voltage and current sources are not ideal, due to their *internal resistances* or *source resistances*  $R_s$  and  $R_p$ . They become ideal as  $R_s \rightarrow 0$  and  $R_p \rightarrow \infty$ .


$$v_L = \frac{R_L}{R_s + R_L} v_s, \text{ if } R_s \ll R_L \text{ or } R_L = \infty, v_L \rightarrow v_s$$


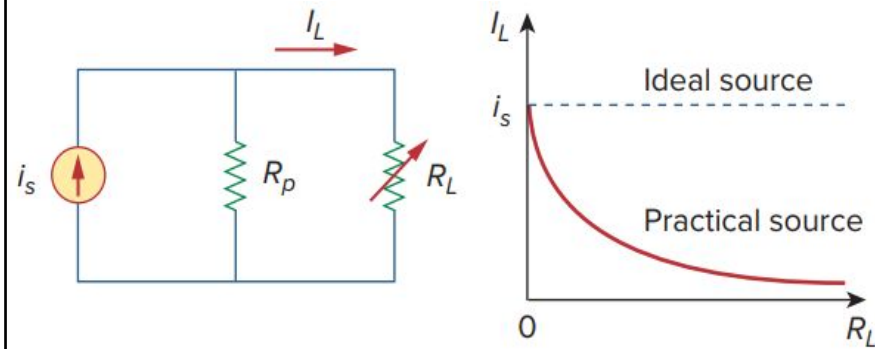
$$i_L = \frac{R_p}{R_p + R_L} i_s, \text{ if } R_p \gg R_L \text{ or } R_p \rightarrow \infty, i_L \rightarrow i_s$$




# Course Outline: broad themes

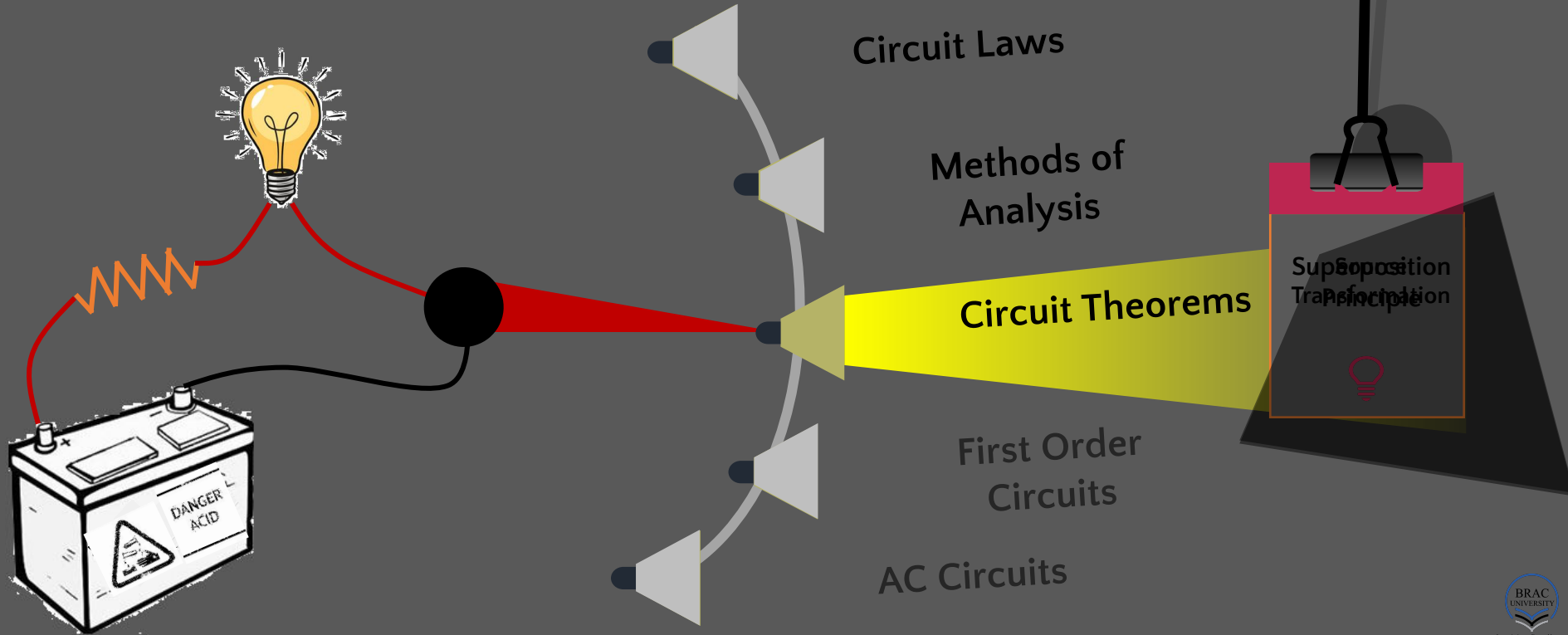
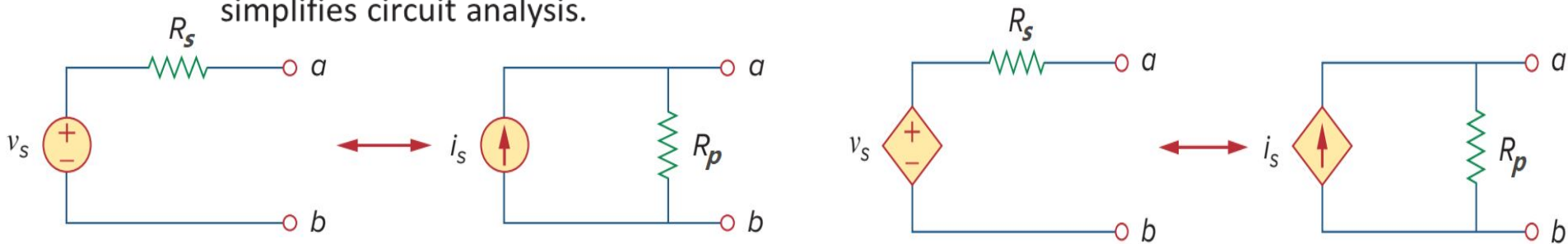
# Source Transformation

- A **source transformation** is the process of replacing a voltage source  $v_s$  in series with a resistor  $R$  by a current source  $i_p$  in parallel with a resistor  $R$ , or vice versa.
- The transformation does not affect the remaining part of the circuit but greatly simplifies circuit analysis.




- Note that the arrow of the current source is directed toward the positive terminal of the voltage source.
- The source transformation is not possible when  $R = 0$  and  $R = \infty$  (see next slide), which are the cases with an ideal voltage and current source respectively. However, for a practical, nonideal voltage source,  $R \neq 0$ , and for a practical, nonideal current source,  $R \neq \infty$ .

# V in series with a R

- We recall that *an equivalent circuit is one whose  $I - V$  characteristics are identical with the original circuit*. Let's see what conditions make the two circuits to have the same  $I - V$  relations at terminals  $a - b$ .
- Let's say we have a configuration of a voltage source ( $v_s$ ) in series with a resistor ( $R_s$ ) between terminals  $a$  and  $b$ . To determine the configuration's  $I - V$  characteristics, if applying a voltage  $V$  gives rise to a current  $I$ , we can write,

$$V = v_s + IR_s$$
$$\Rightarrow I = \frac{1}{R_s}V - \frac{v_s}{R_s}$$

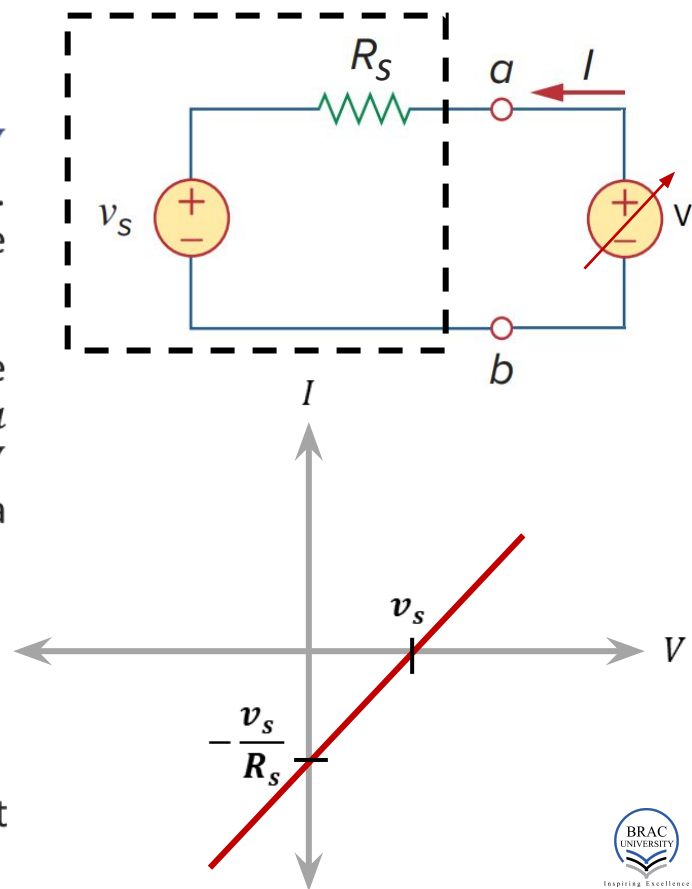- The equation results in a linear  $I$  vs  $V$  plot that intersects the axes at  $v_s$  and  $-\frac{v_s}{R_s}$ .



# I in parallel with a R


- For the other configuration: a current source ( $i_p$ ) in parallel with a resistor ( $R_p$ ) between terminals  $a$  and  $b$ , if applying a voltage  $V$  gives rise to a current  $I$ , using KCL the current through the resistor is,

$$I + i_p$$

- So, the voltage across the resistor can be written as,

$$(I + i_p) R_p = V$$
$$\Rightarrow I = \frac{1}{R_p} V - i_p$$

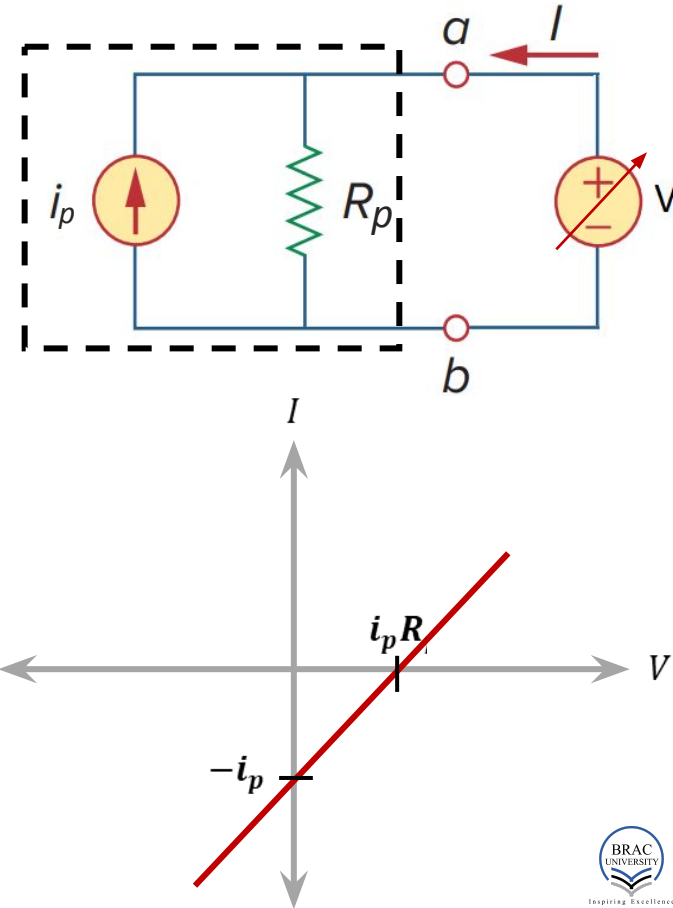- The equation results in a linear  $I$  vs  $V$  plot that intersects the axes at  $i_p R_p$  and  $-i_p$ .





# Conditions for transformation

- The two configurations will be equivalent to each other if their  $I - V$  characteristics are similar. It can be said by looking at the two plots, they will indeed be similar if the intersecting points are same, that is, if  $v_s = i_p R_p$  and  $-\frac{v_s}{R_s} = -i_p$ . This requires  $R_s = R_p = R$ . Both the equations result in an ohmic relation,


$$v_s = i_p R \text{ or } i_p = \frac{v_s}{R}$$

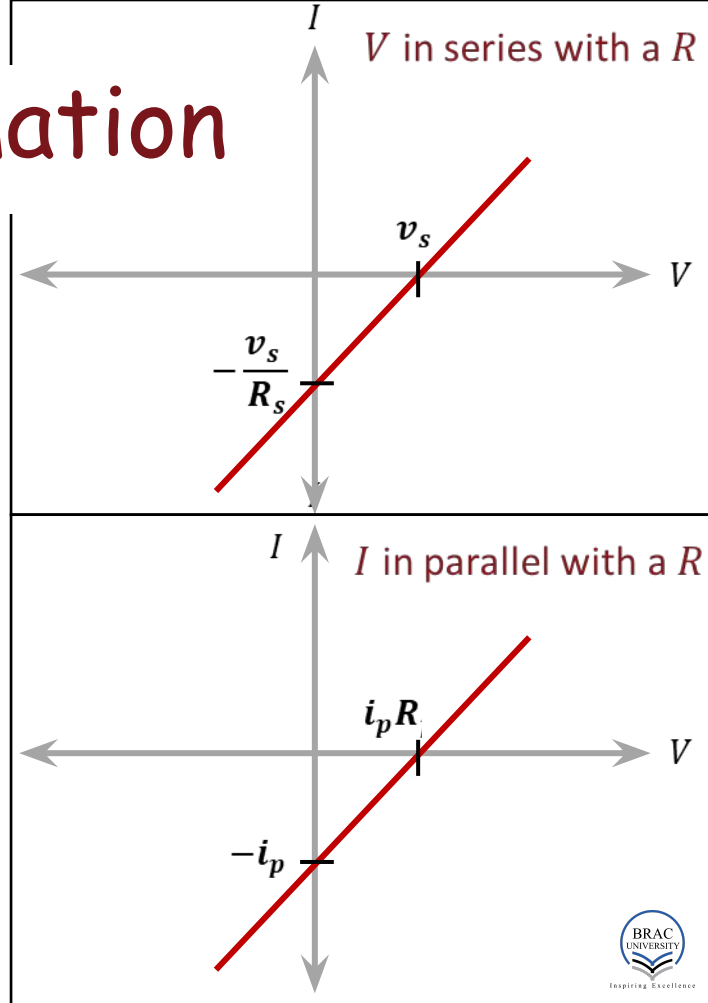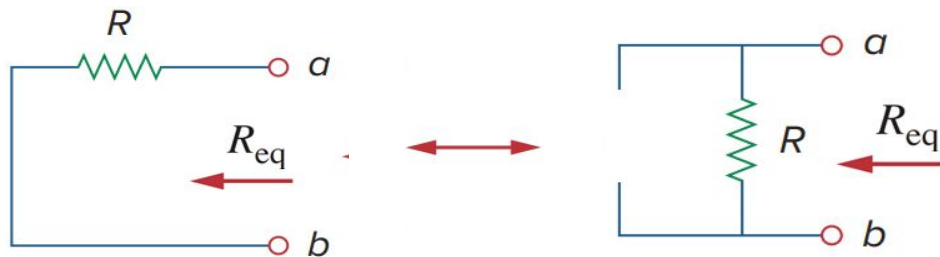- So, if the sources are turned off, the equivalent resistance at terminals  $a - b$  in both circuits is  $R$ .



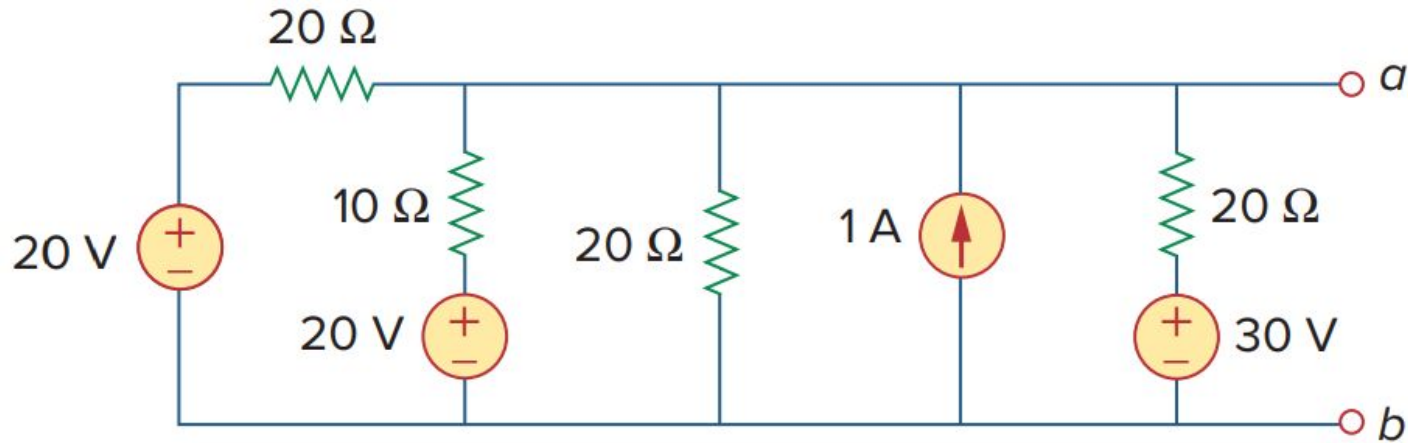
# Example 1

- Use source transformation to reduce the circuit between terminals  $a$  and  $b$  shown to a single voltage source in series with a single resistor.






# Example 1: transforming sources

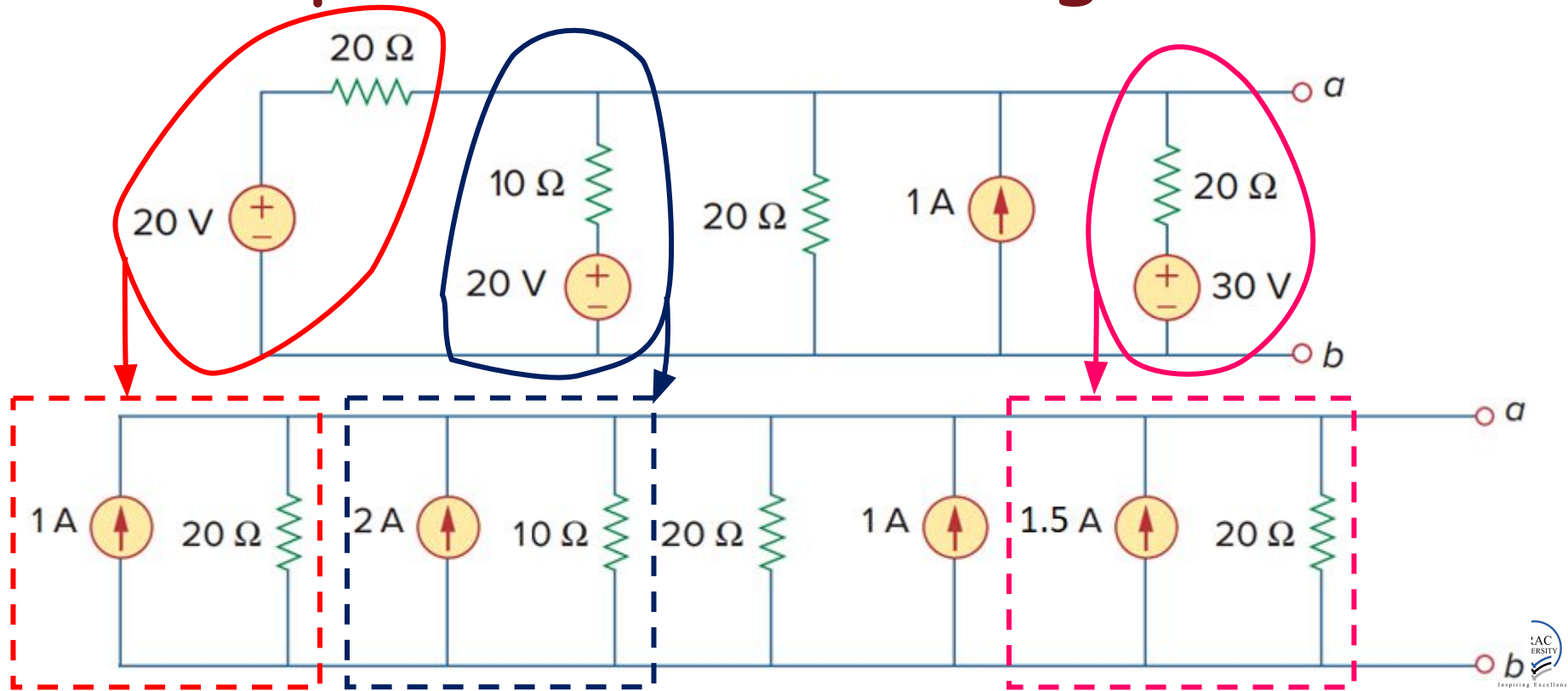


# Example 1 (contd ... 2)

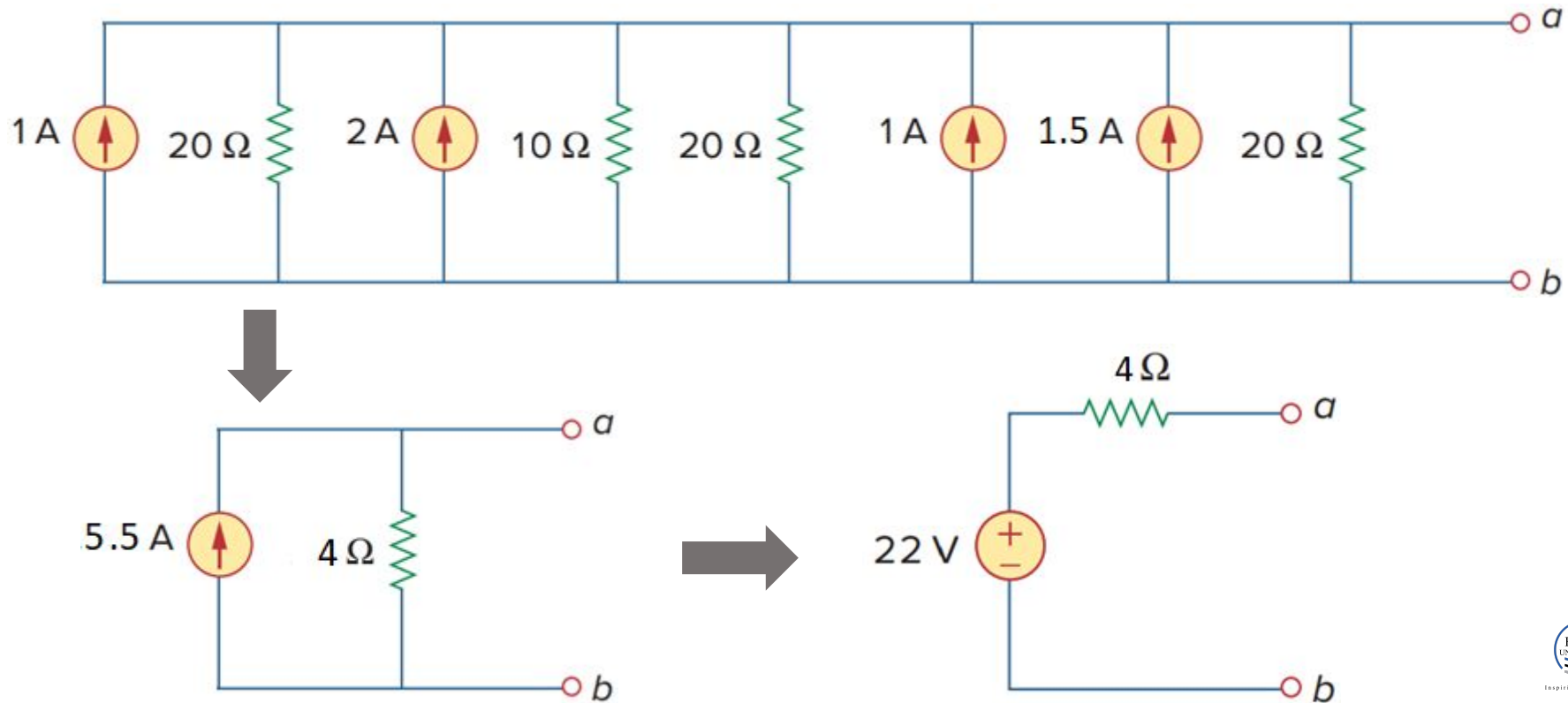
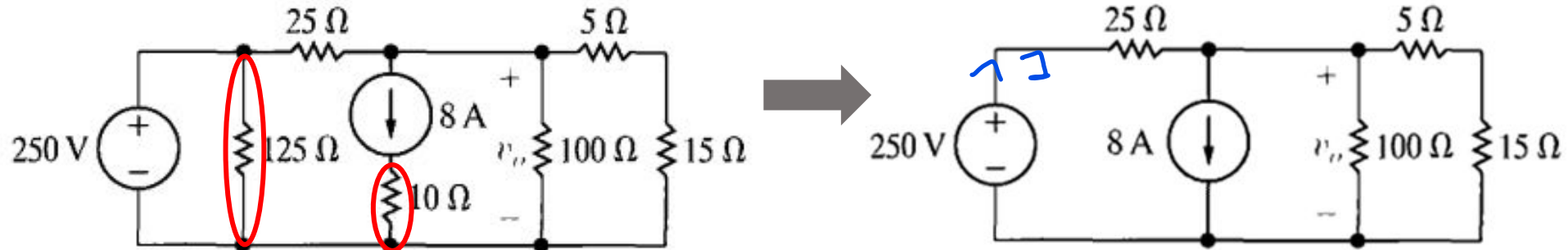
# Problem 1


- Use Source Transformation to find the voltage  $v_0$ . Find the power developed by the 250 V source and 8 A source.




A resistor in series with a current source is redundant, as is a resistor in parallel with a voltage source. We can remove them; this will have no effect on the circuit except for the sources. Opening a resistor parallel to a voltage source will **reduce** the current supplied by the source. Similarly, shorting a resistor in series with a current source **increases** the voltage across the current source. We have to keep in mind those facts while calculating parameters for the sources.

Ans:  $v_0 = 20 \text{ V}$ ;  $P_{250\text{V}} = -2.8 \text{ kW}$ ;  $P_{8\text{A}} = +480 \text{ W}$

Step 1:

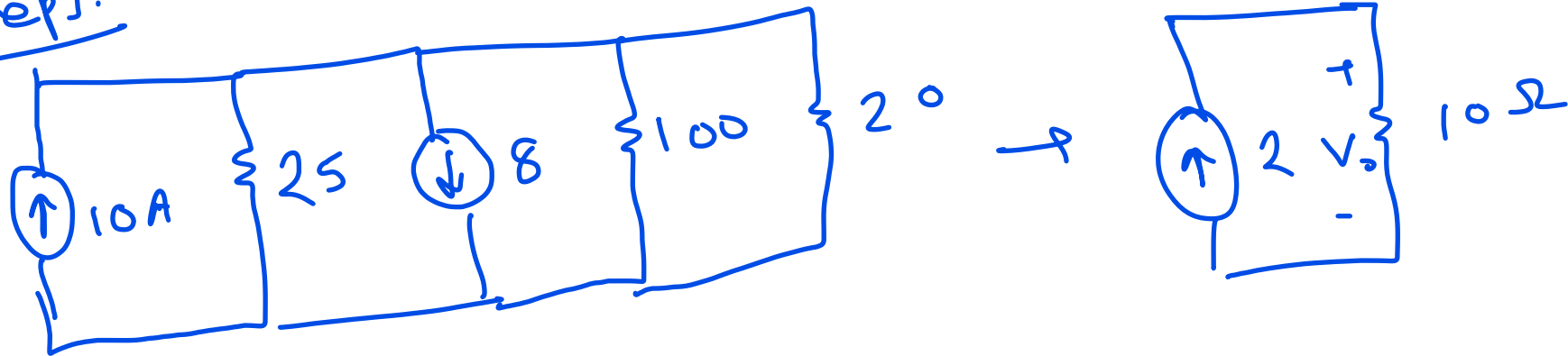

So  $V_0 = 20V$

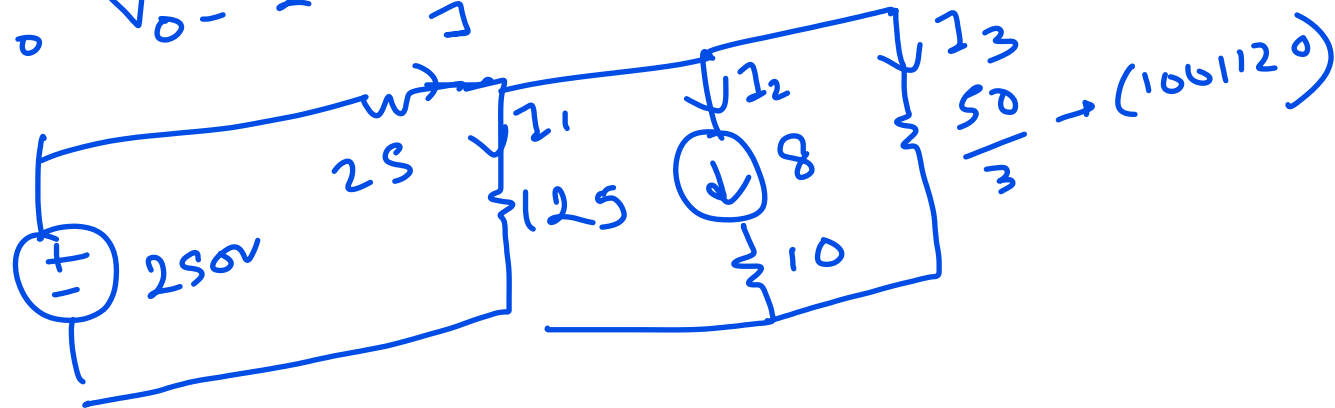


$$I = I_1 + I_2 + I_3$$

$$= \frac{250}{125} + 8 + \frac{V_0}{25/3} = 11.2 \text{ A}$$

$$\text{So, } P_{250} = -11.2 \times 250 \\ = -2.8 \text{ kW}$$


$$V_{8A} = -20 + 8 \times 10 = 60$$
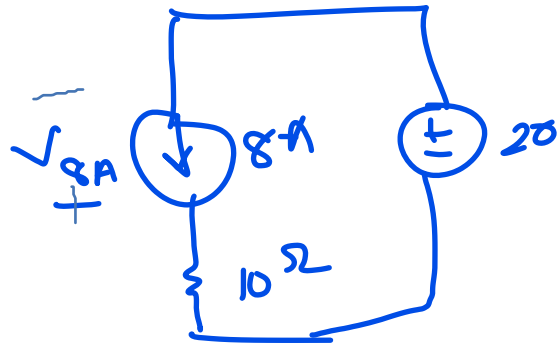
$$P_{8A} = - (60 \times 8) = -480 \text{ W}$$



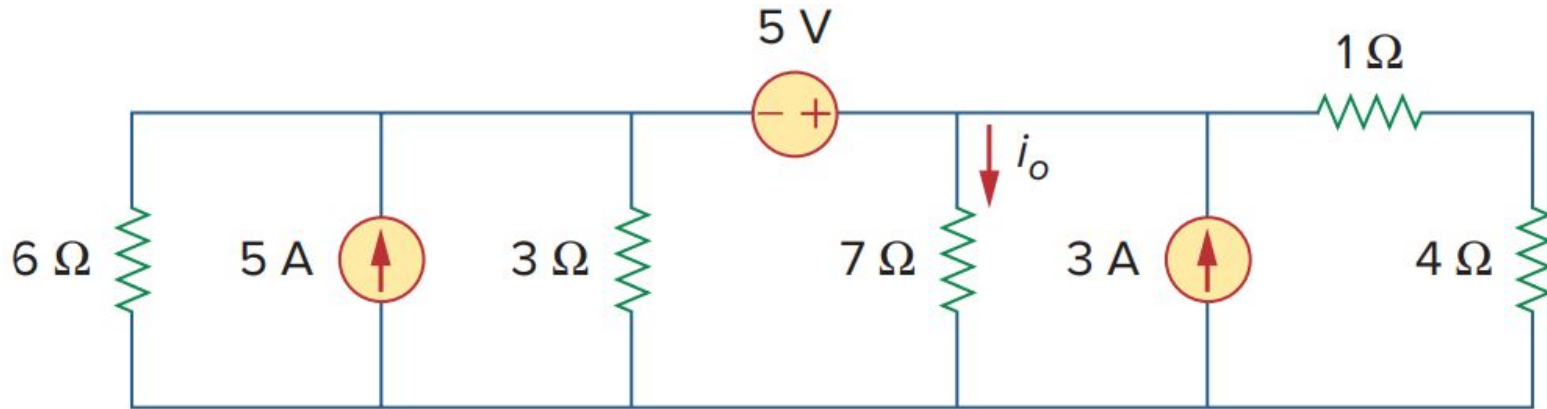
# Problem 2

- Find  $i_o$  in the circuit using Source Transformation.




Ans:  $i_o = 1.78 \text{ A}$



Step 1

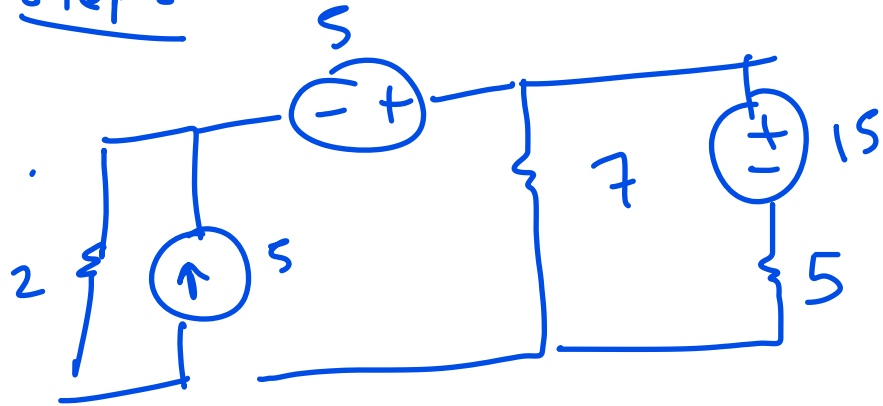


Step 2'

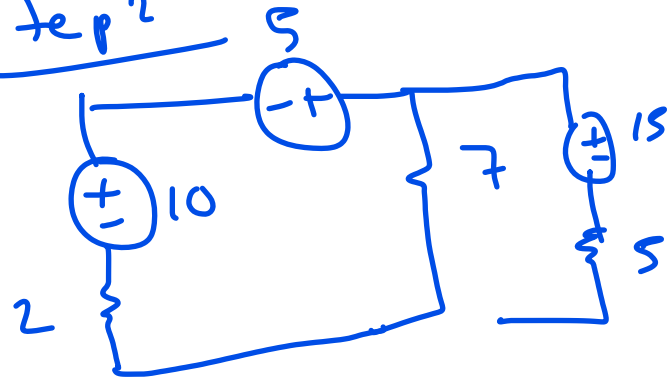

Step 3'

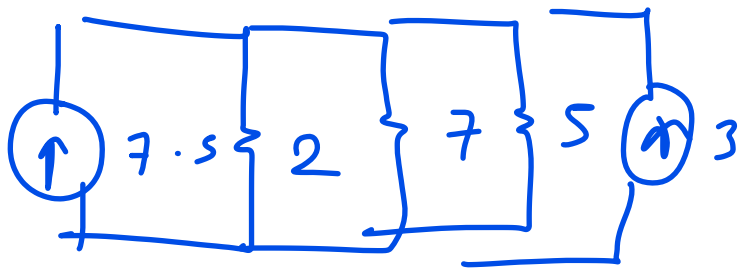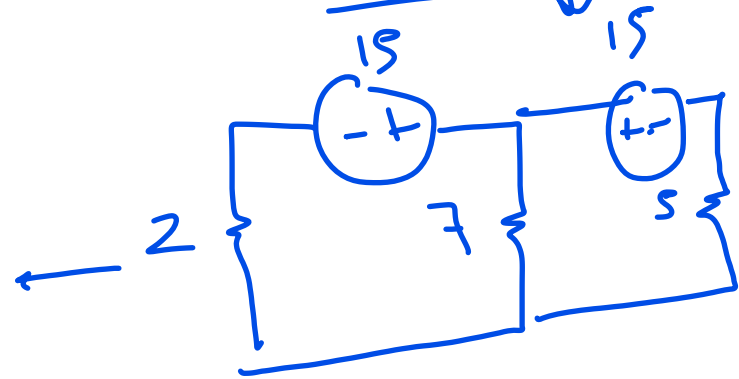

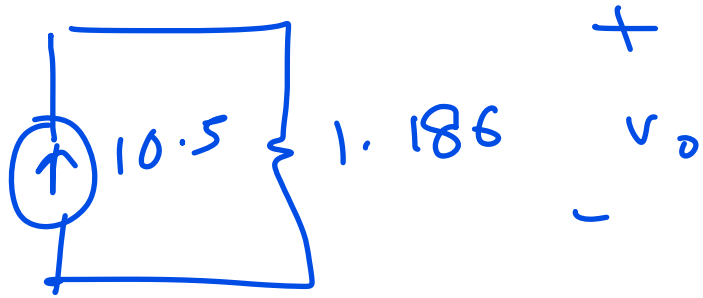


$$V_o = 1.186 \times 10.5$$

$$S_o \quad I_{7\Omega} = \frac{V_o}{7} = 1.78A$$



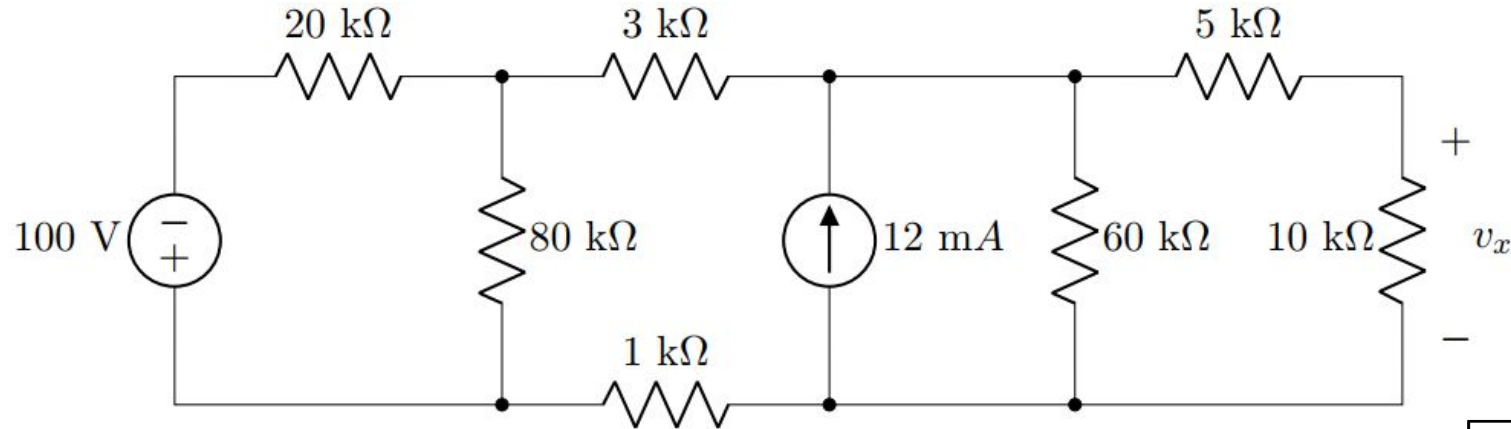
# Problem 3

- Determine the voltage  $v_x$  across the  $10\text{ k}\Omega$  resistor by performing a succession of appropriate Source Transformations.




Ans:  $v_x = 40\text{ V}$


Fall'22

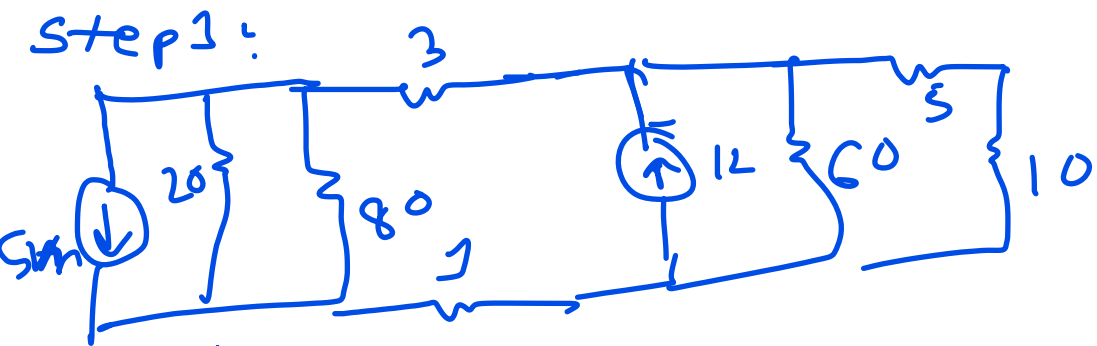


↓ step 2

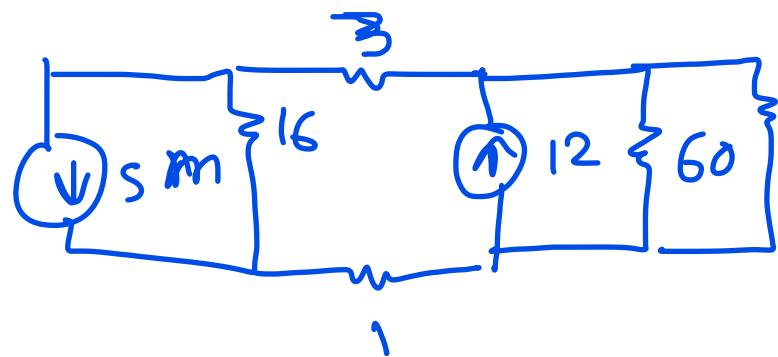


→  
Step 3

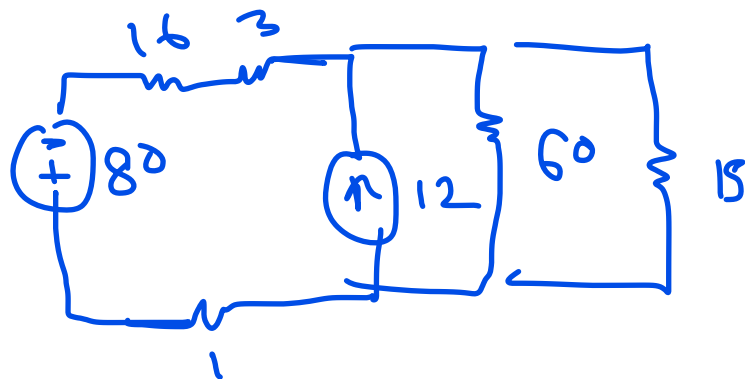


↑ Step 4

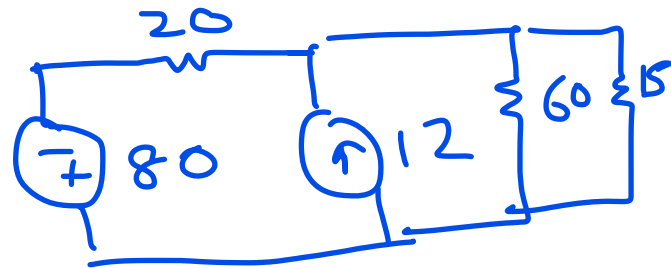

Step 5:

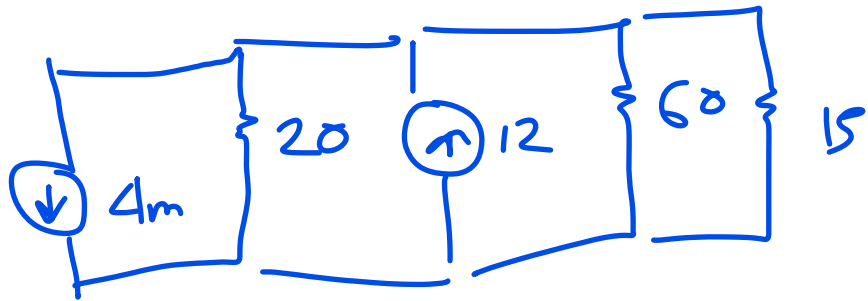

Step 6:

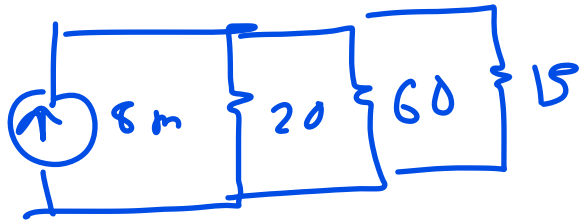


Step 7:

$$V_n = 10 \times I_{15}$$
$$= 10 \times \frac{15^{-1} \times 8}{15^{-1} + 60^{-1} + 20^{-1}}$$

$$= 40V$$

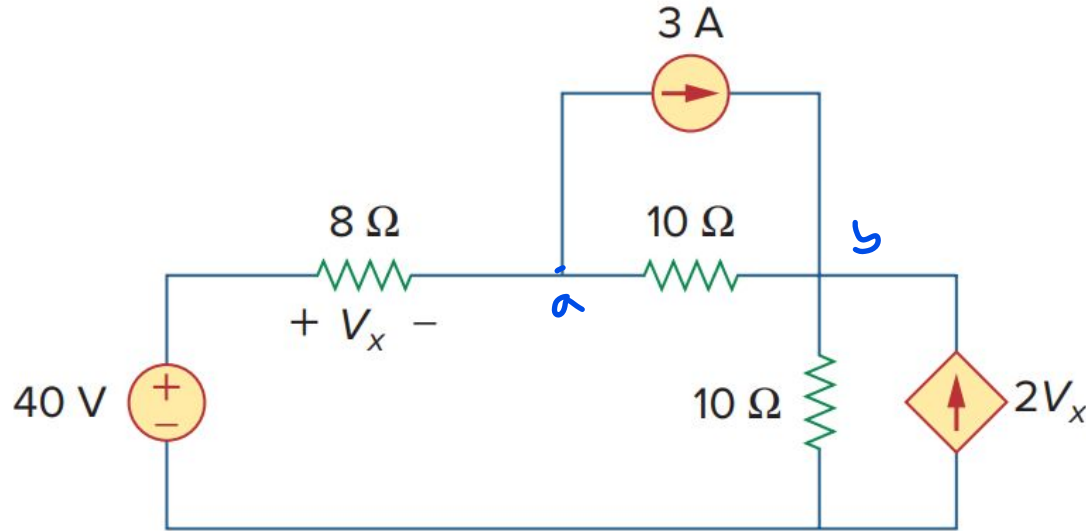
# Problem 4

- Use Source Transformation to find  $V_x$ .



Ans:  $V_x = 2.98 \text{ V}$

Step 1: 8

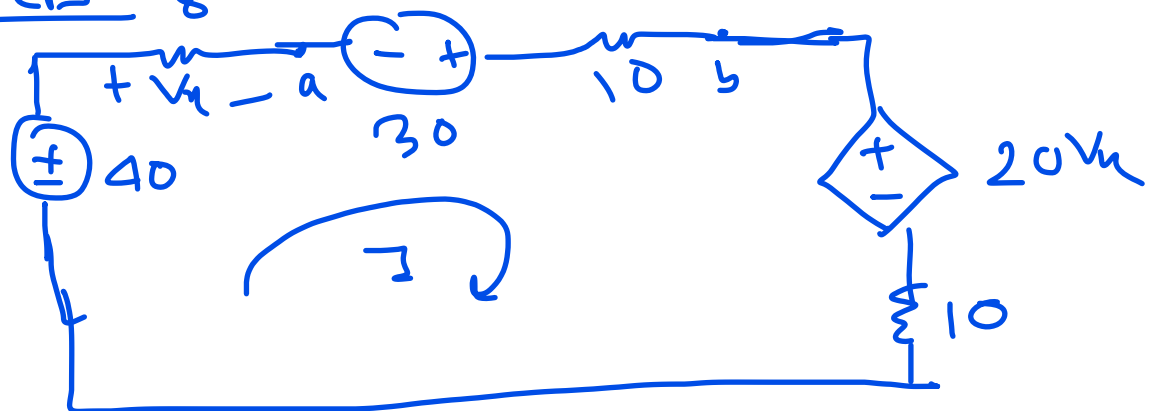

$$1887 = 70$$

$$I = \frac{70}{188}$$

$$\therefore V_x = 2.98$$

Step 2:

$$V_x = 87$$


$$-40 + 87 - 30 + 10I + 20V_x + 10I = 0$$

$$-40 + 87 - 30 + 10I + 160I + 10I = 0$$



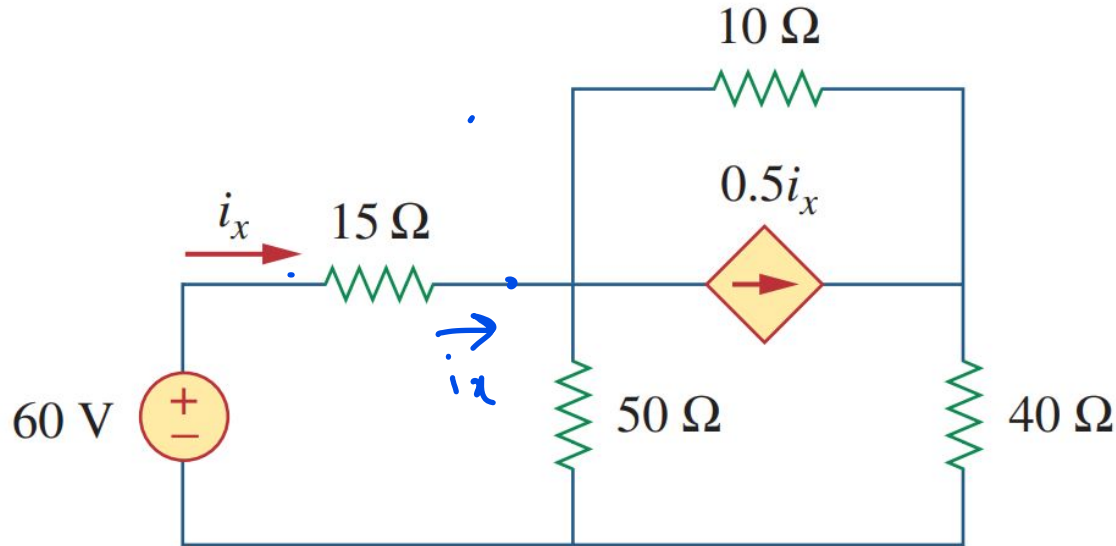
# Problem 5

- Use Source Transformation to find  $i_x$  in the following circuit.




Ans:  $i_x = 1.6\text{ A}$


Step 1:

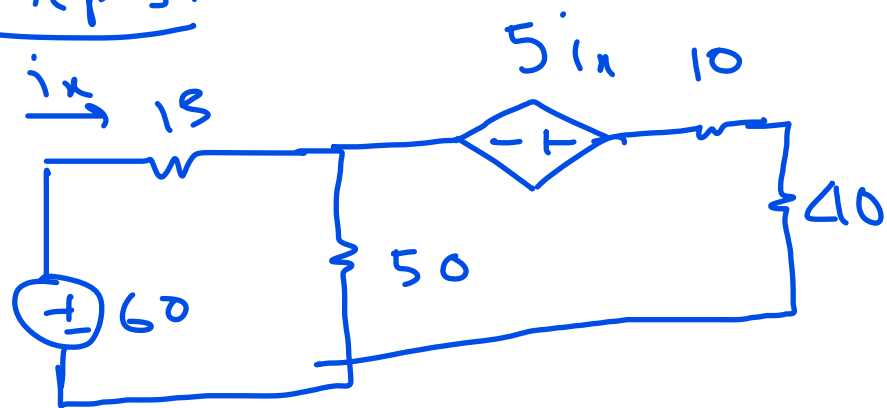


Step 2:

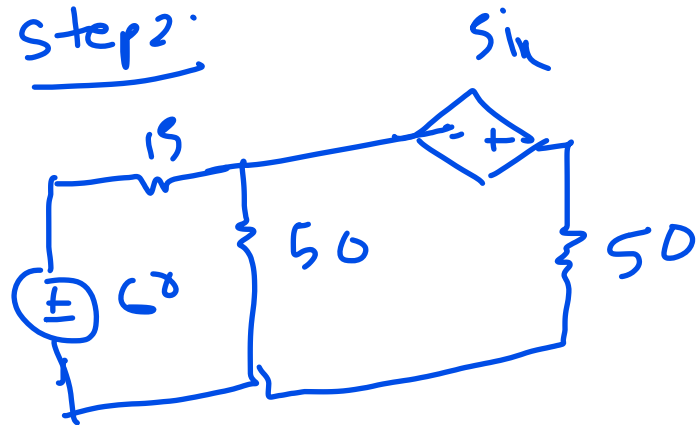

Step 3:

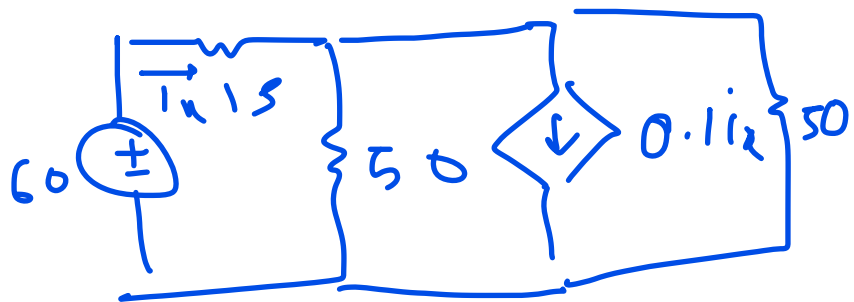


Step 4:

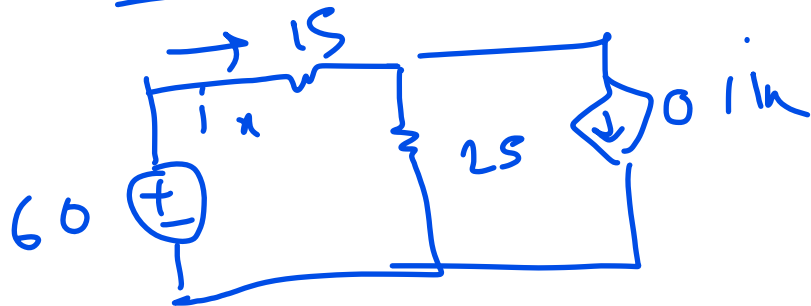



Step 5:

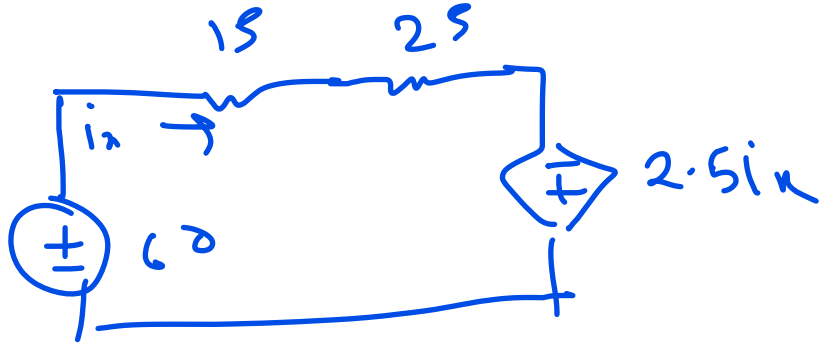


$$\text{So, } -60 + 15i_x + 25i_x - 2.5i_x = 0$$

$$i_x = 1.6 \text{ A}$$

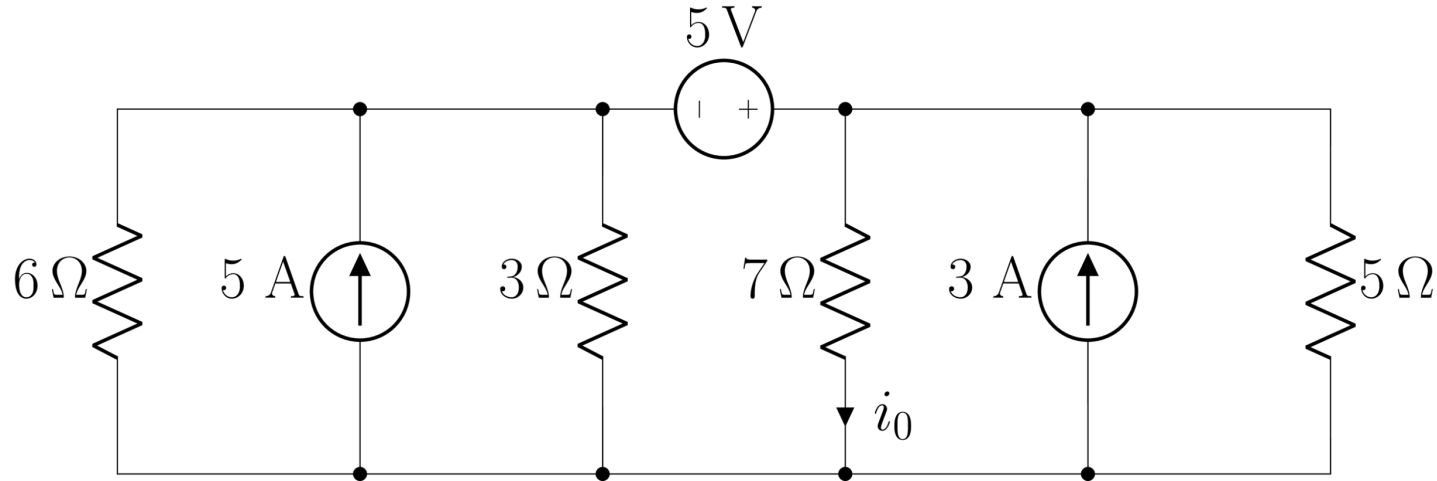
# Problem 6

- Reduce the circuit to a single loop using Source Transformation. Then determine  $i_0$ .




**Ans:  $i_0 = 1.78 \text{ A}$**


Step 1: 3||6  $\rightarrow$  5

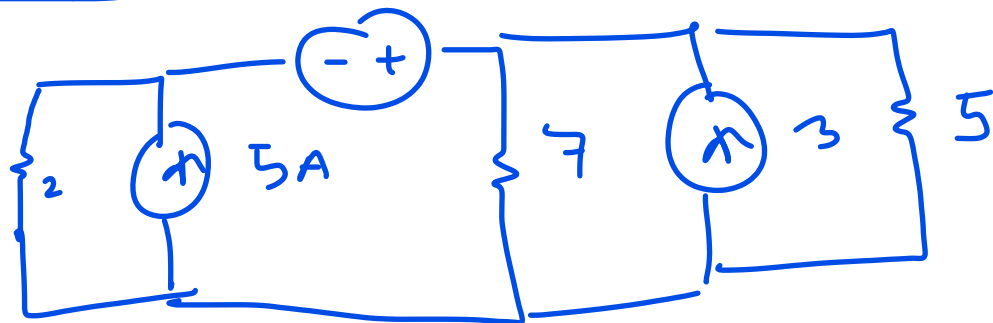


Step 2:

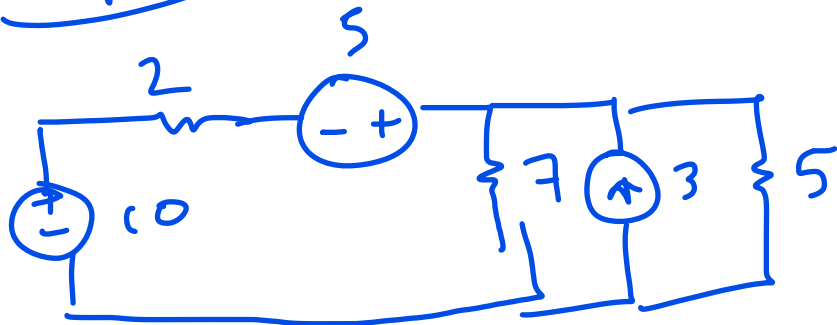


Step 3:  $10V + 5V = 15$

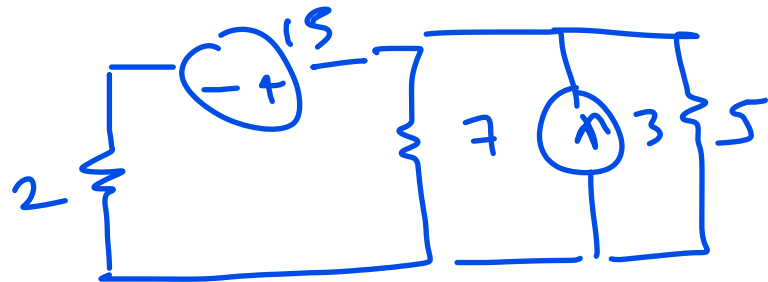

Step 4:

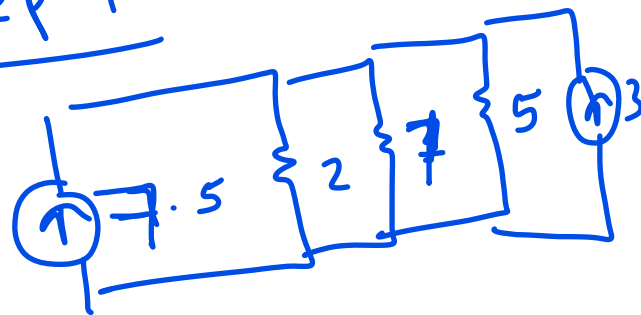


Step 5:

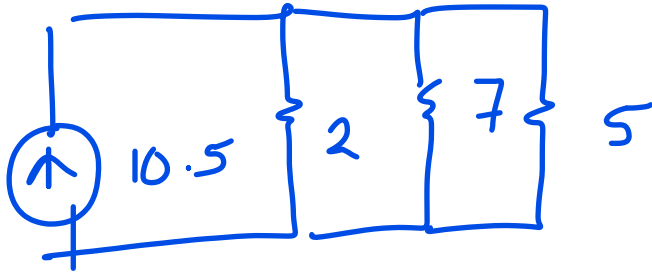

$$i_o = \frac{7^{-1}}{2^{-1} + 5^{-1} + 7^{-1}} \times 10.5 = 1.78 \text{ A}$$
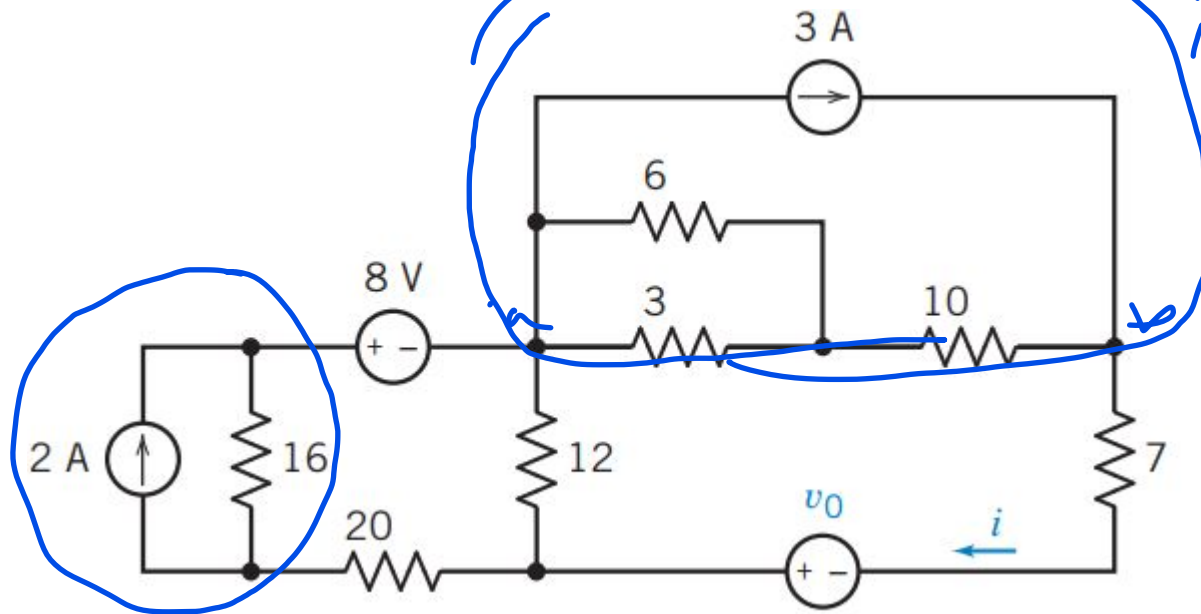
# Problem 7


- Reduce the circuit to a single loop. If  $i = 2.5$  A, determine  $v_0$ .




in a, b node  
 $(6||3) + 10 = 12\Omega$

Ans:  $v_0 = 28$  V


Step 1:

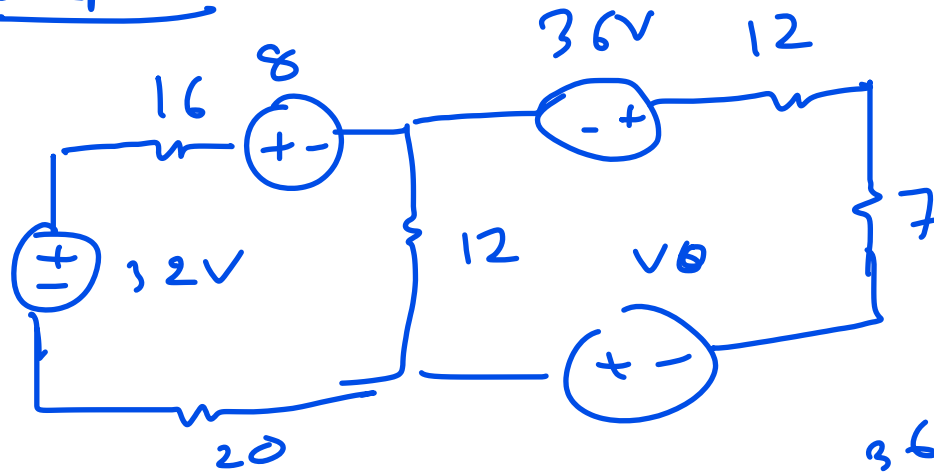


Step 2:

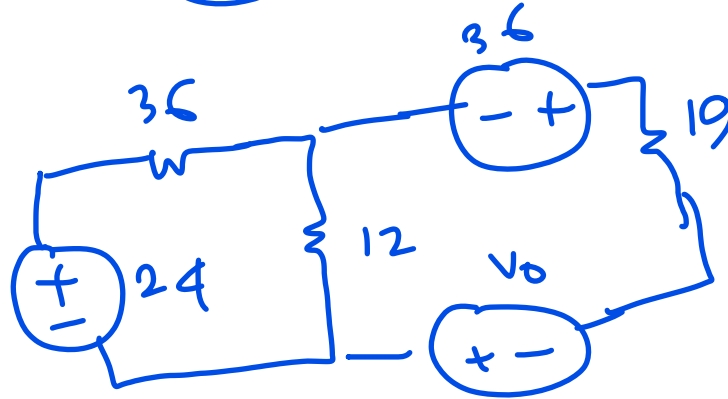

Step 3:

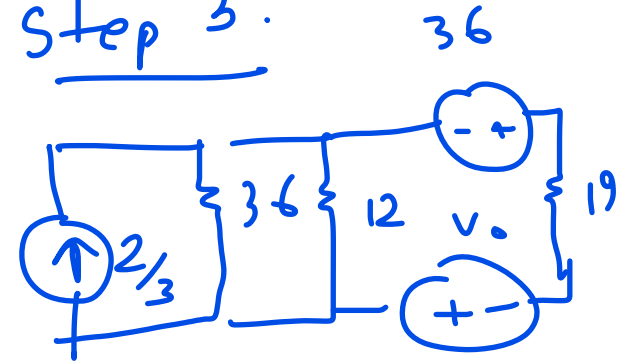

Step 4. (30/12)

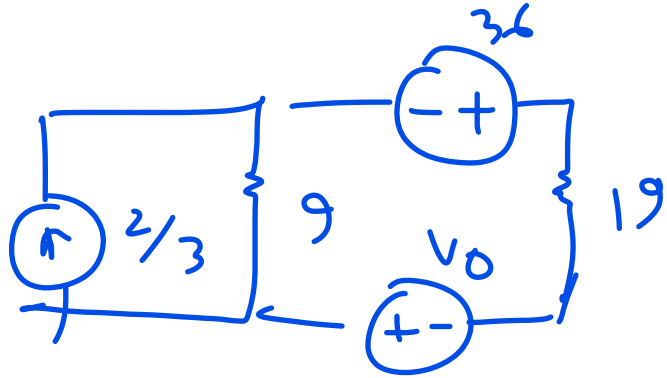


Step 6.

$$-6 + 9i - 36 + 19i - V_o = 0$$

$$I = 2.5A$$


$$\text{So, } V_o = 28V$$

Step 5.

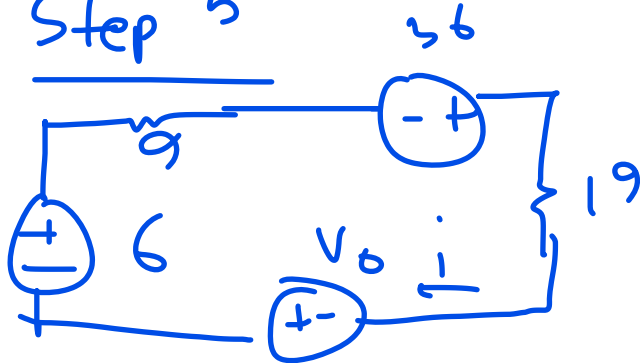
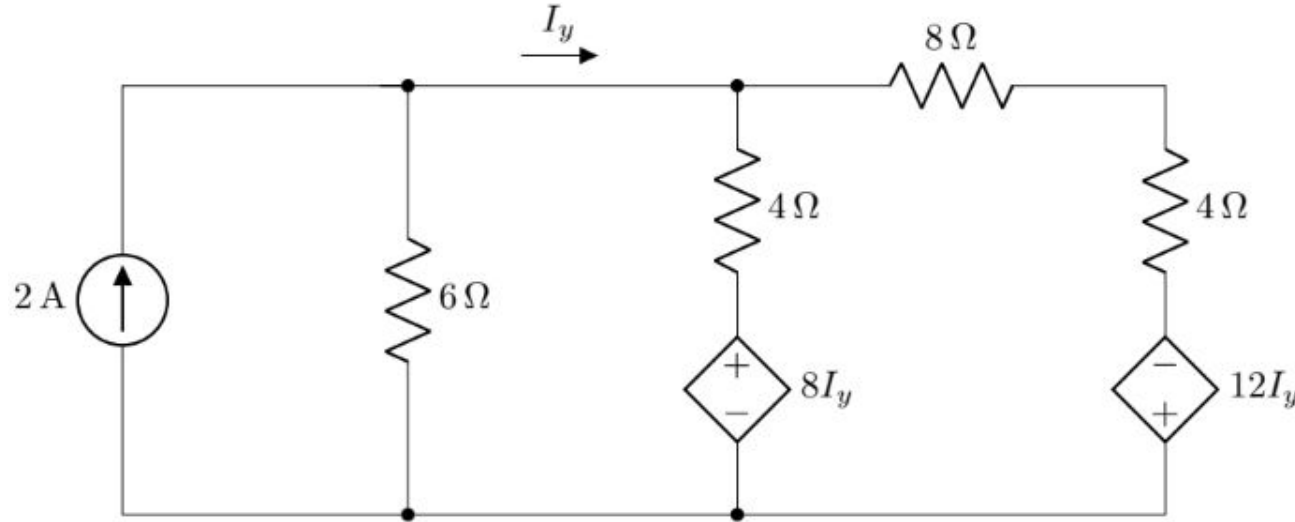
# Problem 8


- Reduce the circuit to a single loop using Source Transformation. Then determine  $I_y$ .




Ans:  $I_y = 1\text{ A}$



Step 1

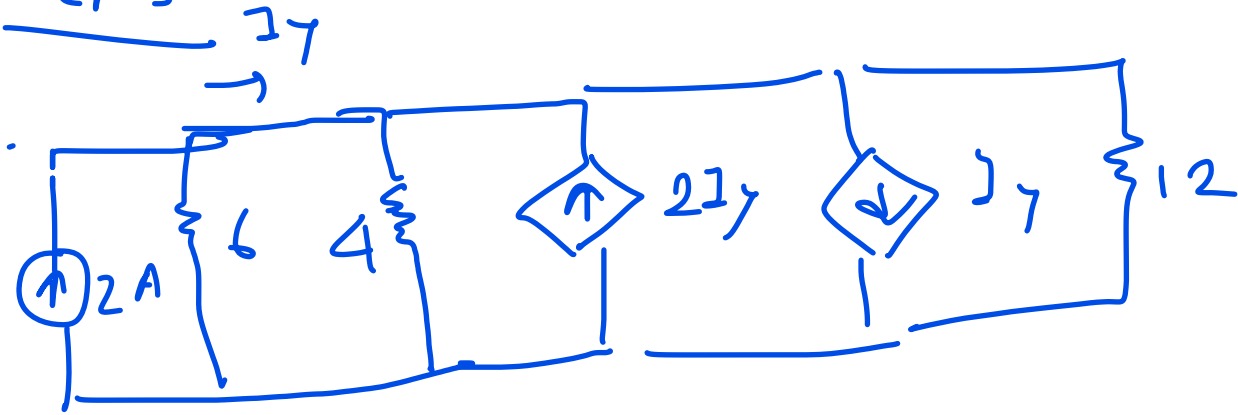

Step 2:

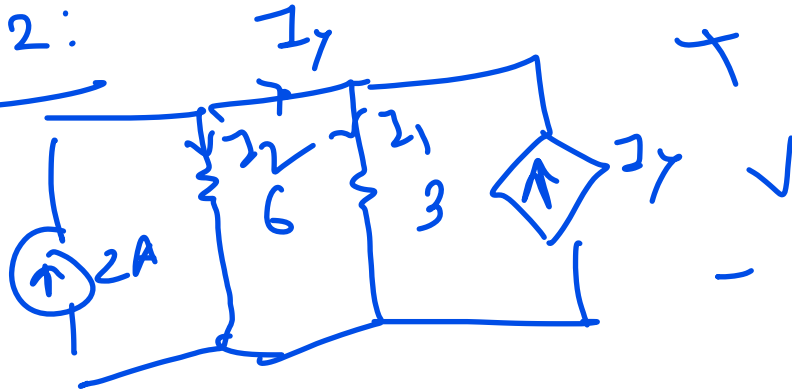

Step 3:

$$I_1 + I_2 = I_1$$

$$2I_1 = \frac{V}{3}$$

$$V = 6I_1$$

So,  $2 = I_1 + I_2$


$$2 = \frac{V}{6} + I_2$$

$$2 = \frac{6I_1}{6} + I_2$$

$$I_2 = 1 \text{ A}$$

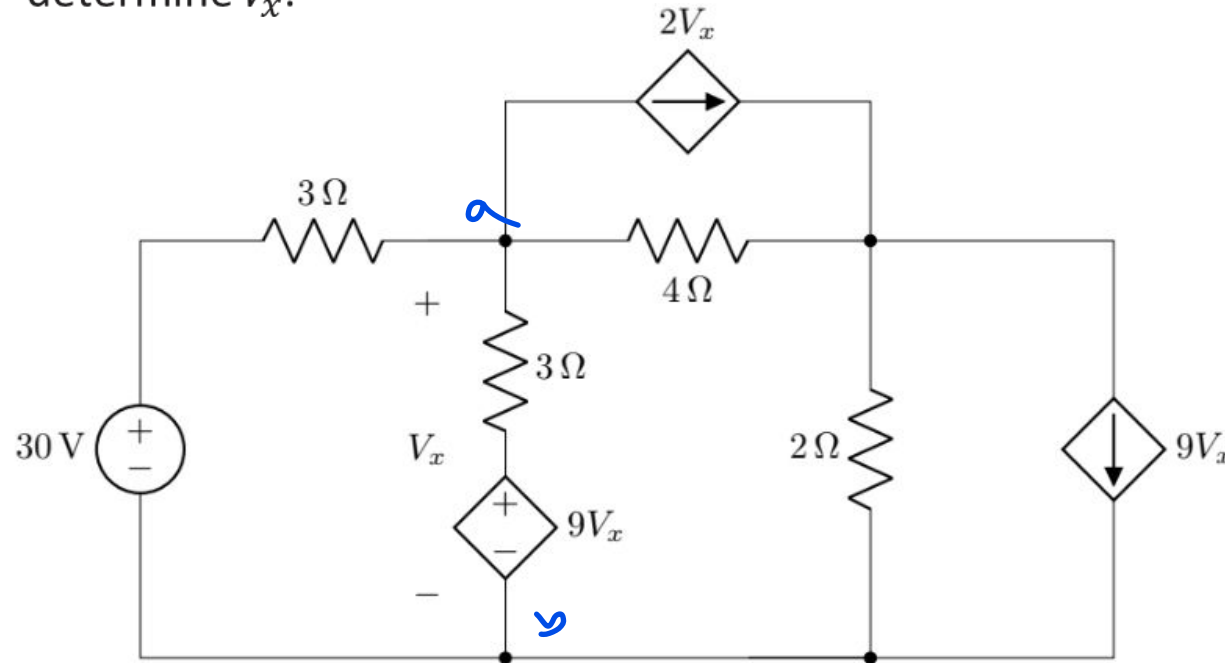
# Problem 9

- Reduce the circuit to a single loop using Source Transformation. Then determine  $V_x$ .




**Ans:  $V_x = 4.62 \text{ V}$**


Step 1:

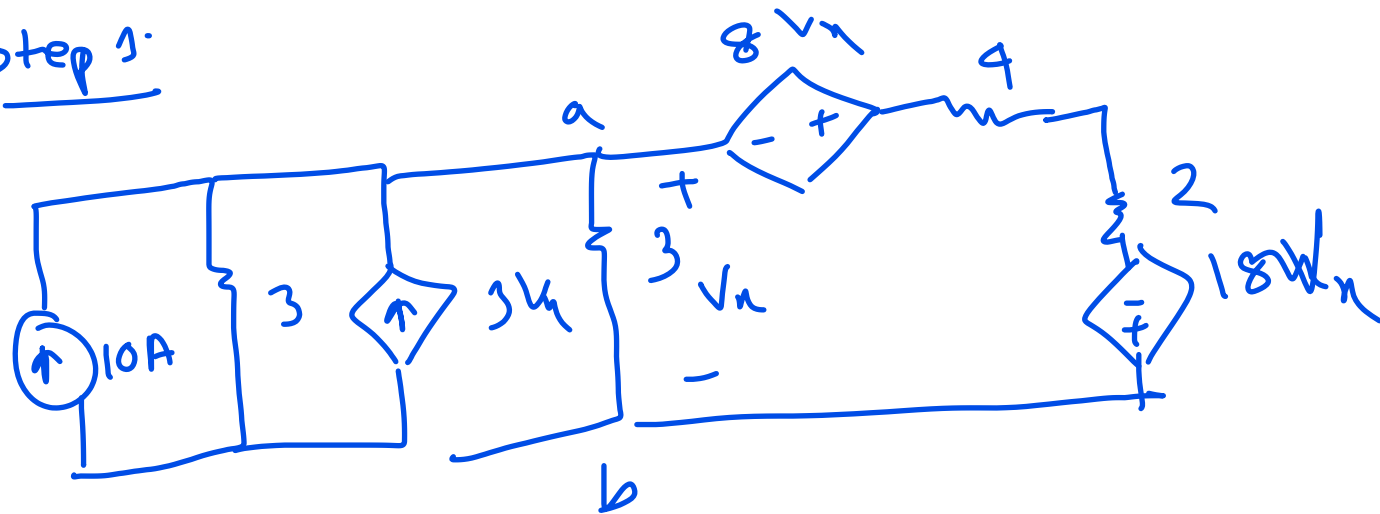


Step 2:

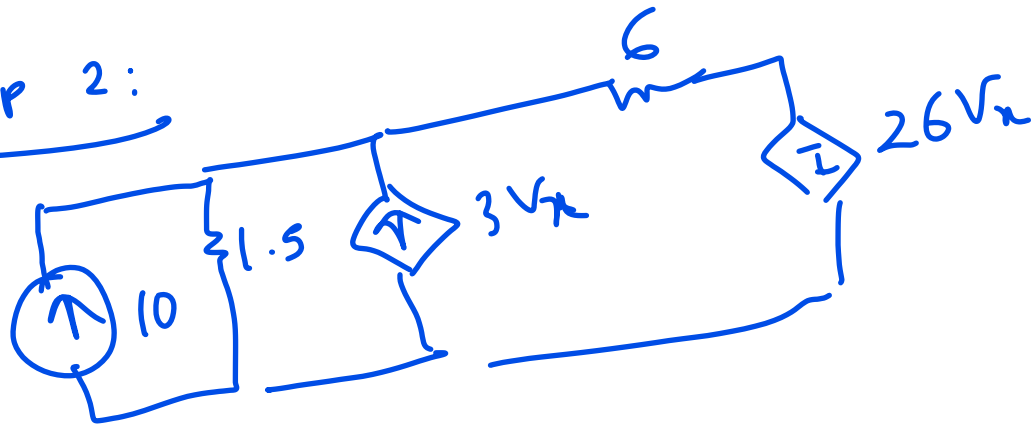

Step 3:

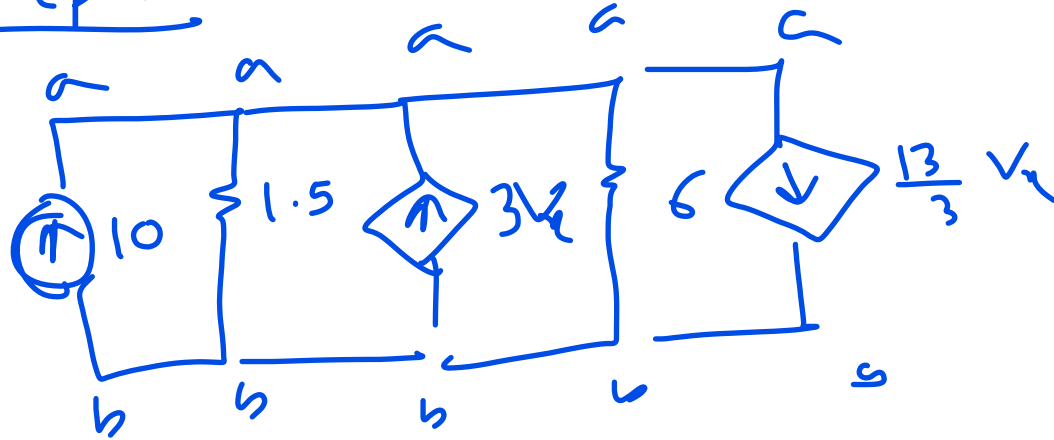

Step 4:

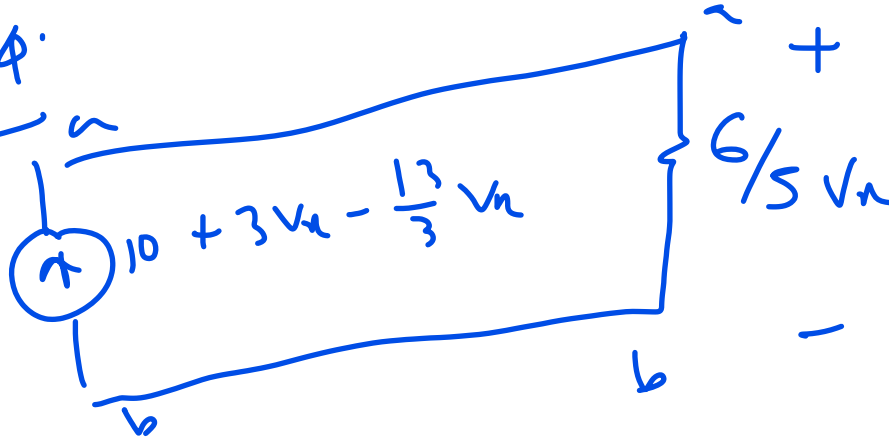

$$\text{So, } V_{ab} = V_x$$

$$V_x = \frac{6}{5} \left( 10 - \frac{4}{3}V_x \right)$$

$$V_x = 12 - \frac{8}{5}V_x$$

$$\frac{13}{5}V_x = 12$$

$$V_x = 4.62 \text{ V}$$

# Practice Problems

- Additional recommended practice problems: [here](#)
- Other suggested problems from the textbook: [here](#)

# Thank you for your attention

# Course Outline: broad themes

