
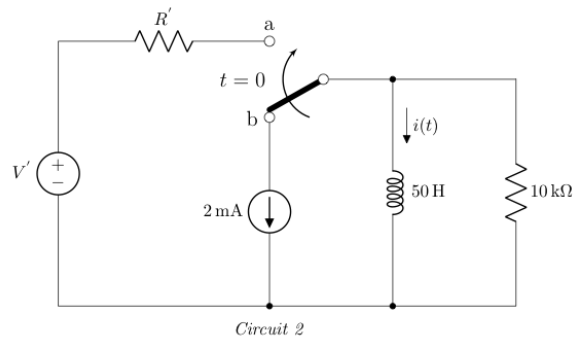



■ Question 1 of 3 [CO2, CO3] [20 marks]




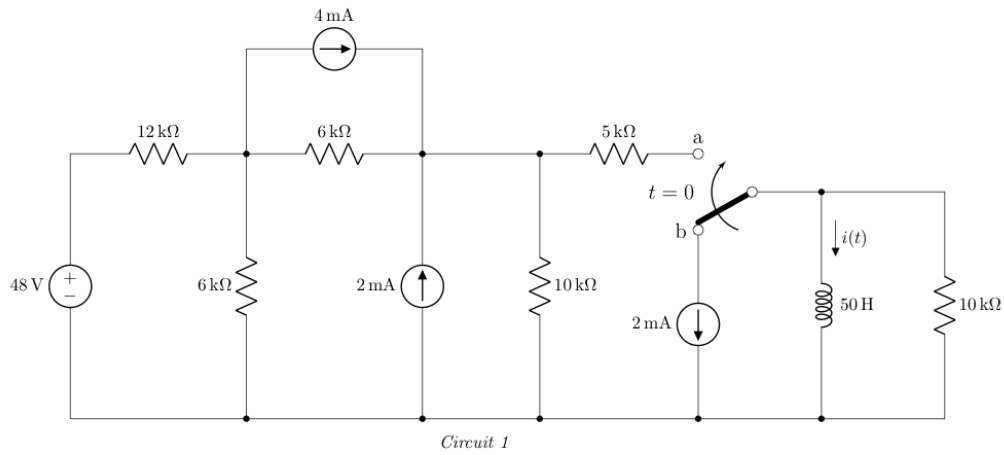
Consider the the following circuits which are equivalent to each other.







(a) [7 marks] Derive Circuit 2 from Circuit 1. What are the values of V' and R' ?

Ans:

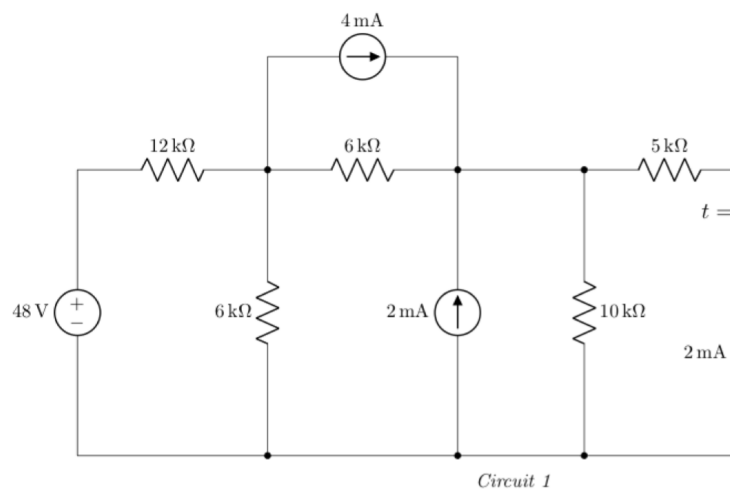

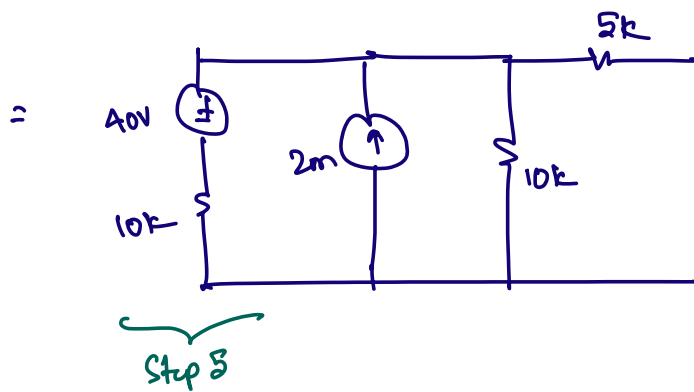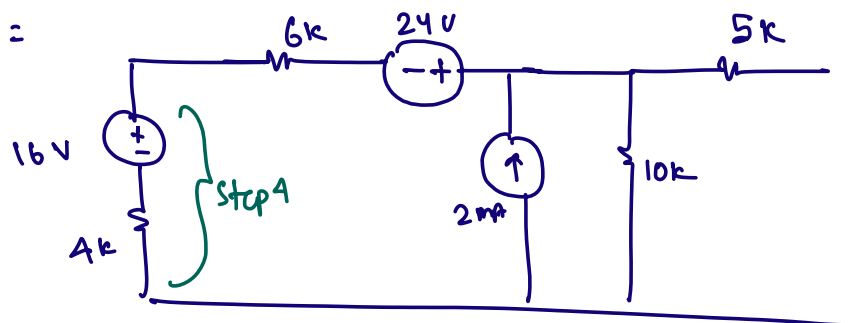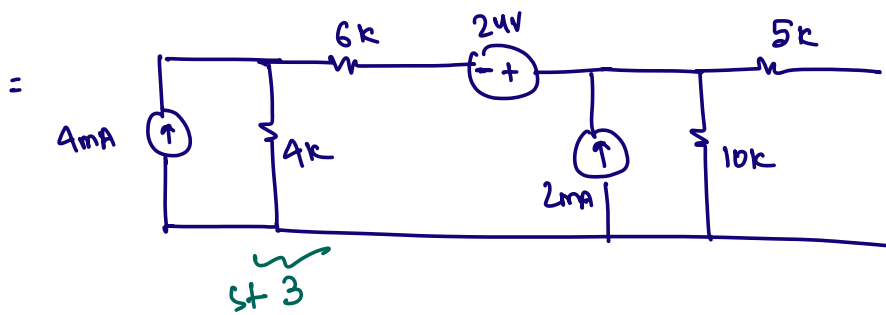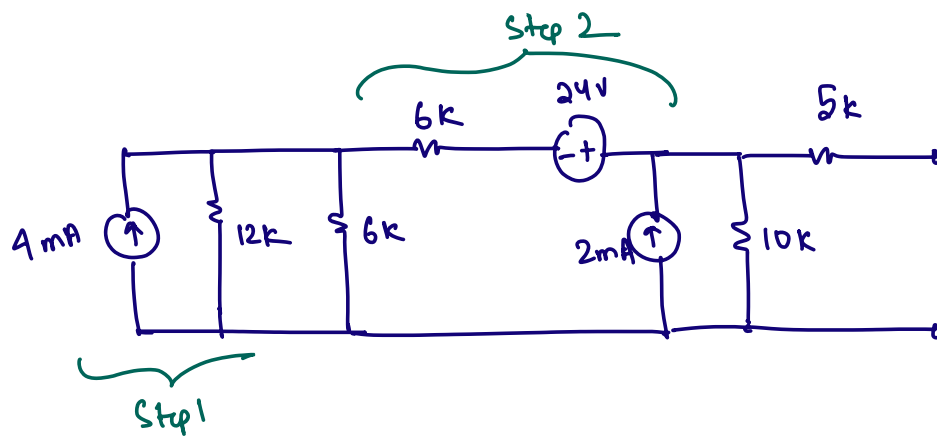


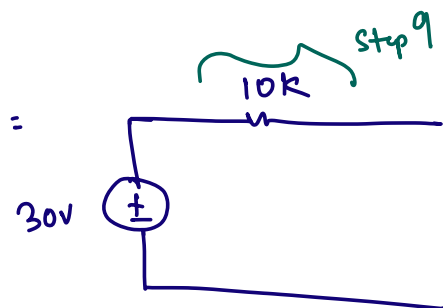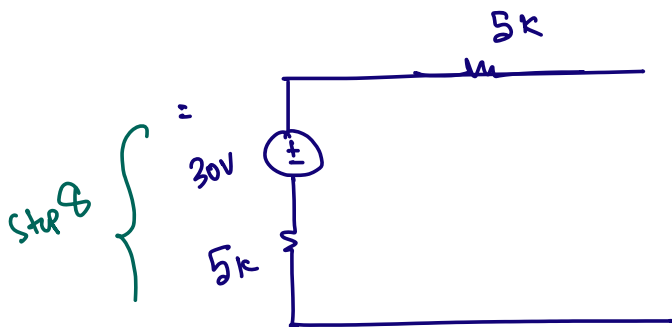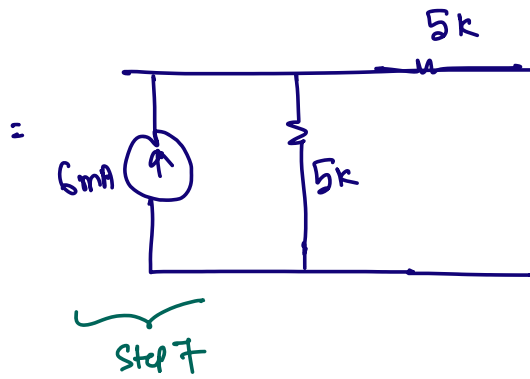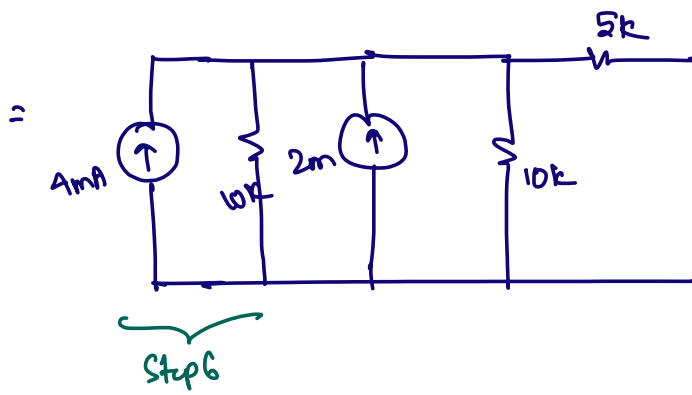

$V' = 30V$	$R' = 10k\Omega$
------------	------------------


- (b) [9 marks] Now, **analyze** the transient behavior of the circuit assuming that the switch moves from position b to position a at $t = 0$. Determine $i(t)$ for $t > 0$.

$t < 0$,

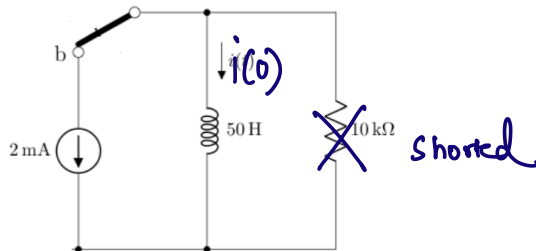


$$i(0) = -2 \text{ mA}.$$

$t > 0$,

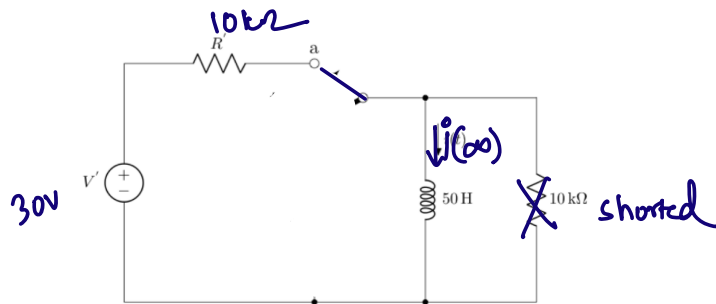

$$i(\infty) = \frac{30 \text{ V}}{10 \text{ k}\Omega} = 3 \text{ mA}$$

Req:

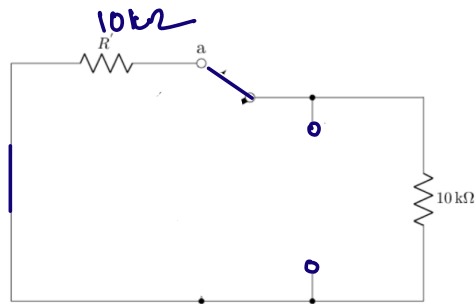


$$R_{eq} = 10k \parallel 10k = 5k\Omega$$

$$\tau = \frac{L}{R} = \frac{50}{5k} = 0.01s$$

$$t > 0, \quad i(t) = 3 + (-2 - 3)e^{-t/0.01} \text{ mA}$$

$$i(t) = 3 - 5e^{-t/0.01} \text{ mA}$$

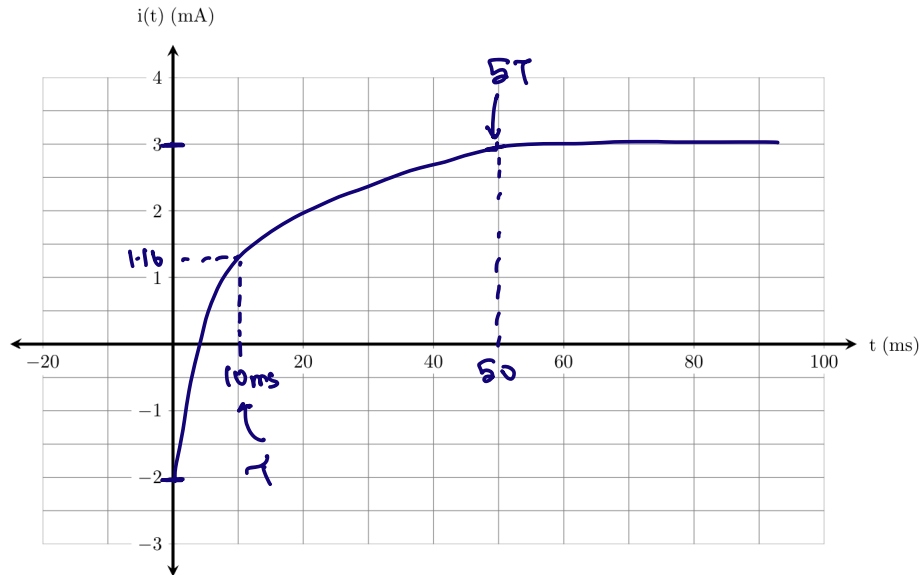- (c) [4 marks] Based on your answer in (b), does the inductor get charged or discharged? In the following grid, draw the current $i(t)$ found in (b) as a function of time. Mark the time where the inductor is fully charged or discharged.




$$i(\infty) > i(0) \therefore \text{charged}$$

$$5T: 5 \times 0.01: 50 \text{ ms}$$

■ Question 2 of 3 [CO2] [15 marks]


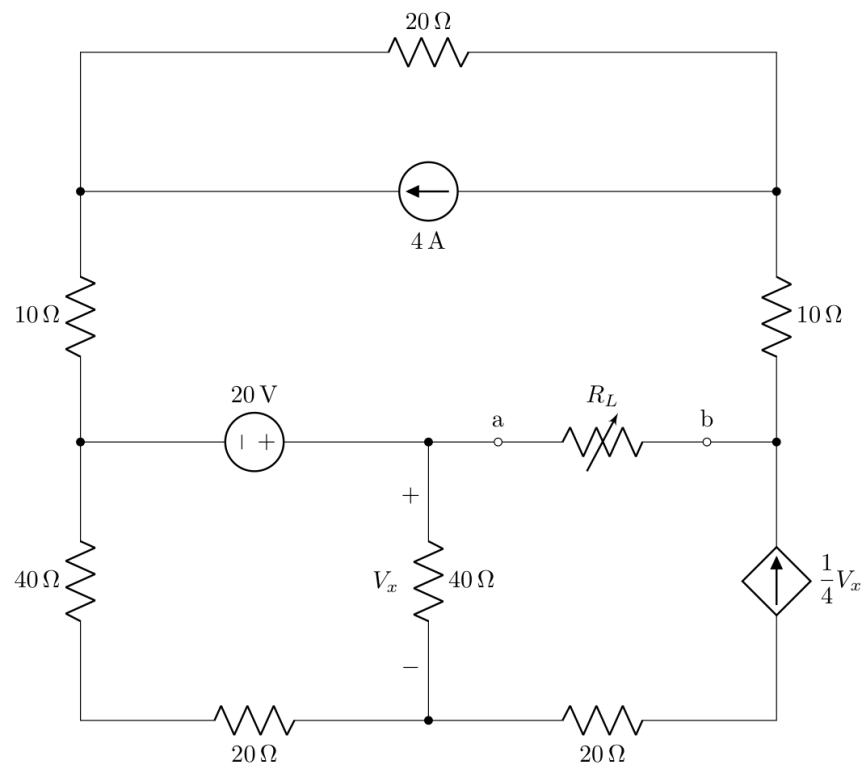
Consider the following circuit with a load R_L connected between terminals a and b.



(a) [8 marks] Determine the value of R_L that will draw the maximum power from the circuit.

Set - A

2(a)

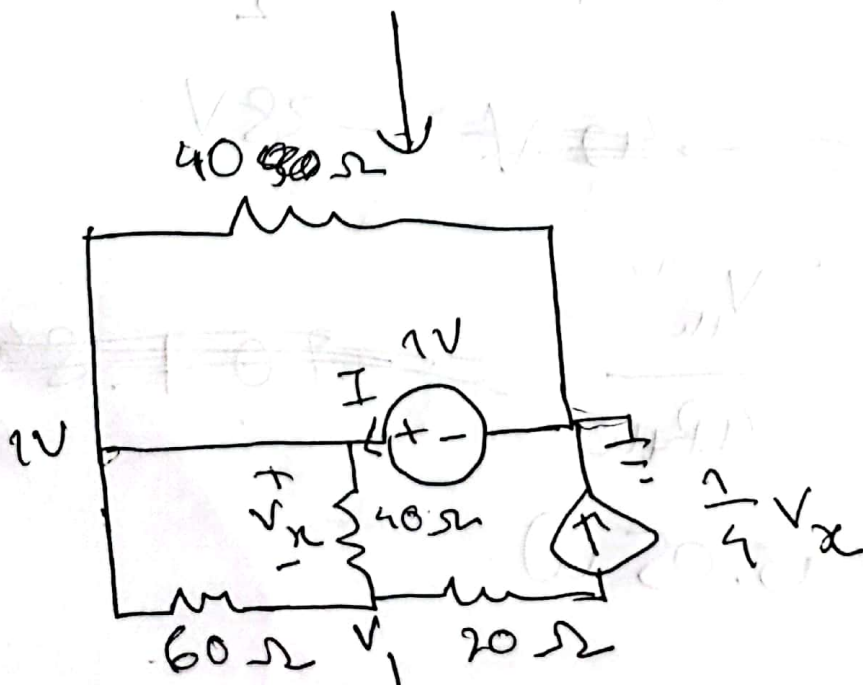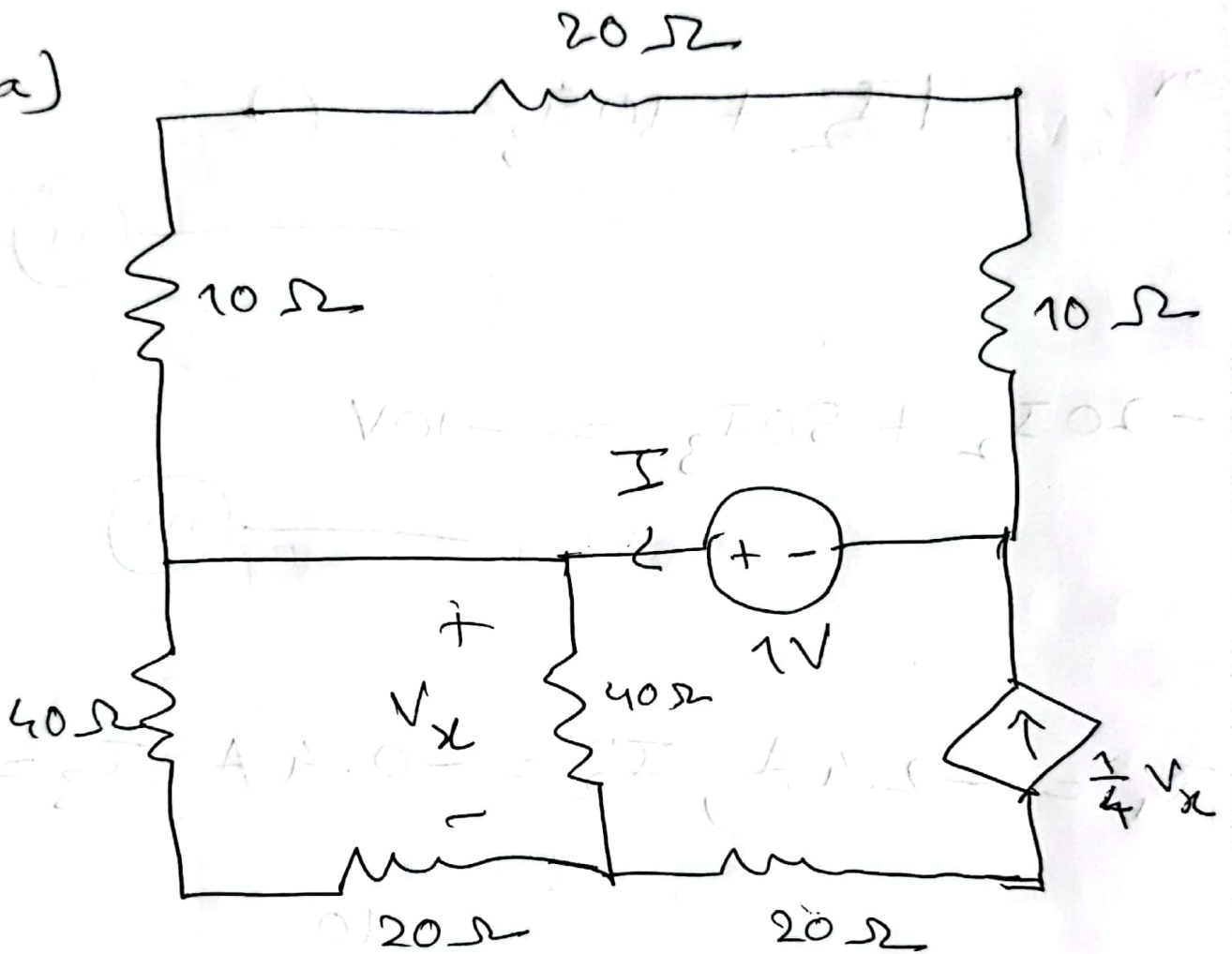

$$V_x = 1 - V_1$$

$$\frac{V_1 - 1}{60} + \frac{V_1 - 1}{40} + \frac{1}{4}(1 - V_1) = 0$$


$$\text{or, } V_1 = 1V$$

$$I = \frac{1}{40} + \frac{1}{4}V_x$$

$$= \frac{1}{40}$$

$$\therefore R_{th} = 40 \Omega$$

(b)

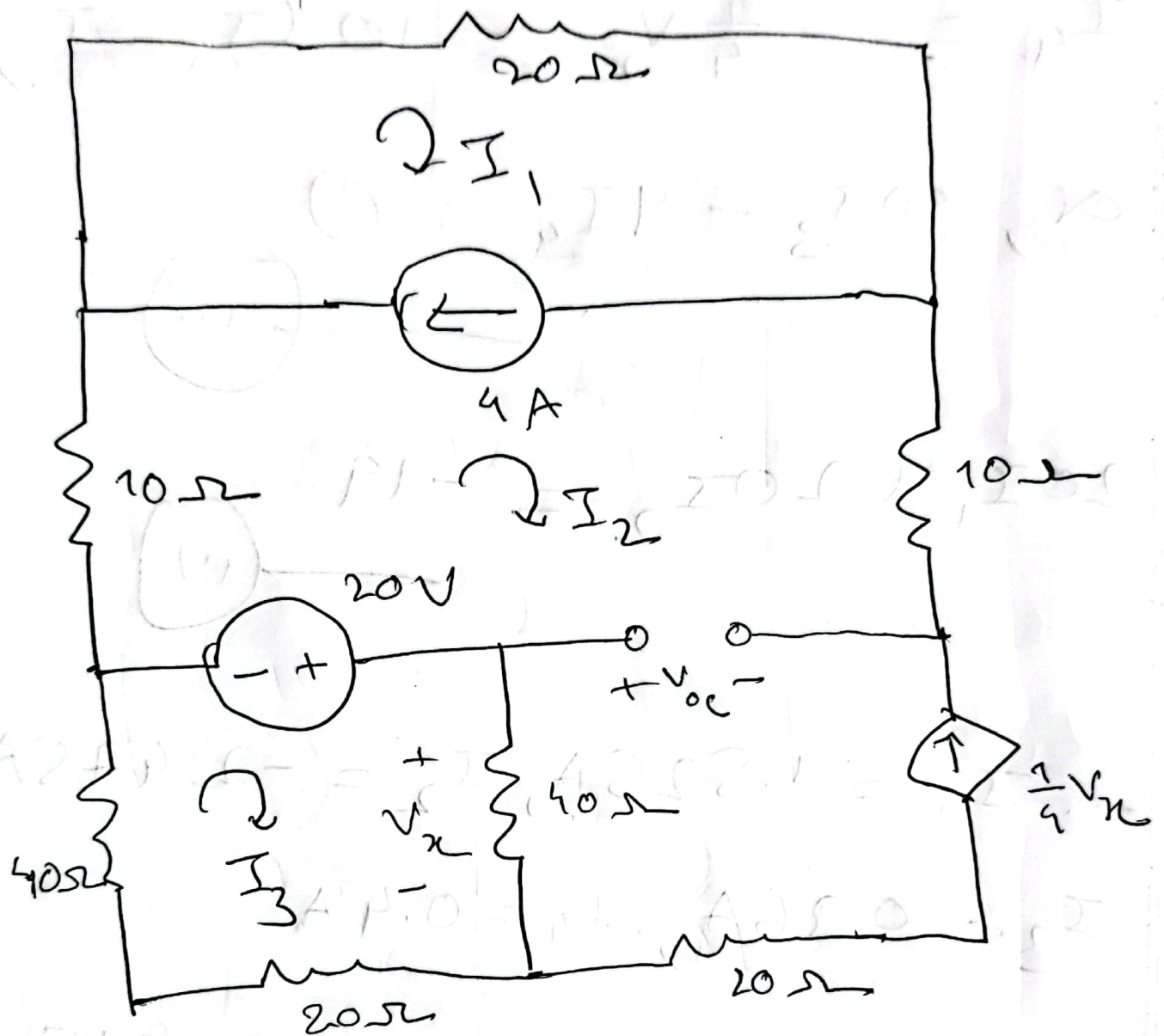

$$I_1 - I_2 = 4 \quad \text{--- (1)}$$

$$V_x = 40(I_3 - I_2)$$

$$I_2 = \text{---} - \frac{1}{4}V_x = 10(I_2 - I_3)$$

$$\text{or, } 9I_2 - 10I_3 = 0$$



$$-40I_2 + 100I_3 = 20$$



$$\therefore I_1 = 4.4 \text{ A}, I_2 = 0.4 \text{ A}, I_3 = 0.36 \text{ A}$$


$$\therefore V_{oc} = V_{th} = 20I_1 + 10I_2 + 20 + 10I_2 = 116 \text{ V}$$

$$\therefore P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{116^2}{4 \times 1.5} = 84.1 \text{ W}$$

$$= 84.1 \text{ W}$$

■ Question 3 of 3 [CO3] [20 marks]

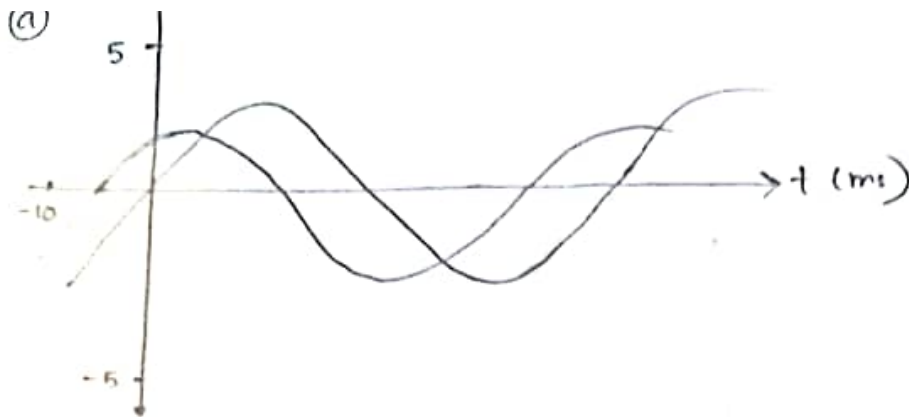- (a) [4 marks] The input $v_{in}(t)$ and output $v_{out}(t)$ voltage waveforms of a two terminal ac circuit are plotted as a function of time below. **Determine** mathematically the phase difference between the two and specify which one is leading.



~~Ans~~ v_{out} → leading

$$f = \frac{1}{T} = \frac{1}{40 \times 10^{-3}} = 25 \text{ Hz}$$


$$\Delta t = 10 \times 10^{-3} \text{ s}$$

$$\theta = 360^\circ \times f \times \Delta t$$

$$= 360^\circ \times \frac{1}{40 \times 10^{-3}} \times 10 \times 10^{-3}$$

$$= 90^\circ$$

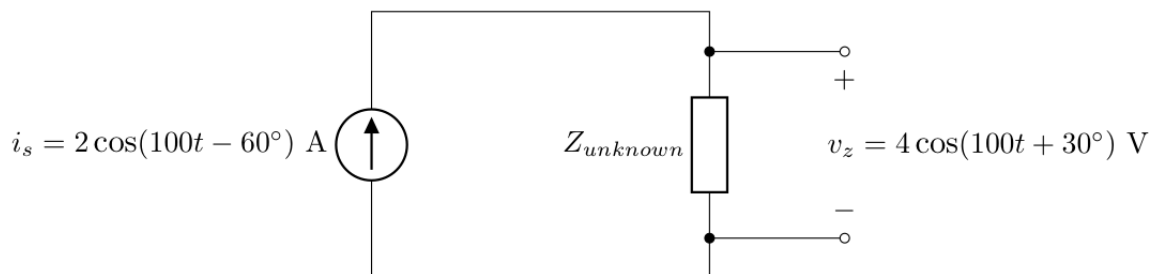- (b) When a current of $i_s = 2 \cos(100t - 60^\circ)$ A passes through an unknown circuit element with an impedance of $Z_{unknown}$, it causes a voltage drop of $v_z = 4 \cos(100t + 30^\circ)$ V across it as shown below.



- [1 mark] Does the voltage (v_z) lead or lag the current (i_s)?
- [1 mark] Determine the value of the impedance $Z_{unknown}$.
- [2 marks] Based on your answer in (ii), guess the circuit element and **determine** the value of it with appropriate units.

(b) $Z_{\text{impedance}} = \frac{4 \angle 30^\circ}{2 \angle -60^\circ} = 2j \rightarrow \text{inductor}$
 $S_{\text{av}} = j\omega L = 2j$ $\omega = 100$
 $100 \times L = 2$
 $L = \frac{2}{100} = 0.02 \text{ H}$


~~2A~~ $L = \frac{2}{2A \times 25}$

(i) V_2 leads i_6

(ii) $Z_{\text{unknown}} = 2j$


(iii) $L = 0.02 \text{ H}$

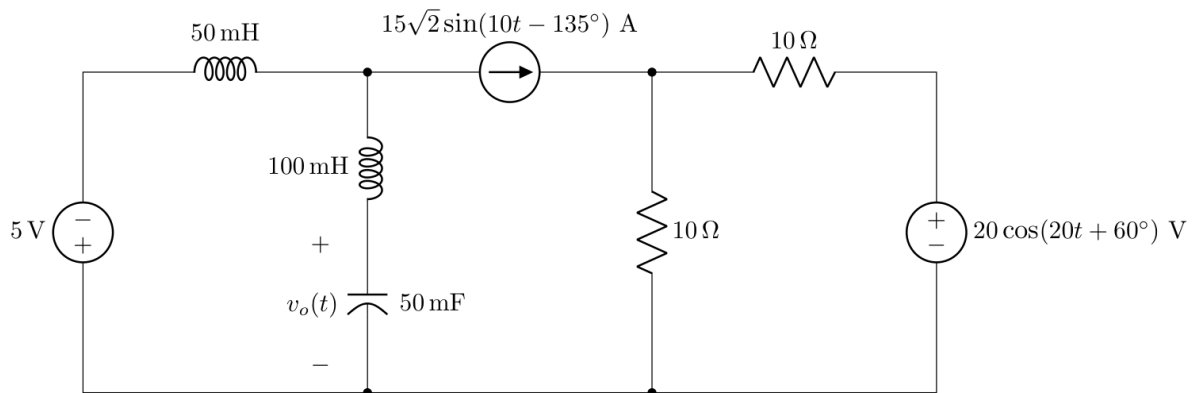(c) [12 marks] For the circuit shown below, **determine** $v_o(t)$, the voltage across the capacitor.



2

DC source active:

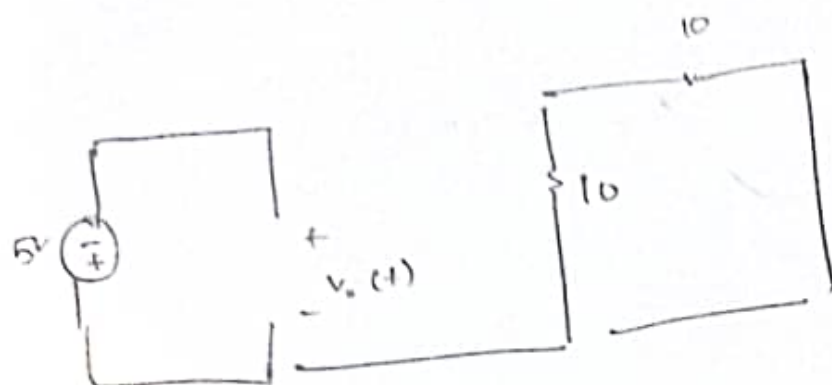

$$V_o(t) = -5V$$


AC Current:

$$\omega = 10$$

$$Z_1 = j\omega L_1 = j \times 10 \times 50 \times 10^{-3} = 0.5j$$

$$Z_2 = j\omega L_2 = j \times 10 \times 100 \times 10^{-3} = 1j$$
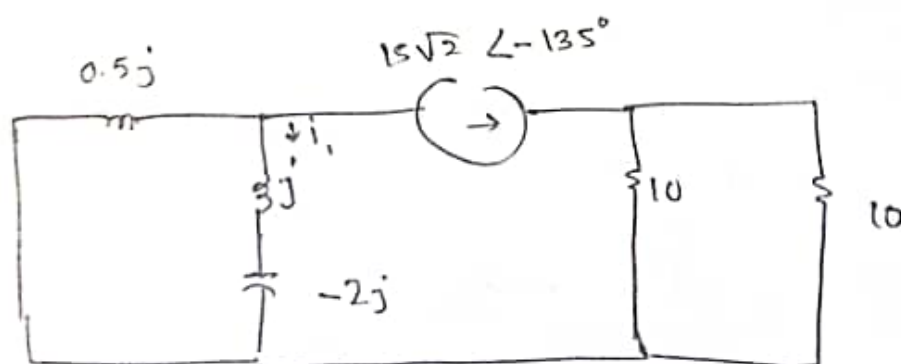
$$Z_3 = \frac{1}{j \times 10 \times 50 \times 10^{-3}} = -2j$$



$$i_1 = \frac{\frac{1}{j-2j}}{\frac{1}{0.5j} + \frac{1}{j-2j}} \times 15\sqrt{2} \angle -135^\circ$$

$$i_1 = 20.8 \angle 132.69^\circ \quad 15\sqrt{2} \angle -135^\circ$$

$$V_o = (-2j \times i_1) = 41.60 \angle 123.7^\circ$$

$$= 30\sqrt{2} \angle 135^\circ$$


AC voltage:

$$\omega = 20 \text{ rad/s}$$

$$Z_1 = j\omega L_1 = j$$

$$Z_2 = 2j$$

$$Z_3 = -j$$

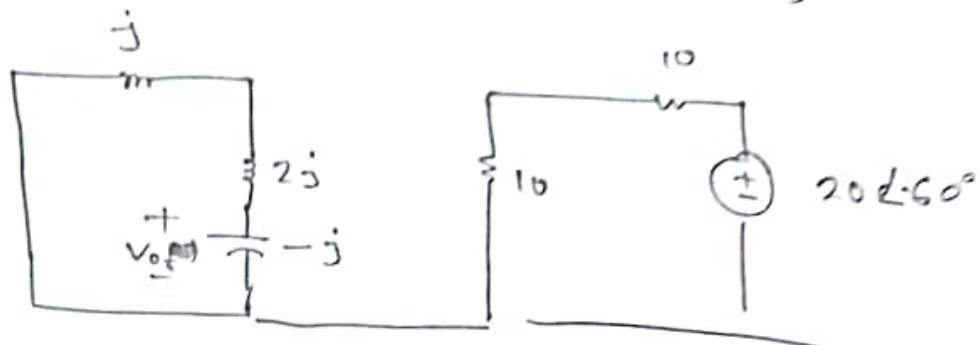

$$V_{o3} = 0 \text{ V}$$

$$S_{\circ} \quad V_o = V_{o1} + V_{o2} + V_{o3}$$

$$= -5 + 41.6 \sin(10t - 135^\circ) + 0$$

$$= -5 + 41.6 \sin(10t + 143^\circ - 31^\circ)$$

$$= -5 + 30\sqrt{2} \sin(10t + 135^\circ) \text{ V}$$