

ID:

Name:

Brac University

Semester: Summer 2024

Course Code: CSE250

Circuits And Electronics

Set

B

Assessment: *Final Exam*

Duration: 1 hour 15 minutes

Date: October 7, 2024


Full Marks (incl. bonus 5): 50

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ At the end of the exam, both the **answer script** and the **question paper** must be returned to the invigilator.
- ✓ All **4 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Draw the plots for the questions **1(c)** and **2(b)** in the grids provided on the question paper.
- ✓ Symbols have their usual meanings.

■ Question 1 of 4



[CO3] [16 marks]

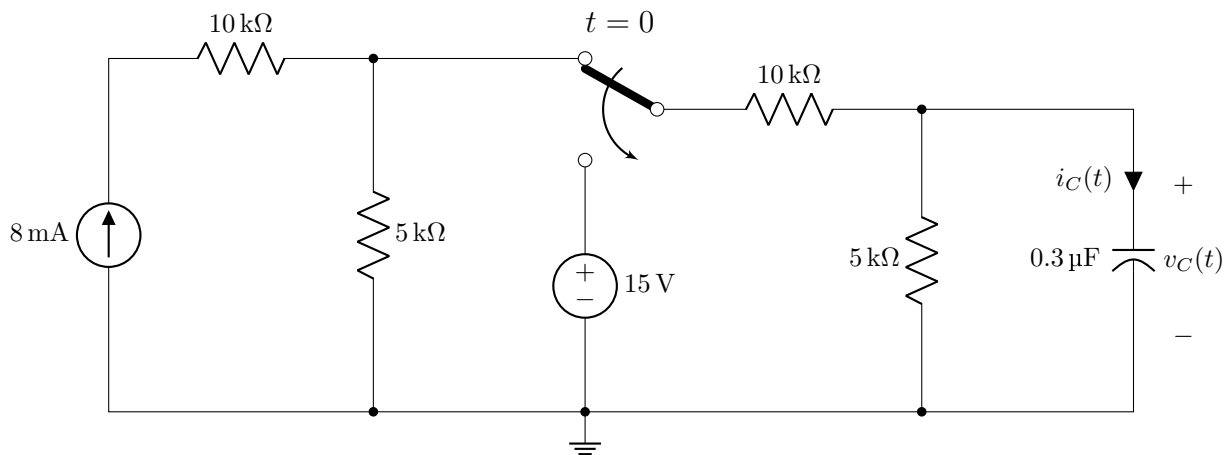The switch in the following circuit shifts at $t = 0$.



Analyze the Transient Behavior to answer the following questions–

- (a) [10 marks] Determine the voltage response of the capacitor $v_C(t)$ as a function of time for $t > 0$.
- (b) [3 marks] Determine the current $i_C(t)$ through the capacitor for $t > 0$.
- (c) [3 marks] On the grids provided below, approximately draw the $v_C(t)$ and $i_C(t)$ found in (a) and (b) respectively.

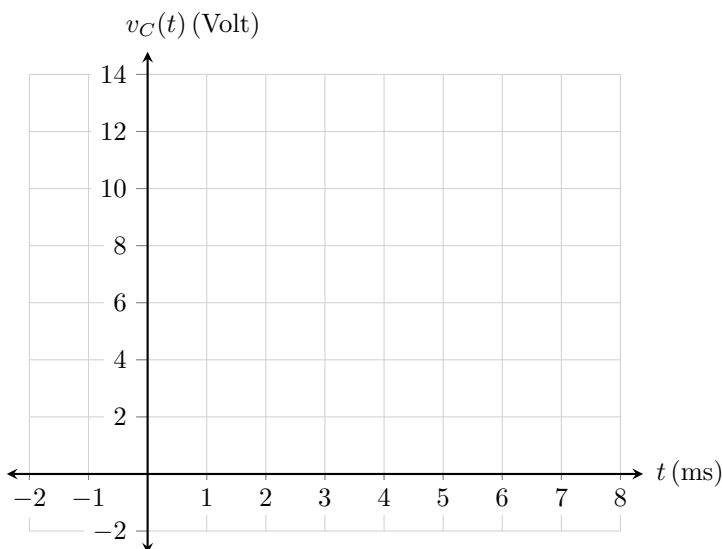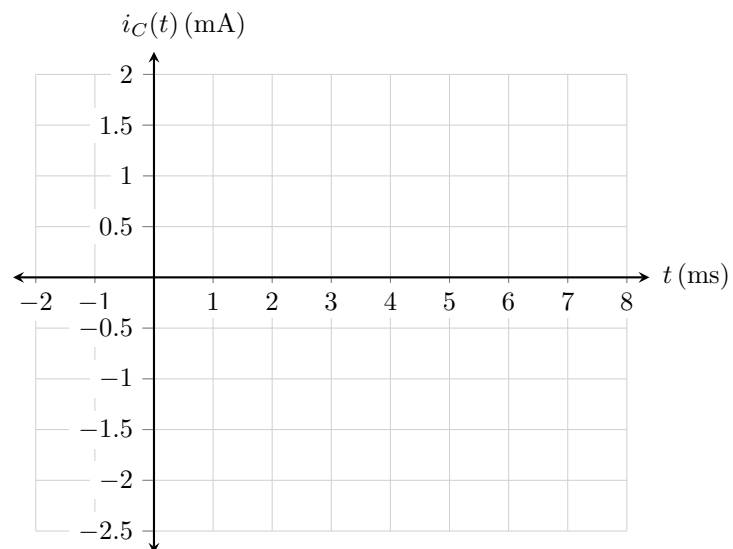Grid for $v_C(t)$ Grid for $i_C(t)$

■ Question 2 of 4

[CO3] [10 marks]

When a voltage $V = 5\text{ V}$ is applied between terminals a and b of a linear two terminal circuit 'X', the circuit draws a current $I = 2\text{ A}$ as shown in *Figure 1* below. When the terminals are shorted, 3 A current flows as shown in *Figure 2*.

- (a) [2 marks] Derive a relationship between I and V .
- (b) [2 marks] Draw the relationship found in (a) on the grid provided below.
- (c) [6 marks] If the circuit in *Figure 3* is an alternative version of the circuit 'X', determine the voltage V' and the resistance R' .

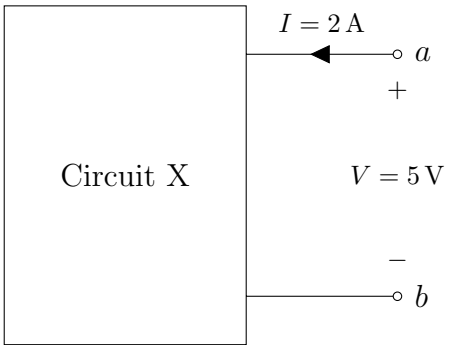


Figure 1

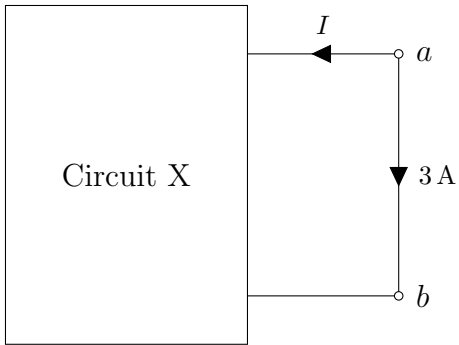


Figure 2



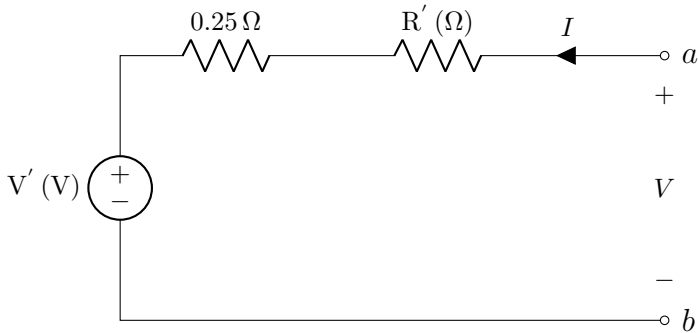


Figure 3

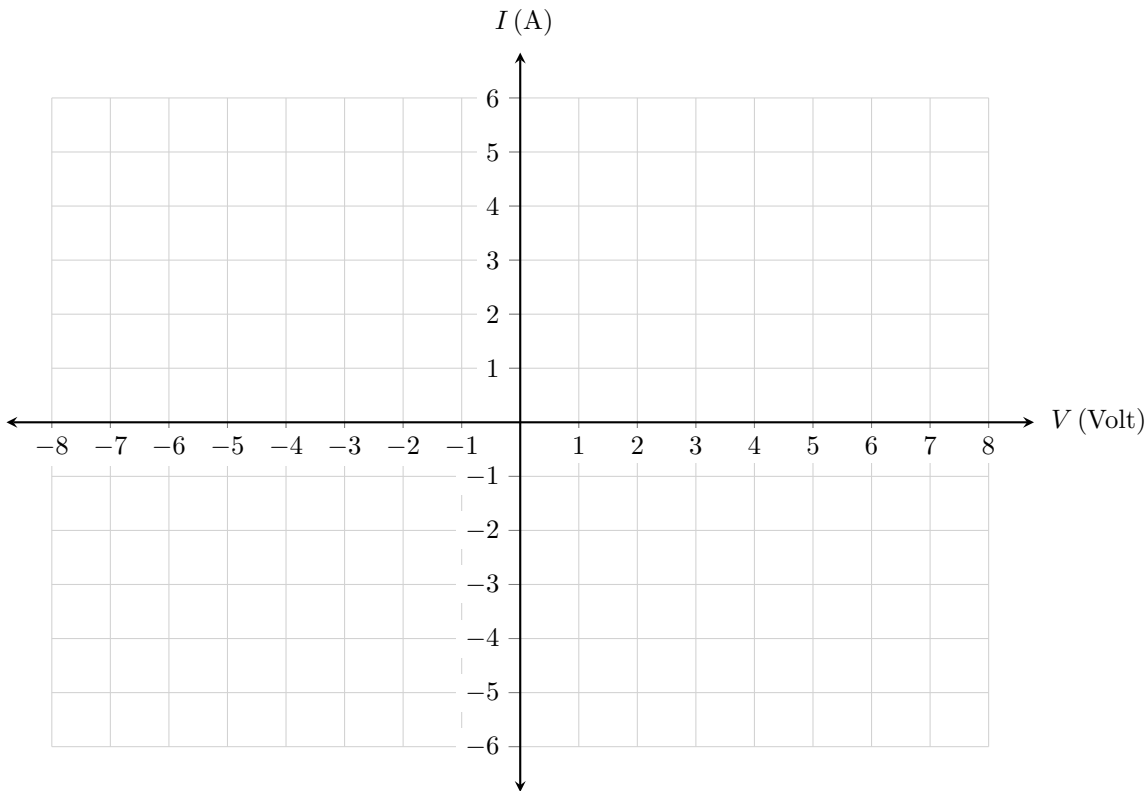

■ Question 3 of 4

[CO3] [16 marks]

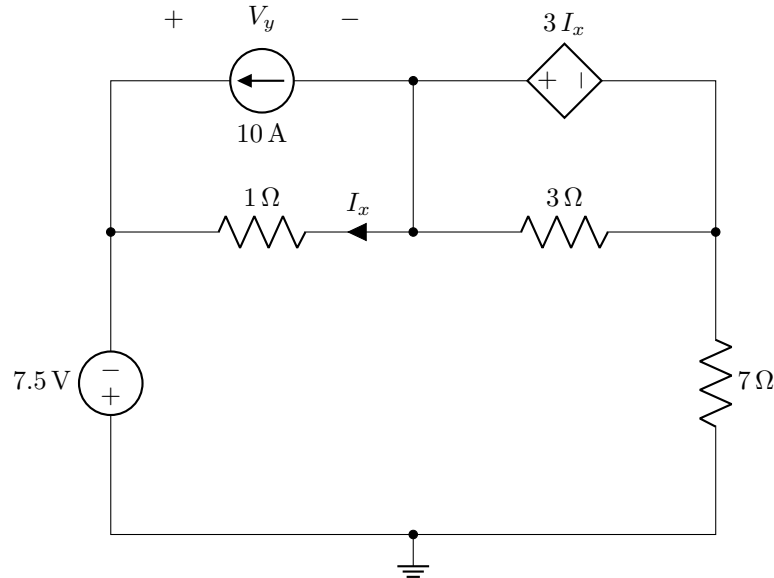

From the above circuit, answer the following questions-

- (a) [13 marks] Find V_y using **Superposition principle**.


After applying Superposition principle you may use any analysis technique you prefer (Nodal, Mesh, Src Tx etc.).

- (b) [3 marks] Find the **power consumed/supplied** by the **current source** (with proper \pm sign and unit).

■ Question 4 of 4

[CO3] [8 marks]

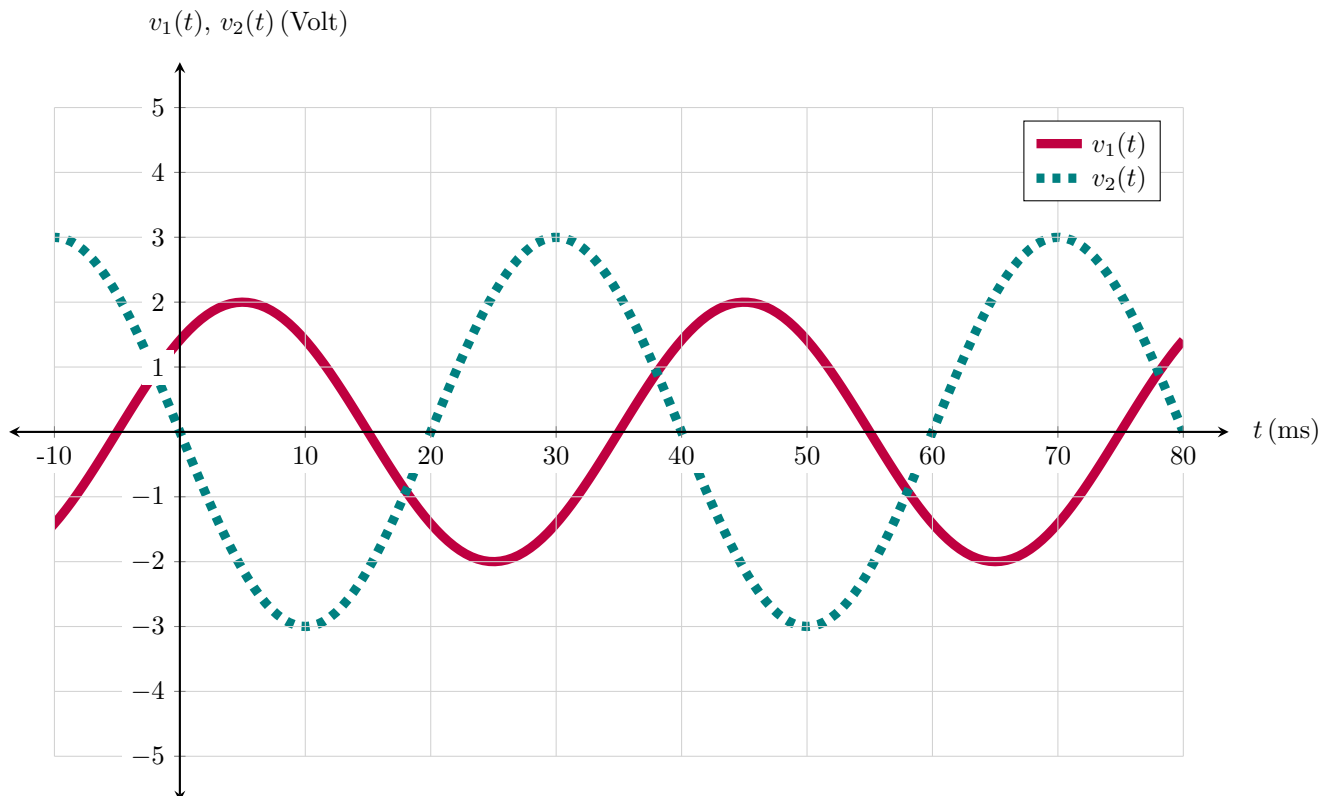Two ac voltage waveforms $v_1(t)$ and $v_2(t)$ from a circuit are plotted below as a function of time t .



- (a) [4 marks] Determine the phase difference between the two and specify which one is leading.
- (b) [4 marks] Write analytical expressions for both $v_1(t)$ and $v_2(t)$. From the expressions, verify the fact found in (a).