

ID:

Name:

**Brac University****Set: 2**

Inspiring Excellence

Semester: Fall 2022

Course No: CSE250

Course Title: CIRCUITS AND ELECTRONICS

Date: January 02, 2023


Final Exam

Full marks: 50 (+5 Bonus)

Duration: 2 hours

**Questions 1 to 3 are mandatory.** Numbers inside box brackets indicate marks.**Question 1 of 4 [15 marks]** [CO2, CO3, CO4]

Consider the circuit show below.

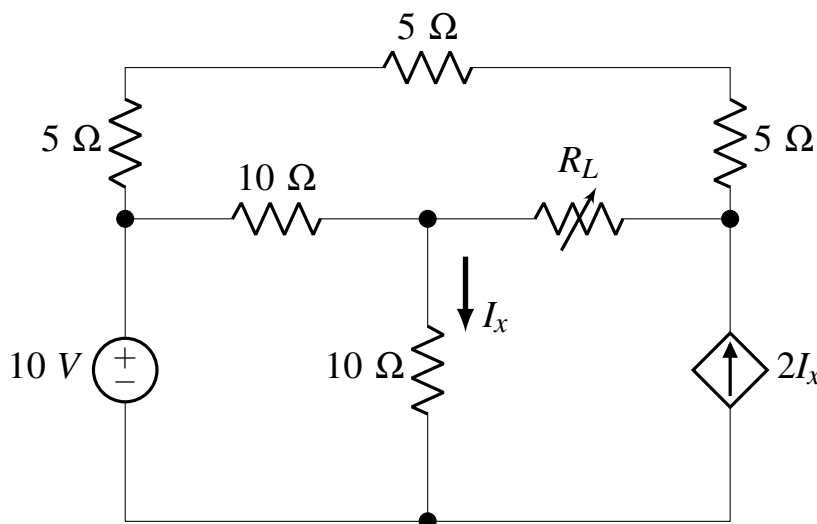

(i)  $R_L = 5\Omega$

ii)  $V_{Th} = \pm 20V$


$P_{max} = 20W$

- (i) **Determine** the value of  $R_L$  that will draw **Maximum Power** from the rest of the circuit. [8]

- (ii) **Determine** that value of the **Maximum Power**. [7]

**Question 2 of 4 [20 marks]** [CO4, CO5]

**Part A:** The figure below shows the current response of a series  $RL$  circuit to a sudden DC current applied through an equivalent resistance of  $6\text{ k}\Omega$ . **Determine** the approximate **time constant** from the figure. Also, **determine** the value of the **inductor**. **Write** the mathematical expression of  $i(t)$  for  $t > 0$ . [Hint: The time it takes for an inductor to be fully charged is approximately five times the time constant]. [3]

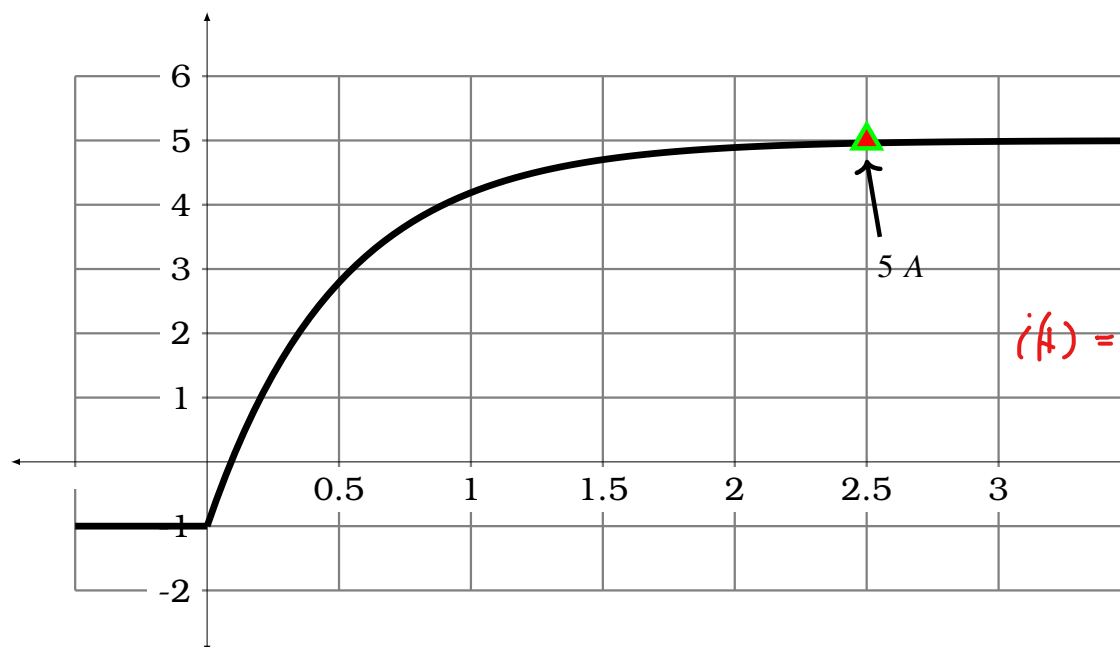 $i(t)$  (A)

$\tau = 0.5ms$

$L = 3H$


$I(0) = -1A$

$I(\infty) = 5A$

$i(t) = 5 - 6e^{-2t} \text{ (A)},$

$t > 0, t \rightarrow ms$

**Part B:** Consider the circuits shown below.

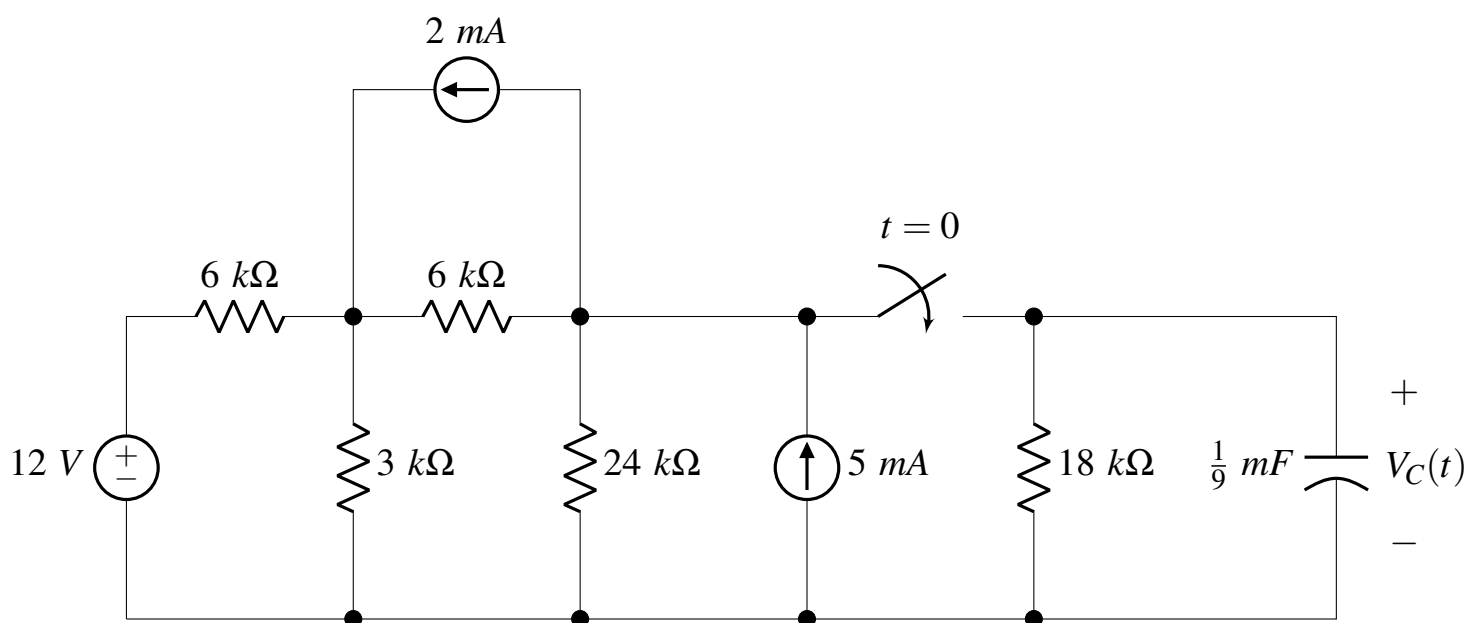

Circuit 1

$$(i) \quad V_1 = 24V$$


$$R_1 = 6k\Omega$$



$$(ii) \quad V(0) = 0V$$

$$V(\infty) = 18V$$

$$\tau = 0.5s$$

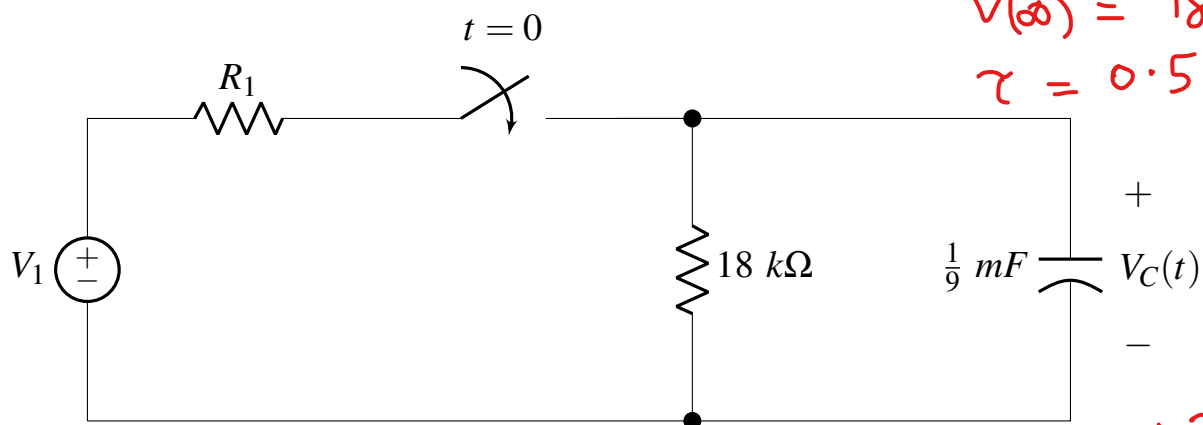

Circuit 2


$$V_C(t) = 18 - 18e^{-2t}, t > 0$$

- (i) **Reduce** the circuit 1 so that it takes the form of the circuit 2 as shown above. [8]
- (ii) **Perform** transient analysis to determine  $V_C(0)$ ,  $V_C(\infty)$ , and  $V_C(t)$  for  $t > 0$ . Also, determine the current through the capacitor at  $t = 0.64$  s. [9]

### Question 3 of 4 [15 marks] [CO4, CO6]

Find  $v_x$  in the circuit shown below [Hint: Use Superposition Principle].


[15]

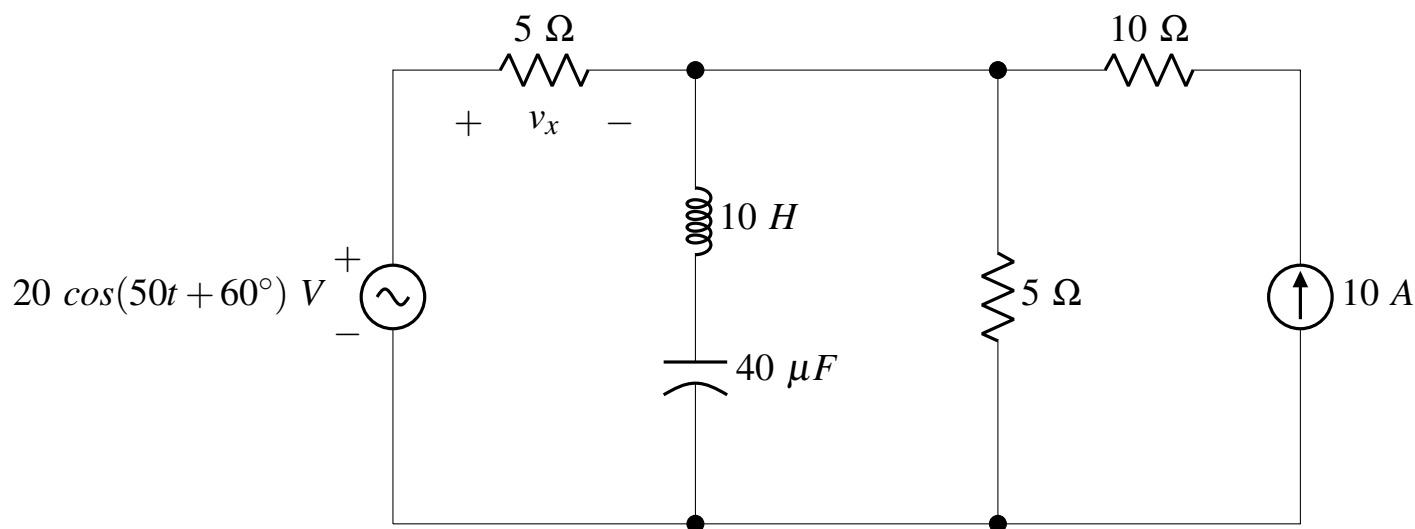

$$v_x(t) = 20 \cos(50t + 60^\circ) - 25 \text{ (V)}$$
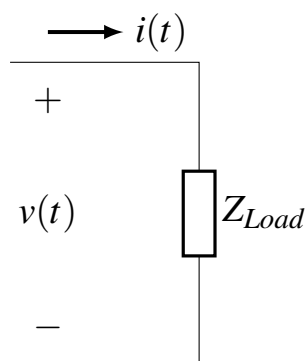
### Question 4 of 4 [Bonus] [5 marks] [CO6]

A series-connected load shown below draws a current  $i(t) = 4 \cos(400t - 30^\circ)$  A when the applied voltage is  $v(t) = -100 \sin(400t - 150^\circ)$  V. **Determine** with appropriate units



[2]

(i) **Complex Power** of the load,

[1]

(ii) **Power Factor** of the load,

[2]

(iii) **Real** and **Reactive Power** absorbed/supplied by the load.