

ID:

Name:

**Brac University**

Semester: Fall 2024

Course Code: CSE250

Circuits And Electronics

Set

A

Assessment: *Midterm Exam*

Duration: 1 hour 10 minutes


Date: November 27, 2024

Full Marks: 44

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ At the end of the exam, both the **answer script** and the **question paper** must be returned to the invigilator.
- ✓ All **3 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Symbols have their usual meanings.

### ■ Question 1 of 3

[CO3] [16 marks]

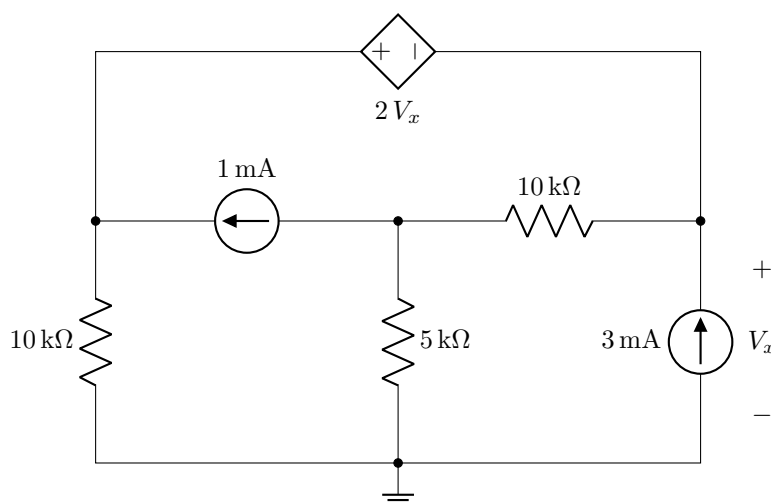


Apply Nodal/Mesh analysis to answer the following questions–

- (a) [12 marks] Find all the node voltages/mesh currents in the circuit shown above.<sup>††</sup> Note that, depending on the analysis method you apply, you have to determine either the mesh currents or the node voltages, not both.
- (b) [4 marks] Determine the power of the the  $2V_x$  dependent voltage source with appropriate  $\pm$  sign and unit. Also mention, whether the source is supplying or absorbing power.

### ■ Question 2 of 3

[CO3] [16 marks]

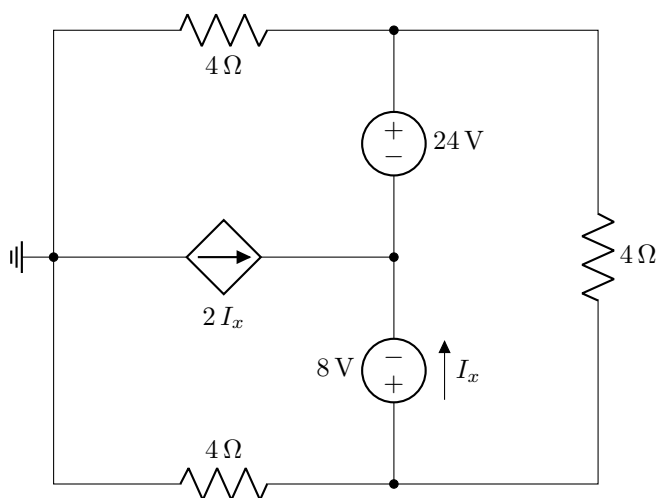

Apply Nodal/Mesh analysis to answer the following questions–


- (a) [12 marks] Find all the node voltages/mesh currents in the circuit shown above.<sup>††</sup> Note that, depending on the analysis method you apply, you have to determine either the mesh currents or the node voltages, not both.
- (b) [1 mark] Which side (top or bottom) of the  $4\ \Omega$  resistor on the right has a higher voltage?
- (c) [3 marks] Determine the voltage across the  $2I_x$  dependent current source.

<sup>††</sup>Node voltage/mesh current variables must be labeled on the diagram


### ■ Question 3 of 3

[CO3, CO1] [12 marks]

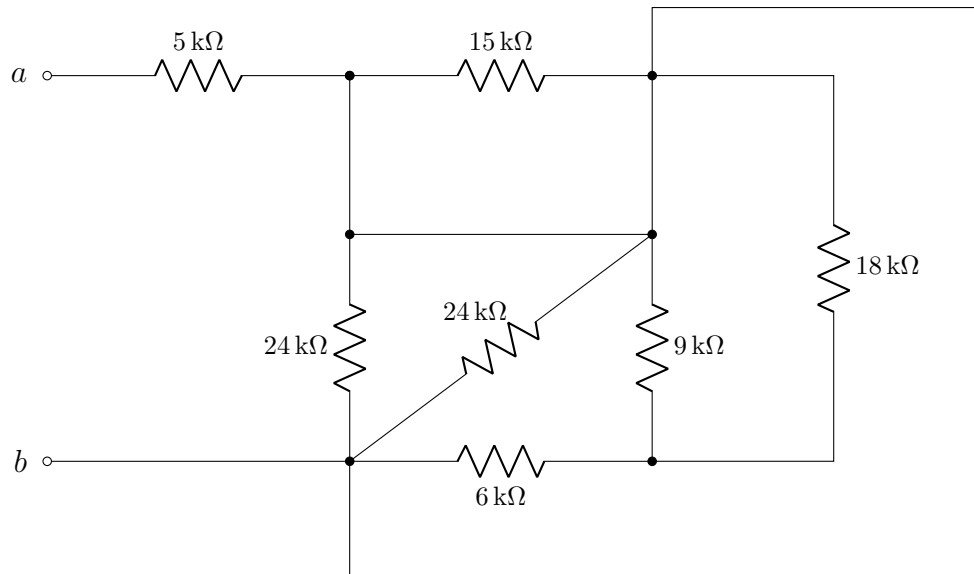- (a) [6 marks] Determine  $R_{ab}$ , the equivalent resistance between the terminals  $a$  and  $b$  in the circuit shown below.



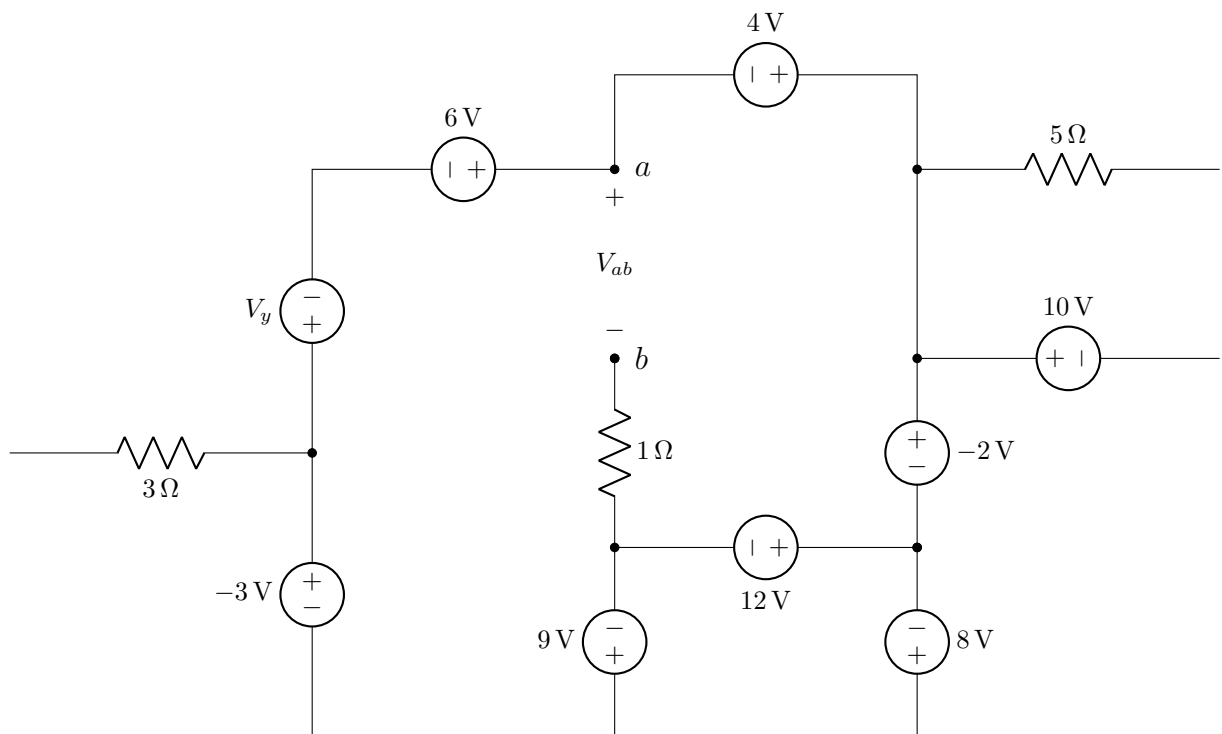- (b) The following circuit consists of only one loop.



**Apply KVL** to answer the following questions–

- [3 marks] Identify the loop and determine the value of  $V_y$  required to satisfy KVL along the loop.
- [3 marks] What is the voltage  $V_{ab}$  across the open terminals  $a$  and  $b$ .

ID:

Name:

**Brac University**

Semester: Fall 2024

Course Code: CSE250

Circuits And Electronics

Set

B

Assessment: *Midterm Exam*

Duration: 1 hour 10 minutes


Date: November 27, 2024

Full Marks: 44

- ✓ No washroom breaks. Phones must be turned off. Using/carrying any notes during the exam is not allowed.
- ✓ At the end of the exam, both the **answer script** and the **question paper** must be returned to the invigilator.
- ✓ All **3 questions** are compulsory. Marks allotted for each question are mentioned beside each question.
- ✓ Symbols have their usual meanings.

### ■ Question 1 of 3

[CO3] [16 marks]

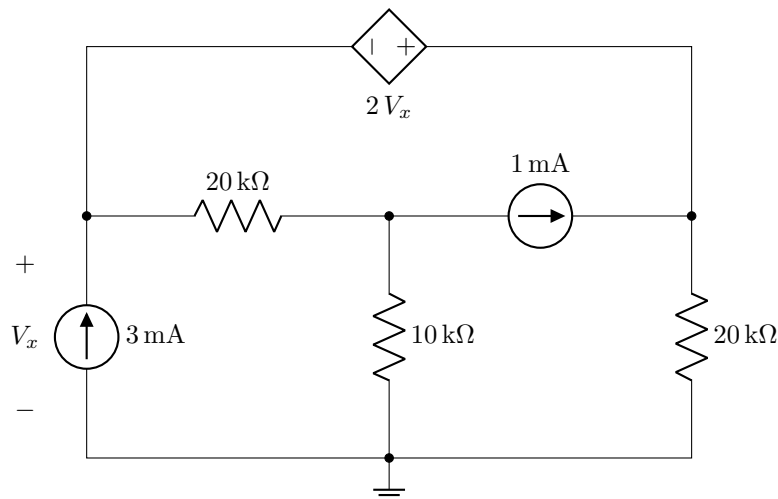


Apply Nodal/Mesh analysis to answer the following questions–

- (a) [12 marks] Find all the node voltages/mesh currents in the circuit shown above.<sup>††</sup> Note that, depending on the analysis method you apply, you have to determine either the mesh currents or the node voltages, not both.
- (b) [4 marks] Determine the power of the the  $2V_x$  dependent voltage source with appropriate  $\pm$  sign and unit. Also mention, whether the source is supplying or absorbing power.

### ■ Question 2 of 3

[CO3] [16 marks]

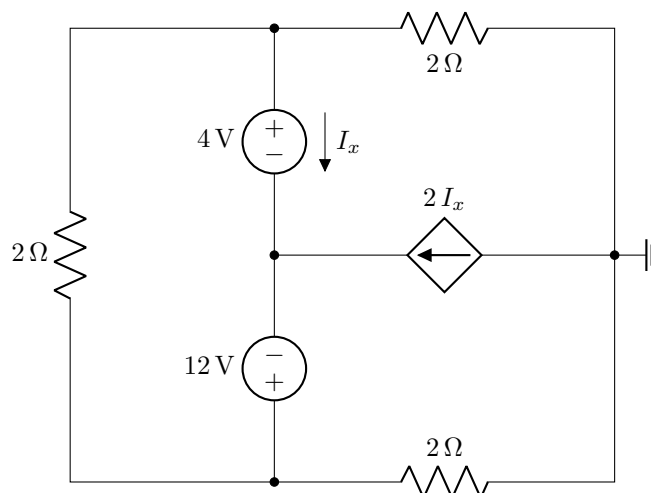

Apply Nodal/Mesh analysis to answer the following questions–


- (a) [12 marks] Find all the node voltages/mesh currents in the circuit shown above.<sup>††</sup> Note that, depending on the analysis method you apply, you have to determine either the mesh currents or the node voltages, not both.
- (b) [1 mark] Which side (top or bottom) of the  $2\Omega$  resistor on the left has a higher voltage?
- (c) [3 marks] Determine the voltage across the  $2I_x$  dependent current source.

<sup>††</sup>Node voltage/mesh current variables must be labeled on the diagram


### ■ Question 3 of 3

[CO3, CO1] [12 marks]

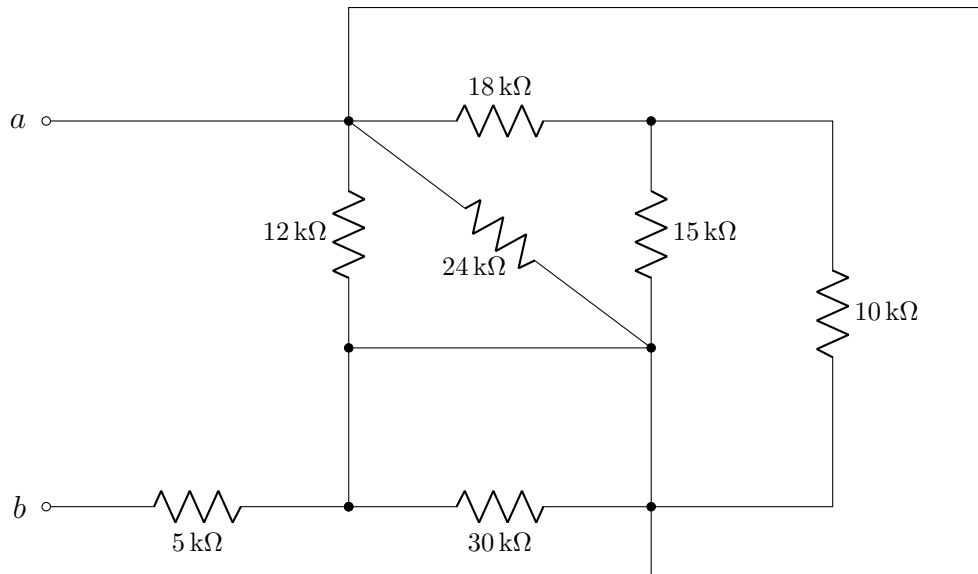(a) [6 marks] Determine  $R_{ab}$ , the equivalent resistance between the terminals  $a$  and  $b$  in the circuit shown below.



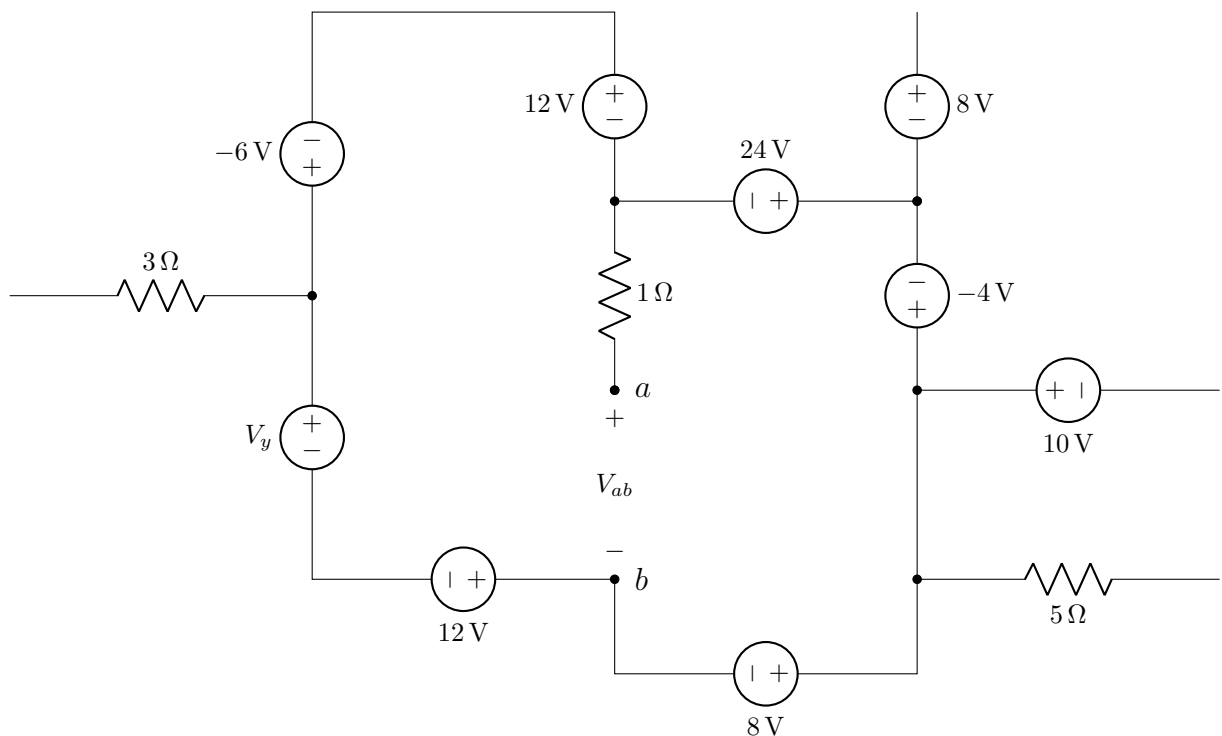(b) The following circuit consists of only one loop.



**Apply KVL** to answer the following questions–

- [3 marks] Identify the loop and determine the value of  $V_y$  required to satisfy KVL along the loop.
- [3 marks] What is the voltage  $V_{ab}$  across the *open* terminals  $a$  and  $b$ .