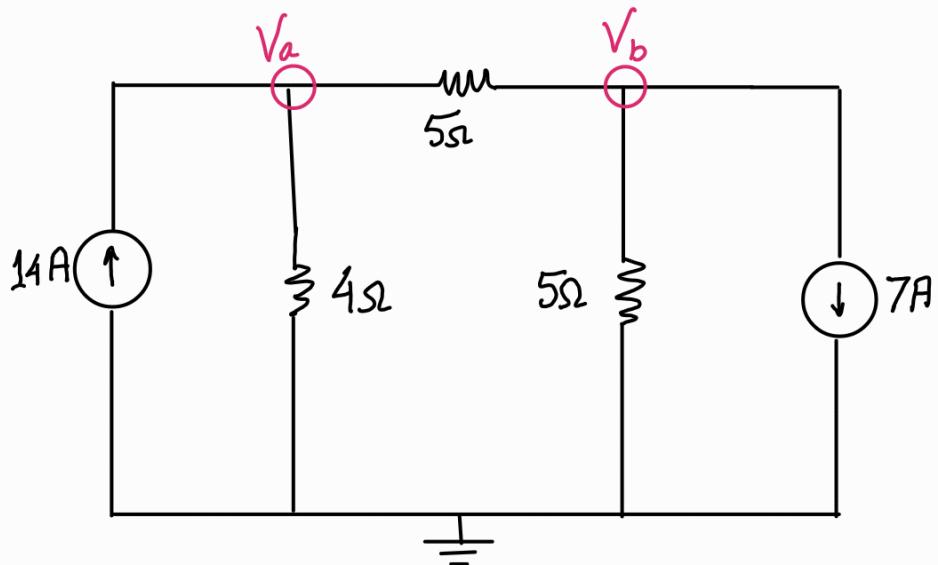


Problem 3



Find all node voltages

KCL @ a —

$$-14 + \frac{V_a}{4} + \frac{V_a - V_b}{5} = 0$$

$$\Rightarrow 5V_a + 4V_a - 4V_b = 280$$

$$\Rightarrow 9V_a - 4V_b = 280 \quad \textcircled{i}$$

KCL @ b —


$$7 + \frac{V_b}{5} + \frac{V_b - V_a}{5} = 0$$

$$\Rightarrow V_a - 2V_b = 35 \quad \textcircled{ii}$$

Solving \textcircled{i} & \textcircled{ii} — $V_a = 30\text{V}$
 $V_b = -2.5\text{V}$

Answer — $0\text{V}, 30\text{V}, -2.5\text{V}$

Problem 4

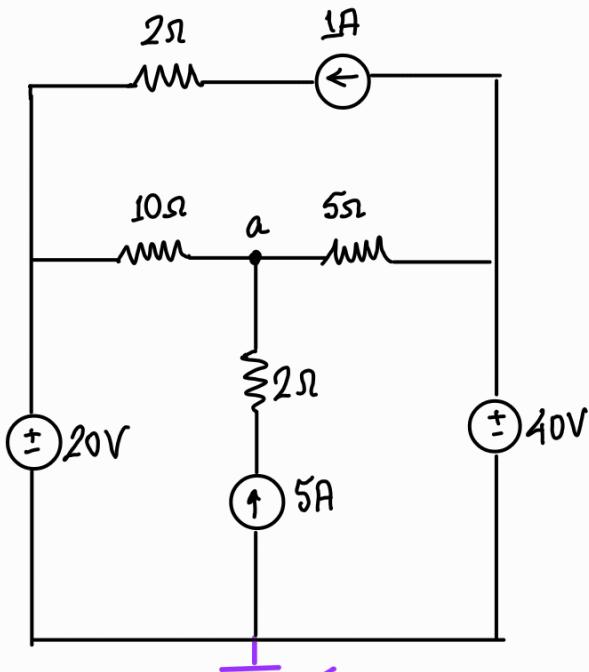

Find V_a

This is an example of a problem that will never come in the central exam (probably)

Since there is no fixed ground location, you can literally place a ground on the node a and write the answer as 0V.

If you place a ground here → the equation @ a (KCL) —


$$\frac{V_a - 20}{10} + \frac{V_a - 40}{5} - 5 = 0$$

$$\Rightarrow V_a - 20 + 2V_a - 80 = 50$$

$$\Rightarrow 3V_a = 150$$

$$\Rightarrow V_a = 50$$

Problem 5

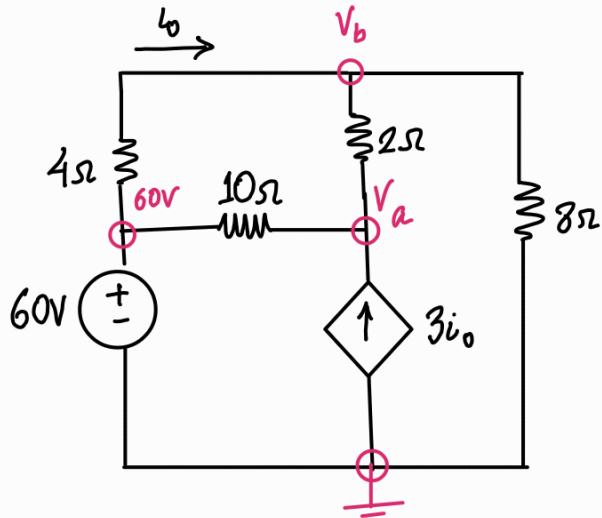

Find i_o using nodal analysis. Determine the current supplied by the 60V source.

KCL @ a —

$$-3i_o + \frac{V_a - 60}{10} + \frac{V_a - V_b}{2} = 0$$

$$\Rightarrow V_a - 60 + 5V_a - 5V_b - 30i_o = 0$$

$$\Rightarrow 6V_a - 5V_b - 60 - 30i_o = 0 \quad \textcircled{i}$$

KCL @ b —

$$\frac{V_b - 60}{4} + \frac{V_b - V_a}{2} + \frac{V_b}{8} = 0$$

$$\Rightarrow 2V_b - 120 + 4V_b - 4V_a + V_b = 0$$

$$\Rightarrow 4V_a - 7V_b = -120 \quad \textcircled{ii}$$

From the ckt —

$$i_o = \frac{60 - V_b}{4} = 15 - \frac{V_b}{4}$$

$$\therefore \textcircled{i} \Rightarrow 6V_a - 5V_b - 450 - 60 + \frac{15V_b}{2} = 0$$

$$\Rightarrow 12V_a + 5V_b = 1020 \quad \textcircled{iii}$$


Solving \textcircled{ii} & \textcircled{iii} —

$$V_a = 62.88 \text{ V} \quad \& \quad V_b = 53.077 \text{ V}$$


$$\therefore i_o = \frac{60 - 53.077}{4} \text{ A} = 1.731 \text{ A}$$

$$I = i_o + \frac{60 - 62.88}{10} = 1.731 - 0.288$$

$= 1.443 \text{ A}$ (Wrong answer in the slide)

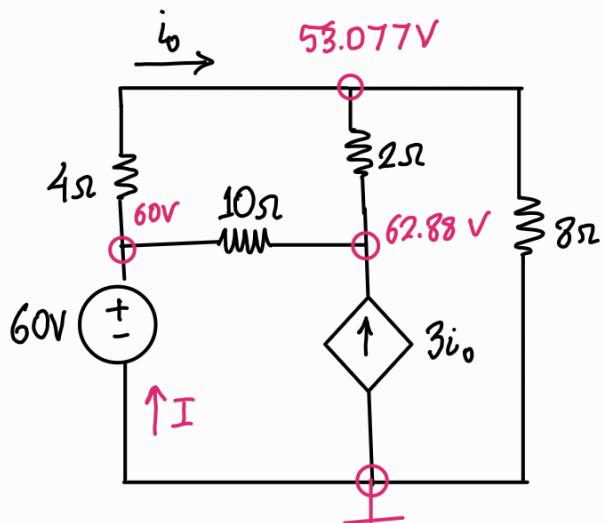

Problem 6

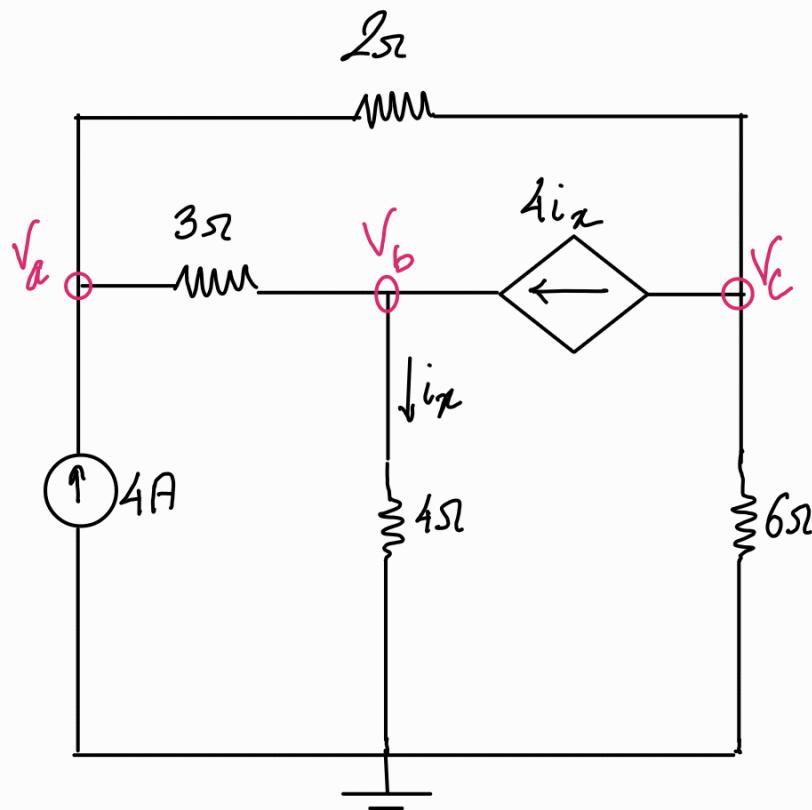

Find the node voltages

KCL @ a —

$$-4 + \frac{V_a - V_b}{3} + \frac{V_a - V_c}{2} = 0$$

$$\Rightarrow 2V_a - 2V_b + 3V_a - 3V_c = 24$$

$$\Rightarrow 5V_a - 2V_b - 3V_c = 24 \quad \textcircled{i}$$

KCL @ b —

$$\frac{V_b - V_a}{3} + \frac{V_b}{4} - 4i_x = 0$$

$$\Rightarrow 4V_b - 4V_a + 3V_b - 12V_b = 0 \quad [\text{From } \textcircled{ii}]$$

$$\Rightarrow 4V_a + 5V_b = 0 \quad \textcircled{iii}$$

KCL @ c —

$$\frac{V_c - V_a}{2} + 4i_x + \frac{V_c}{6} = 0$$

$$\Rightarrow 3V_c - 3V_a + 6V_b + V_c = 0 \quad [\text{From } \textcircled{ii}]$$

$$\Rightarrow 3V_a - 6V_b - 4V_c = 0 \quad \textcircled{iv}$$

Solving $\textcircled{i}, \textcircled{iii}$ & \textcircled{iv} —


$$V_a = 32V$$

$$V_b = -25.6V$$

$$V_c = 62.4V$$

$$\text{and } V_{\text{ref}} = 0V$$

Problem 7

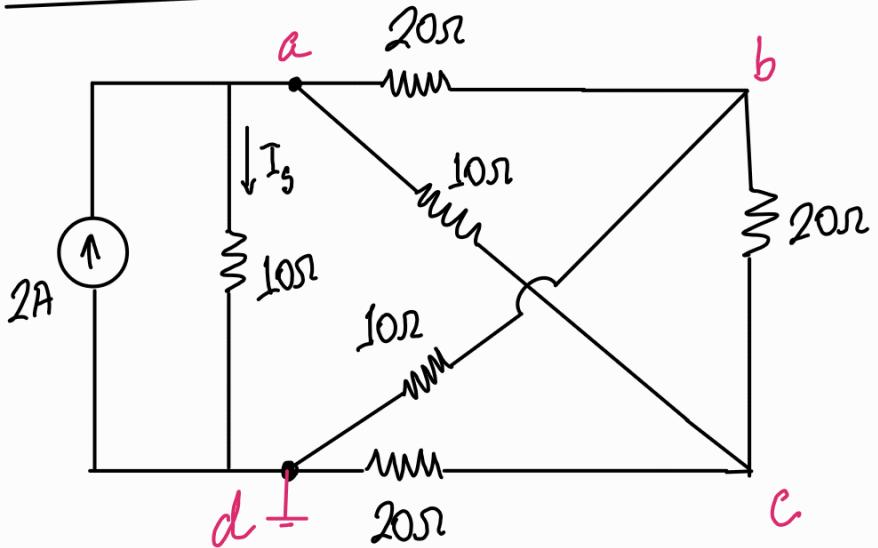

Find I_s using nodal analysis

KCL @ a —

$$-2 + \frac{V_a}{10} + \frac{V_a - V_c}{10} + \frac{V_a - V_b}{20} = 0$$

$$\Rightarrow 2V_a + 2V_a - 2V_c + V_a - V_b = 40$$

$$\Rightarrow 5V_a - V_b - 2V_c = 40 \quad \textcircled{i}$$

KCL @ b —

$$\frac{V_b - V_a}{20} + \frac{V_b}{10} + \frac{V_b - V_c}{20} = 0$$

$$\Rightarrow V_b - V_a + 2V_b + V_b - V_c = 0$$


$$\Rightarrow -V_a + 4V_b - V_c = 0 \quad \textcircled{ii}$$

Solving \textcircled{i} , \textcircled{ii} & \textcircled{iii} —

$$V_a = 11.76 \text{ V} \quad V_b = 4.71 \text{ V} \quad V_c = 7.06 \text{ V}$$

$$\therefore I_s = \frac{V_a}{10} = 1.18 \text{ A}$$

Problem 8

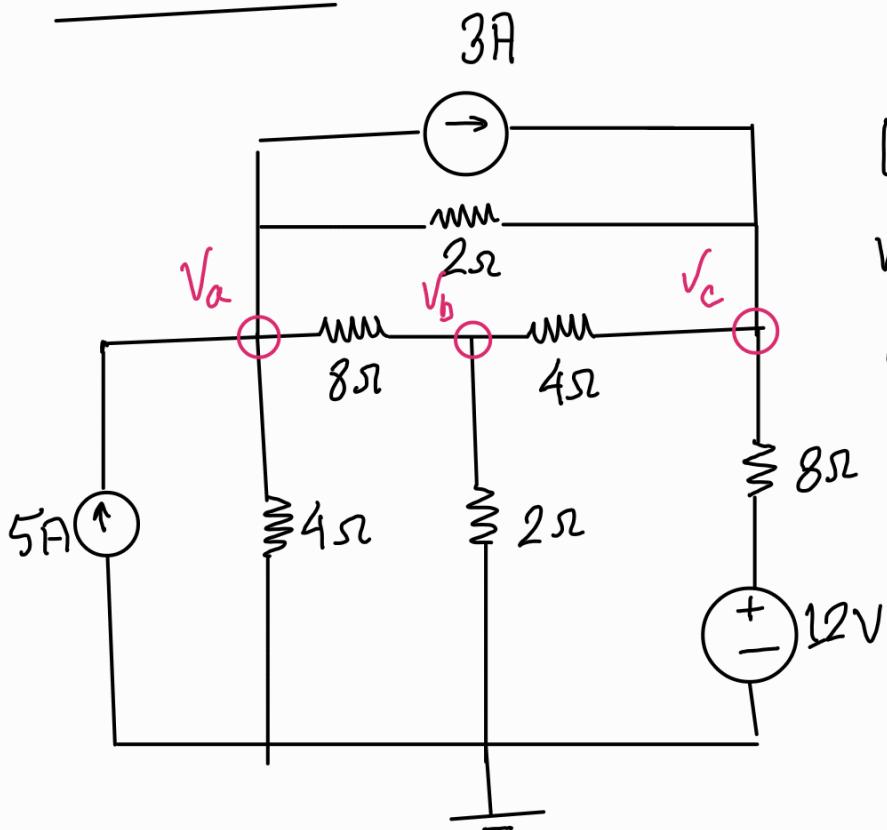

Use nodal analysis to determine voltage across the 3A current source. Also find the power of the source. Is it absorbing or supplying?

KCL @ a —

$$-5 + \frac{V_a}{4} + \frac{V_a - V_b}{8} + \frac{V_a - V_c}{2} + 3 = 0$$

$$\Rightarrow 2V_a + V_a - V_b + 4V_a - 4V_c = 16$$

$$\Rightarrow 7V_a - V_b - 4V_c = 16 \quad \textcircled{i}$$

KCL @ b —

$$\frac{V_b - V_a}{8} + \frac{V_b}{2} + \frac{V_b - V_c}{4} = 0$$

$$\Rightarrow V_b - V_a + 4V_b + 2V_b - 2V_c = 0$$

$$\Rightarrow -V_a + 7V_b - 2V_c = 0 \quad \textcircled{ii}$$

KCL @ C —

$$-3 + \frac{V_c - V_a}{2} + \frac{V_c - V_b}{4} + \frac{V_c - 12}{8} = 0$$

$$\Rightarrow 4V_c - 4V_a + 2V_c - 2V_b + V_c - 12 = 24$$

$$\Rightarrow -4V_a - 2V_b + 7V_c = 36 \quad \text{--- (iii)}$$

Solving (i), (ii) & (iii) —

$$V_a = 10V$$

$$V_b = 4.933V$$

$$V_c = 12.267V$$

Here, $V_{3A} = \pm(V_a - V_c)$ \pm because no polarity specified

$$= \pm 2.267V$$


Here $P_{3A} = \pm V_{3A} \times 3$

$$= + (V_a - V_c) \times 3$$

$$= - 2.267 \times 3$$


$$= - 6.8W \quad [\text{Supplying}]$$

Current entering +ve
polarity

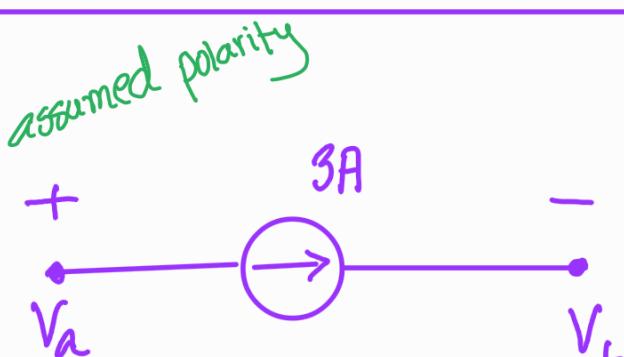

You can consider opposite polarity and still reach the same result.

Problem 9

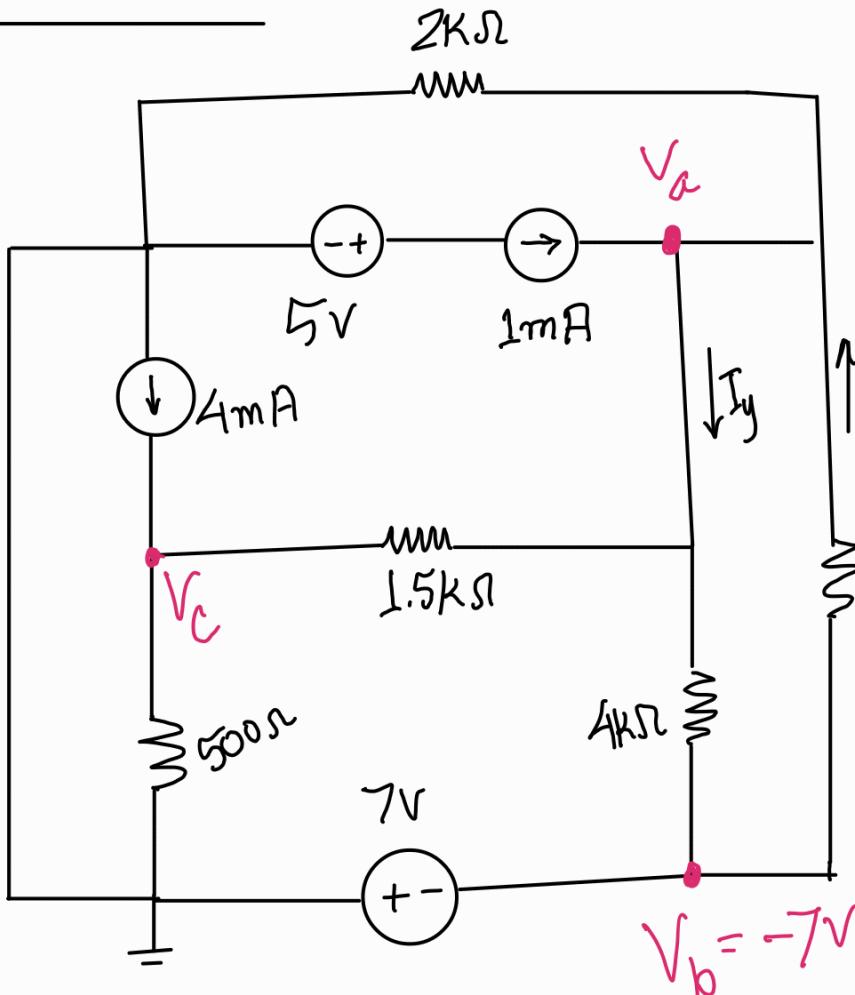

Find I_x & I_y

KCL @ a —

$$-1 + \frac{V_a}{2} + \frac{V_a + 7}{4} \times 2 + \frac{V_a - V_c}{1.5} = 0$$

$4k\Omega$

$$\Rightarrow 3V_a + 3V_a + 21 + 4V_a - 4V_c = 6$$

$$\Rightarrow 10V_a - 4V_c = -15 \quad \textcircled{i}$$

KCL @ c —

$$\therefore I_x = \frac{-7 - V_a}{4}$$

$$-4 + \frac{V_c}{0.5} + \frac{V_c - V_a}{1.5} = 0$$

$$= \frac{-7 + 1}{4}$$

$$= -1.5 \text{ mA}$$

$$\Rightarrow -12 + 6V_c + 2V_c - 2V_a = 0$$

$$\Rightarrow -2V_a + 8V_c = 12 \quad \textcircled{ii}$$

KCL @ a —

$$I_y = 1 - 1.5 + \frac{-V_a}{2}$$

$$= 0 \text{ mA}$$

Solving \textcircled{i} and \textcircled{ii} —


$$V_a = -1V$$

$$V_c = 1.25V$$

Note — make sure units are consistent

If resistances are in $k\Omega$ and voltages are in V , current will be in mA

Problem 10

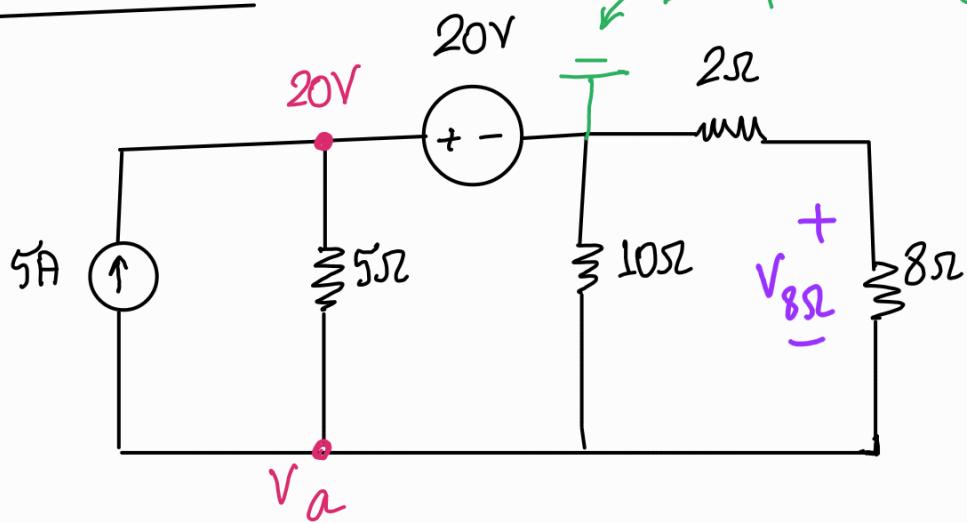

Find voltage across the 8Ω resistor

KCL @ a —

$$5 + \frac{V_a - 20}{5} + \frac{V_a}{10} + \frac{V_a}{10} = 0$$

$$\Rightarrow \frac{2V_a - 20}{5} = -5$$

$$\Rightarrow 2V_a = -25 + 20$$

$$\Rightarrow V_a = -2.5 \text{ V}$$

Applying voltage divider —

$$V_{8\Omega} = \frac{0 - V_a}{10} \times 8$$


$$= \frac{2.5}{5} \times 4$$

$$= 2 \text{ V}$$

but since polarity isn't mentioned,

$$V_{8\Omega} = \pm 2 \text{ V}$$

Problem 11

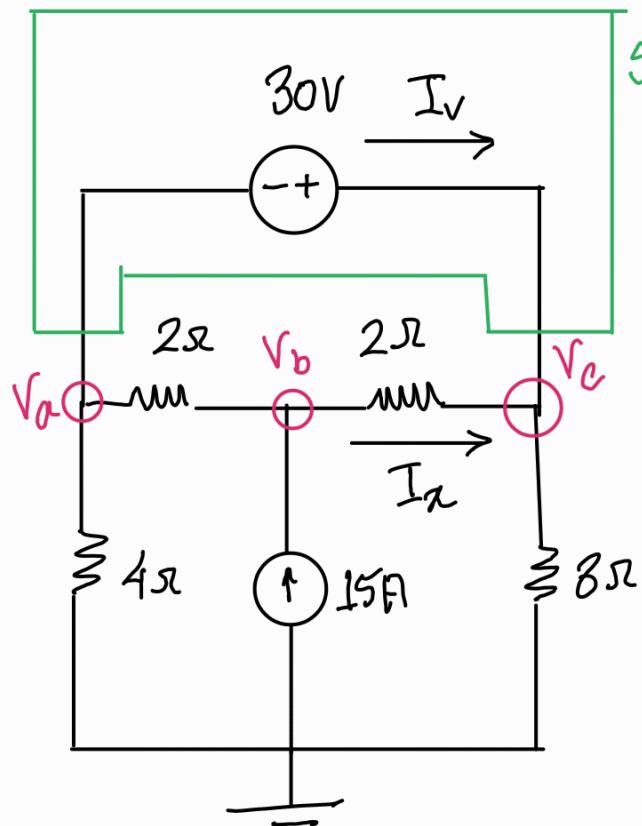

Supernode 1

Find I_a and I_v using nodal analysis.

@ Supernode 1 —

$$V_a - V_b = -30 \quad \text{--- (i)}$$

$$\& \frac{V_a}{4} + \frac{V_a - V_b}{2} + \frac{V_c - V_b}{2} + \frac{V_c}{8} = 0$$

Solving (i), (ii), (iii) —

$$V_a = 30V$$

$$V_b = 60V$$

$$V_c = 60V$$

$$I_a = \frac{V_b - V_c}{2}$$

$$= 0A$$

@ C —

$$I_v + I_a = \frac{V_c}{8}$$

$$\Rightarrow I_v = \frac{60}{8} = 7.5A$$

$$\Rightarrow 2V_a + 4V_a - 4V_b + 4V_c - 4V_b + V_c = 0$$


$$\Rightarrow 6V_a - 8V_b + 5V_c = 0 \quad \text{--- (ii)}$$

KCL @ b —

$$\frac{V_b - V_a}{2} + \frac{V_b - V_c}{2} = 15$$

$$\Rightarrow -V_a + 2V_b - V_c = 30 \quad \text{--- (iii)}$$

Problem 12

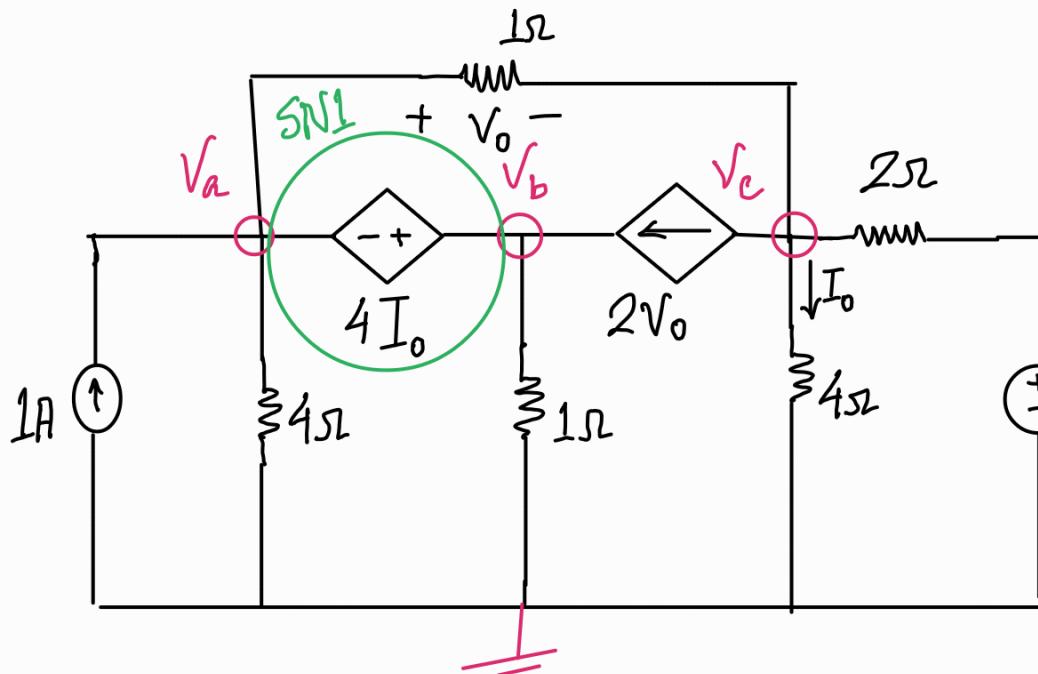

Use nodal analysis to find current through the dependent voltage source

Voltage relation @ Supernode 1 (SN1) —

$$V_a - V_b = -4I_o$$

$$\Rightarrow V_a - V_b = -V_c \quad [\text{From } ①]$$

$$\Rightarrow V_a - V_b + V_c = 0 \quad ①$$

$$I_o = \frac{V_c}{4} \quad ①$$

$$V_o = V_a - V_c \quad ②$$

KCL @ SN1 —

$$-1 + \frac{V_a - V_c}{1} + \frac{V_a}{4} - 2V_o + \frac{V_b}{1} = 0$$

$$\Rightarrow -4 + 4V_a - 4V_c + V_a - 8V_o + 4V_b = 0$$

$$\Rightarrow 5V_a + 4V_b - 4V_c - 8V_o = 4$$

$$\Rightarrow 5V_a + 4V_b - 4V_c - 8V_o + 8V_c = 4 \quad [\text{From } ②]$$

$$\Rightarrow -3V_a + 4V_b + 4V_c = 4 \quad \text{--- (ii)}$$

KCL @ C —

$$2V_0 + \frac{V_c - V_a}{1} + \frac{V_c}{4} + \frac{V_c - 10}{2} = 0$$

$$\Rightarrow 8V_0 + 4V_c - 4V_a + V_c + 2V_c - 20 = 0$$

$$\Rightarrow -4V_a + 7V_c + 8V_0 = 20$$

$$\Rightarrow -4V_a + 7V_c + 8V_a - 8V_c = 20$$

$$\Rightarrow 4V_a - V_c = 20 \quad \text{--- (iii)}$$

Solving (i), (ii) & (iii) —

$$V_a = 4.97V$$

$$V_b = 4.85V$$

$$V_c = -0.12V$$

Current through $4I_0$ — KCL @ b —


$$2V_0 - V_b = \pm I_{4I_0}$$

$$\begin{aligned} \Rightarrow \pm I_{4I_0} &= 2V_a - 2V_c - V_b \\ &= 5.33A \end{aligned}$$

$$\Rightarrow I_{4I_0} = \pm 5.33A$$

↑ direction not specified

Problem 13

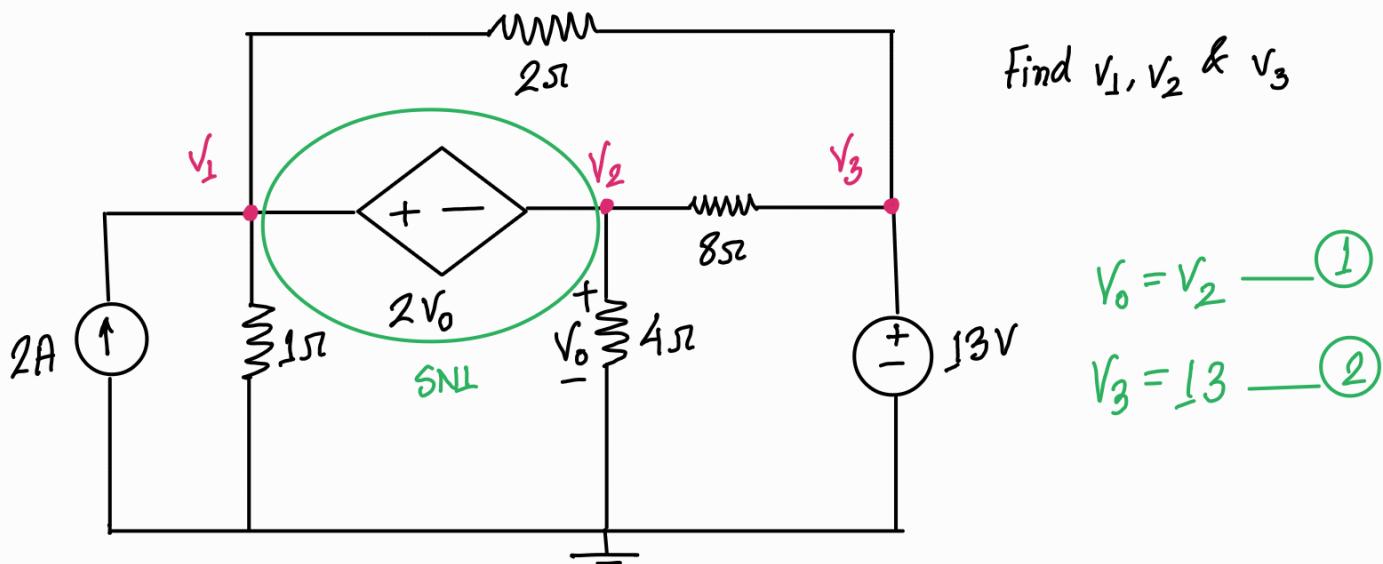

$$V_0 = V_2 \quad \text{--- (1)}$$

$$V_3 = 13 \quad \text{--- (2)}$$

Voltage relation at SN1 —

$$V_1 - V_2 = 2V_0$$

$$\Rightarrow V_1 - 3V_2 = 0 \quad \text{--- (i) [From (1)]}$$

KCL @ SN1 —

$$-2 + \frac{V_1}{1} + \frac{V_1 - 13}{2} + \frac{V_2}{4} + \frac{V_2 - 13}{8} = 0$$

$$\Rightarrow 8V_1 + 4V_1 - 52 + 2V_2 + V_2 - 13 = 16$$


$$\Rightarrow 12V_1 + 3V_2 = 81 \quad \text{--- (ii)}$$

Solving (i) & (ii) —

$$V_1 = 6.23V$$

$$V_2 = 2.08V$$

Problem 14

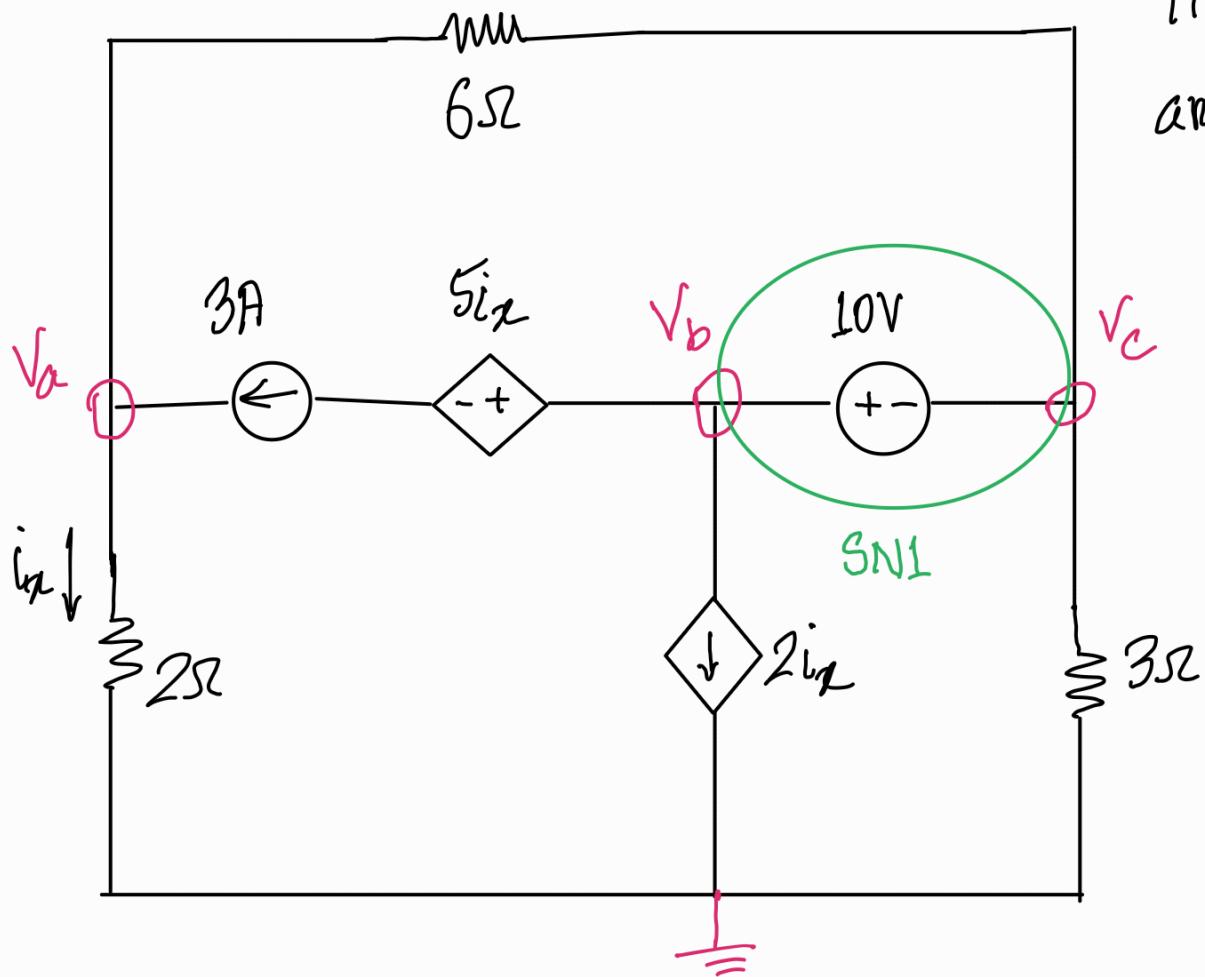

Find i_x , V_{2i_x} ,
and i_{20V}

KCL @ a —

$$i_x = \frac{V_a}{2} \quad \text{--- (1)}$$

$$\frac{V_a}{2} - 3 + \frac{V_a - V_c}{6} = 0$$

$$\Rightarrow 3V_a - 18 + V_a - V_c = 0$$

$$\Rightarrow 4V_a - V_c = 18 \quad \text{--- (i)}$$

Voltage relation @ SN1 —

$$V_b - V_c = 10 \quad \text{--- (ii)}$$

KCL @ SN1 —

$$3 + 2i_x + \frac{V_c}{3} + \frac{V_c - V_a}{6} = 0$$

$$\Rightarrow 18 + 12i_x + 2V_c + V_c - V_a = 0$$

$$\Rightarrow -V_a + 3V_c + 12i_x = -18$$

$$\Rightarrow 5V_a + 3V_c = -18 \quad [\text{From (1)}] \quad \text{--- (iii)}$$

Solving (i), (ii), (iii) —

$$V_a = 2.12 \text{ V}$$

$$V_b = 0.47 \text{ V}$$

$$V_c = -9.53 \text{ V}$$


$$\therefore i_x = \frac{V_a}{2} = 1.06 \text{ A}$$

$$V_{2i_x} = \pm V_b = \pm 0.47 \text{ V}$$

$$i_{10V} = \pm (3 + 2i_x) = \pm 5.12 \text{ A}$$

no assigned direction/polarity

Problem 15

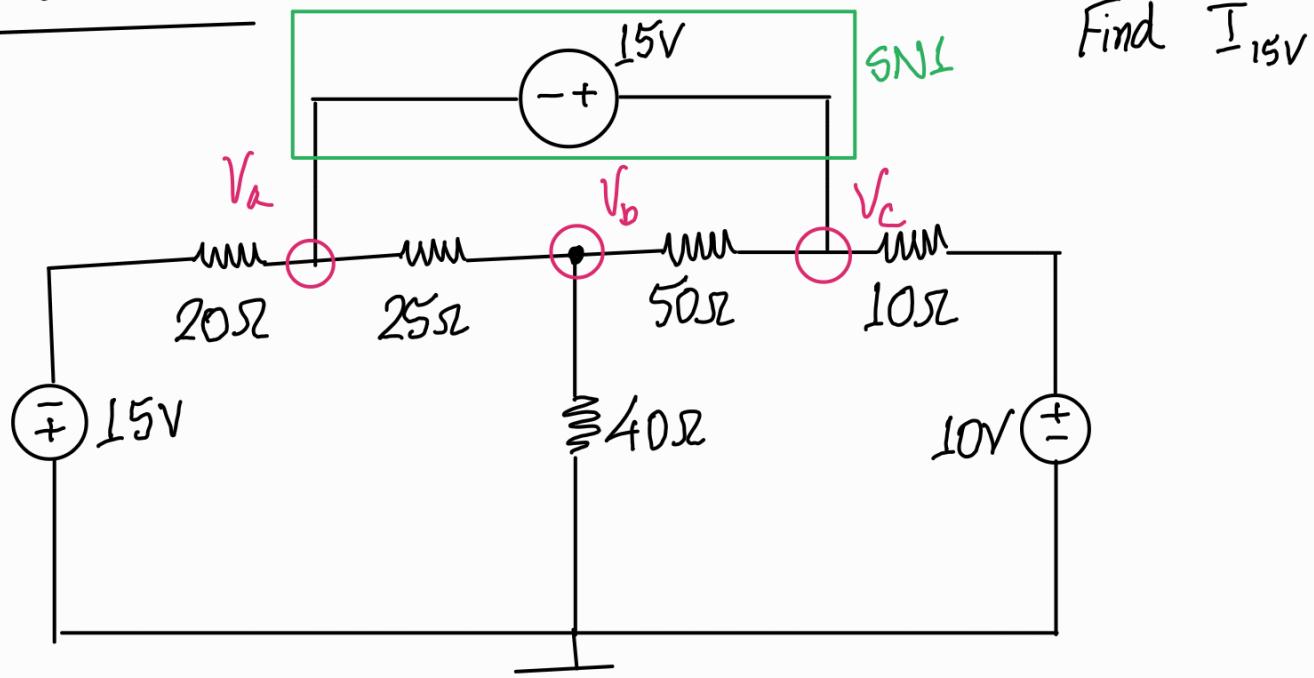

KCL @ SNI —

$$\frac{V_a + 15}{20} + \frac{V_a - V_b}{25} + \frac{V_c - V_b}{50} + \frac{V_c - 10}{10} = 0$$

$$\Rightarrow 5V_a + 75 + 4V_a - 4V_b + 2V_c - 2V_b + 10V_c - 100 = 0$$

$$\Rightarrow 9V_a - 6V_b + 12V_c = 25 \quad \text{--- (i)}$$

Voltage relation @ SNI —

$$-V_a + V_c = 15 \quad \text{--- (ii)}$$

KCL @ b —

$$\frac{V_b - V_a}{25} + \frac{V_b}{40} + \frac{V_b - V_c}{50} = 0$$

$$\Rightarrow 8V_b - 8V_a + 5V_b + 4V_b - 4V_c = 0$$

$$\Rightarrow -8V_a + 17V_b - 4V_c = 0 \quad \text{--- (iii)}$$

Solving ①, ②, ③ —

$$V_a = -7.982 \text{ V}$$


$$V_b = -2.105 \text{ V}$$

$$V_c = 7.017 \text{ V}$$

$$\therefore I_{ISV} = \pm \left(\frac{V_c - V_b}{50} + \frac{V_c - 10}{10} \right)$$

$$= \pm 0.116 \text{ A}$$

Problem 16

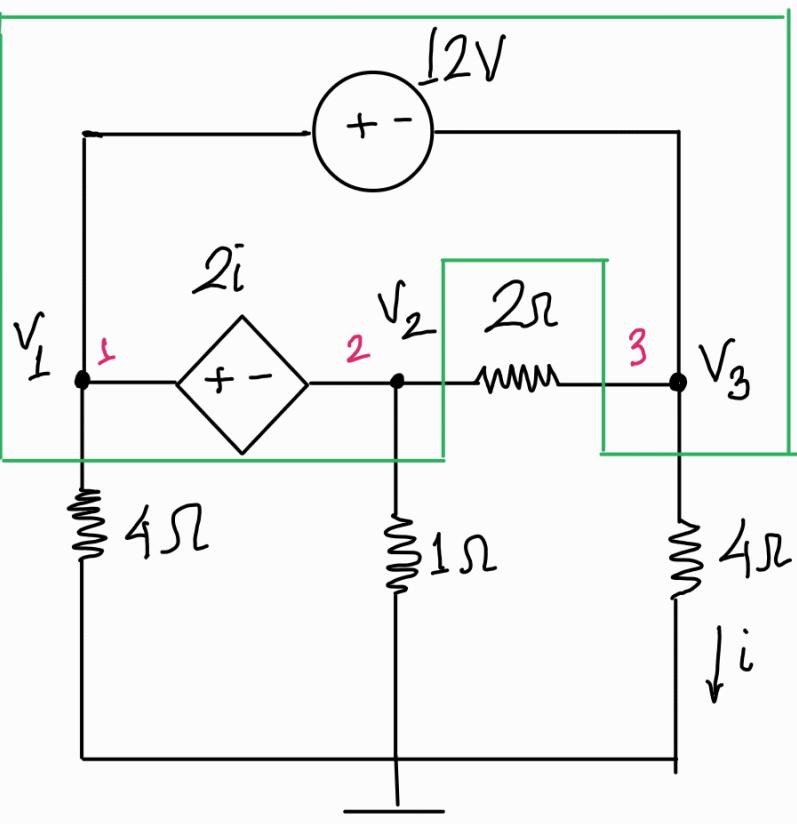

SN1

Find V_1 , V_2 & V_3 . Find current supplied by 12V & $2i$ source.

$$i = \frac{V_3}{4} \quad \text{--- (1)}$$

Voltage relationships at SN1 —

$$V_1 - V_2 = 2i$$

$$\Rightarrow V_1 - V_2 = 2 \cdot \frac{V_3}{4} \quad [\text{From (1)}]$$

$$\Rightarrow 2V_1 - 2V_2 - V_3 = 0 \quad \text{--- (i)}$$

&

$$V_1 - V_3 = 12 \quad \text{--- (ii)}$$

KCL @ SN1 —

$$\frac{V_1}{4} + \frac{V_2}{1} + \frac{V_3}{4} = 0 \quad [2\Omega \text{ is shorted}]$$


$$\Rightarrow V_1 + 4V_2 + V_3 = 0 \quad \text{--- (iii)}$$

Solving (i), (ii) & (iii) —

$$V_1 = -3V$$

$$V_2 = 4.5V$$

$$V_3 = -15V$$

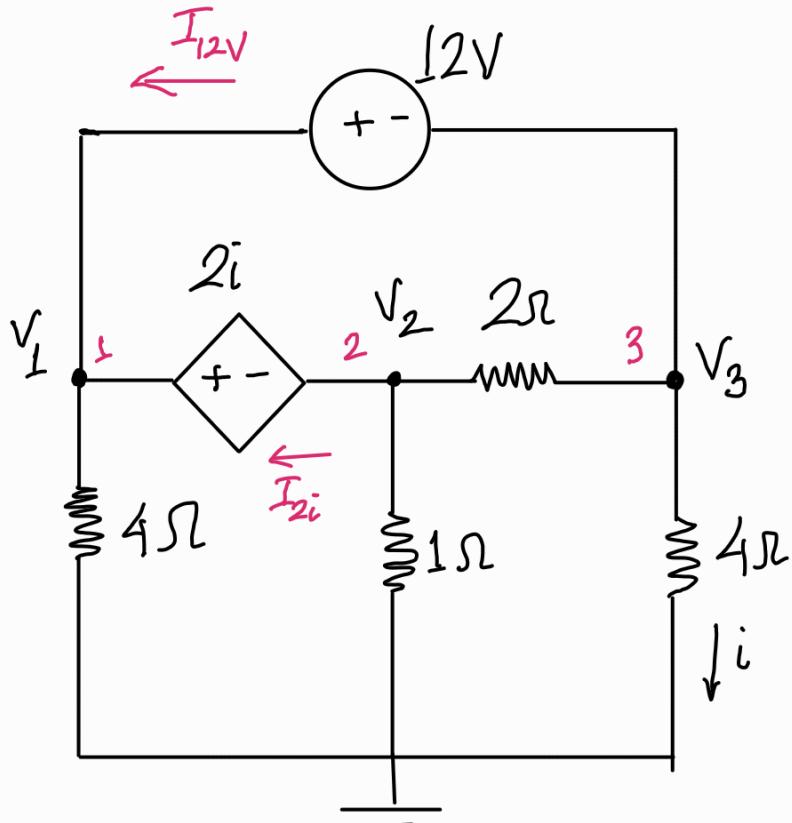

Here, KCL @ 3 —

$$I_{12V} = \frac{V_2 - V_3}{2} + \frac{0 - V_3}{4}$$

$$= 9.75 + 3.75$$

$$= 13.5 \text{ A} \quad (\text{Wrong in slide})$$


KCL @ 1 —

$$I_{2i} + I_{12V} = \frac{V_1}{4}$$

$$\Rightarrow I_{2i} = \frac{-3}{4} - 13.5$$

$$= -14.25 \text{ A}$$

Problem 17

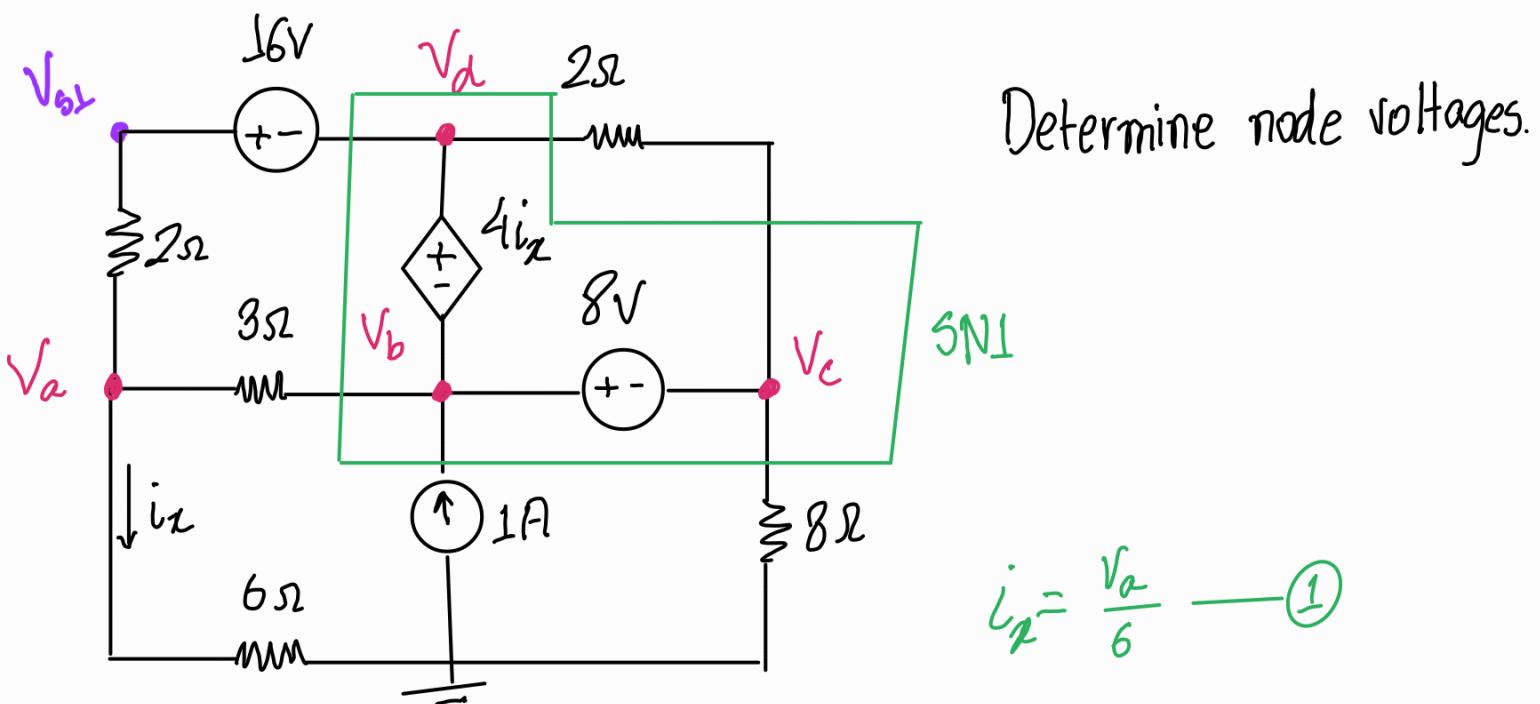

$$i_x = \frac{V_a}{6} \quad \text{--- (1)}$$

Voltage relationships at SN1—

$$V_d - V_b = 4i_x$$

$$\Rightarrow V_d - V_b = \frac{2V_a}{3} \quad [\text{From (1)}]$$

$$\Rightarrow 2V_a + 3V_b - 3V_d = 0 \quad \text{--- (i)}$$

&

$$V_b - V_c = 8 \quad \text{--- (ii)}$$

KCL @ SN1—

$$\frac{V_d + 16 - V_a}{2} + \frac{V_b - V_a}{3} - 1 + \frac{V_c}{8} = 0 \quad [2\Omega \text{ shorted}]$$

$$\Rightarrow 12V_d - 12V_a + 192 + 8V_b - 8V_a - 24 + 8V_c = 0$$

$$\Rightarrow -20V_a + 8V_b + 3V_c + 12V_d = -168 \quad \text{--- (iii)}$$

KCL @ a —

$$\frac{V_a - V_d - 16}{2} + \frac{V_a - V_b}{3} + \frac{V_a}{6} = 0$$

$$\Rightarrow 3V_a - 3V_d - 48 + 2V_a - 2V_b + V_a = 0$$

$$\Rightarrow 6V_a - 2V_b - 3V_d = 48 \quad \text{--- (iv)}$$

Solving (i), (ii), (iii) & (iv) —

$$V_a = 12V$$

$$V_b = 0V$$

$$V_c = -8V$$


$$V_d = 8V$$

$$\therefore V_{S1} = V_d + 16 = 24V$$

If you do not have an EX calculator, replace 1 variable in all equations.

$$\begin{aligned}
 2V_a + 3V_b - 3V_d &= 0 & 2V_a + 3V_c - 3V_d &= -24 \\
 V_b - V_c = 8 &\Rightarrow V_b = 8 + V_c & \\
 -20V_a + 8V_b + 3V_c + 12V_d &= -168 & -20V_a + 11V_c + 12V_d &= -232 \\
 6V_a - 2V_b - 3V_d &= 48 & 6V_a - 2V_c - 3V_d &= 64
 \end{aligned}
 \quad \left. \begin{array}{l} V_a = 12V \\ V_c = -8V \\ V_d = 8V \\ \therefore V_b = 0V \end{array} \right\}$$

Problem 18

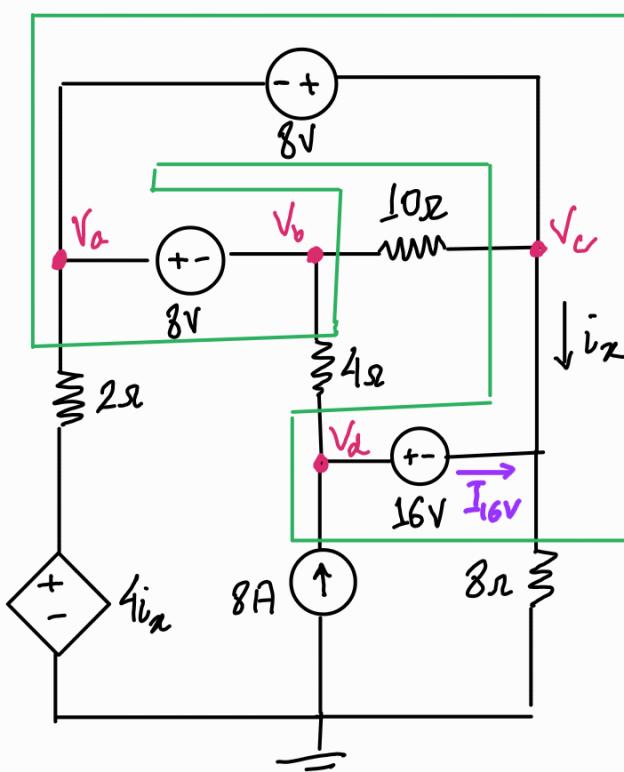

SNI

Determine i_x

Voltage relations @ SNI —

$$V_a - V_b = 8 \quad \text{--- i}$$

$$-V_a + V_c = 8 \quad \text{--- ii}$$

$$-V_c + V_d = 16 \quad \text{--- iii}$$

KCL @ SNI —

$$\frac{V_a - 4i_x}{2} - 8 + \frac{V_c}{8} = 0 \quad [4\Omega \text{ & } 10\Omega \text{ shorted}]$$

$$\Rightarrow 4V_a - 16i_x + V_c = 64$$

$$\Rightarrow 4V_a - 2V_c + 4V_b - 4V_d + 128 + V_c = 64 \quad [\text{From 3}]$$

$$\Rightarrow 4V_a + 4V_b - V_c - 4V_d = -64 \quad \text{--- iv}$$

KCL @ C —

$$i_x + I_{16V} = \frac{V_c}{8} \quad \text{--- 1}$$

KCL @ d —

$$8 + \frac{V_b - V_d}{4} = I_{16V} \quad \text{--- 2}$$

$$\therefore \text{--- 1} \rightarrow i_x = \frac{V_c}{8} - \frac{V_b - V_d}{4} - 8 \quad \text{--- 3}$$

Solving i, ii, iii, iv —

$$V_a = 24V$$

$$V_b = 16V$$

$$V_c = 32V$$

$$V_d = 48V$$

$$\therefore i_a = \frac{V_c}{8} - \frac{V_b - V_d}{4} - 8$$

$$= \frac{32}{8} - \frac{16 - 48}{4} - 8$$

$$= 4 - 4 + 12 - 8$$

$$= 4A$$