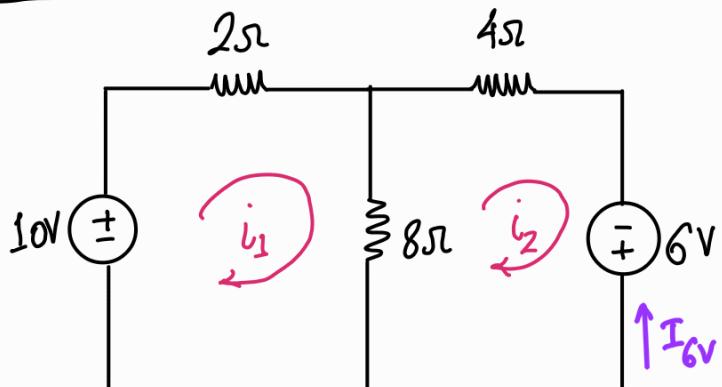


### Problem 1



Determine current absorbed by the 6V source.

KVL @ 1 —

$$-10 + 10i_1 - 8i_2 = 0$$

$$\Rightarrow 5i_1 - 8i_2 = 5 \quad \textcircled{i}$$

KVL @ 2 —

$$-8i_1 + 12i_2 = 6$$

$$\Rightarrow -4i_1 + 6i_2 = 3 \quad \textcircled{ii}$$


Solving  $\textcircled{i}$  &  $\textcircled{ii}$

$$i_1 = 3A$$

$$i_2 = 2.5A$$

$$\therefore I_{6v} = -i_2 = -2.5A$$

## Problem 2

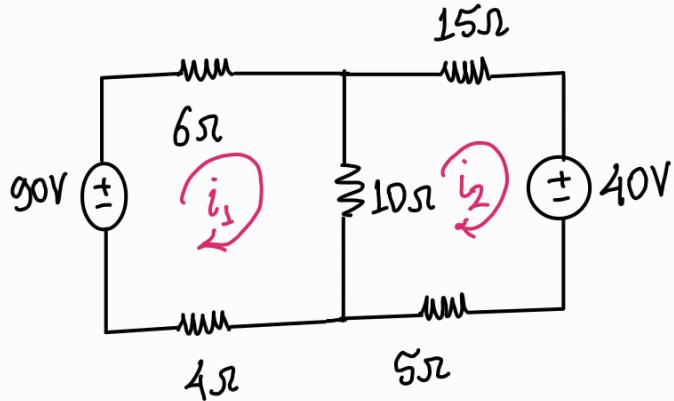

Calculate current through the  $10\Omega$  resistor.

KVL @ 1 —

$$20i_1 - 10i_2 = 90$$

$$\Rightarrow 2i_1 - i_2 = 9 \quad \textcircled{i}$$

KVL @ 2 —

$$-10i_1 + 30i_2 = -40$$

$$\Rightarrow -i_1 + 3i_2 = -4 \quad \textcircled{ii}$$

Solving  $\textcircled{i}$  &  $\textcircled{ii}$  —

$$i_1 = 4.6A$$


$$i_2 = 0.2A$$

no assigned direction

$$\therefore I_{10\Omega} = \pm (i_1 - i_2)$$

$$= \pm 4.4A$$

### Problem 3

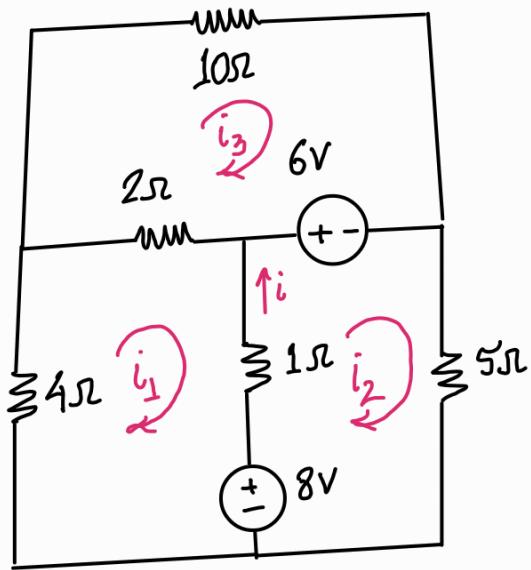

Calculate current  $i$

KVL @ 1 —

$$-i_1 - i_2 - 2i_3 = -8 \quad \textcircled{i}$$

KVL @ 2 —

$$-i_1 + 6i_2 = 2 \quad \textcircled{ii}$$

KVL @ 3 —

$$-2i_1 + 12i_3 = 6$$

$$\Rightarrow -i_1 + 6i_3 = 3 \quad \textcircled{iii}$$

Solving  $\textcircled{i}$ ,  $\textcircled{ii}$  &  $\textcircled{iii}$  —


$$i_1 = -1.026 \text{ A}$$

$$i_2 = 0.162 \text{ A}$$

$$i_3 = 0.329 \text{ A}$$

$$\begin{aligned} \text{Here, } i &= i_2 - i_1 \\ &= 1.188 \text{ A} \end{aligned}$$

## Problem 4

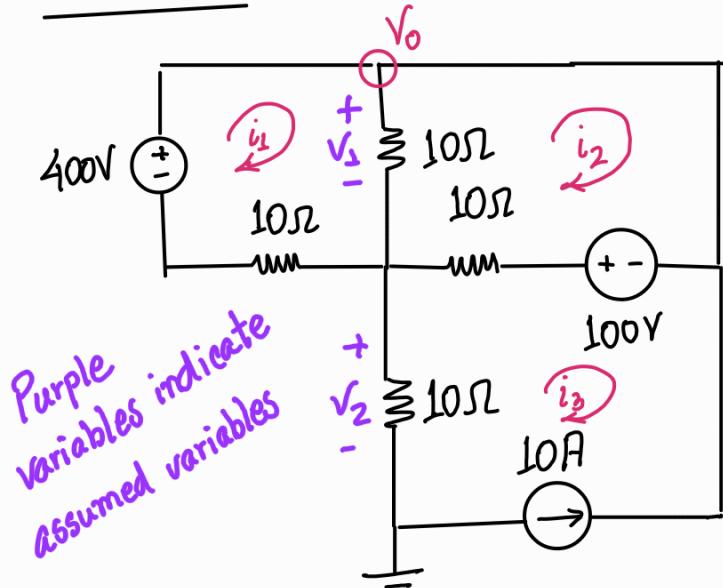

$$V_o = V_1 + V_2$$

$$= (i_1 - i_2) \times 10 + (-i_3) \times 10$$

$$= 233.4 \text{ V}$$

Apply mesh analysis to find  $V_o$

Here,  $i_3 = -10 \text{ A}$

KVL @ 1 —

$$20i_1 - 10i_2 = 400$$

$$\Rightarrow 2i_1 - i_2 = 40 \quad \textcircled{i}$$

KVL @ 2 —

$$-10i_1 + 20i_2 - 10 \times 10 = -100$$


$$\Rightarrow -i_1 + 2i_2 = 0 \quad \textcircled{ii}$$

Solving  $\textcircled{i}$  &  $\textcircled{ii}$  —

$$i_1 = 26.67 \text{ A}$$

$$i_2 = 13.33 \text{ A}$$

### Problem 5

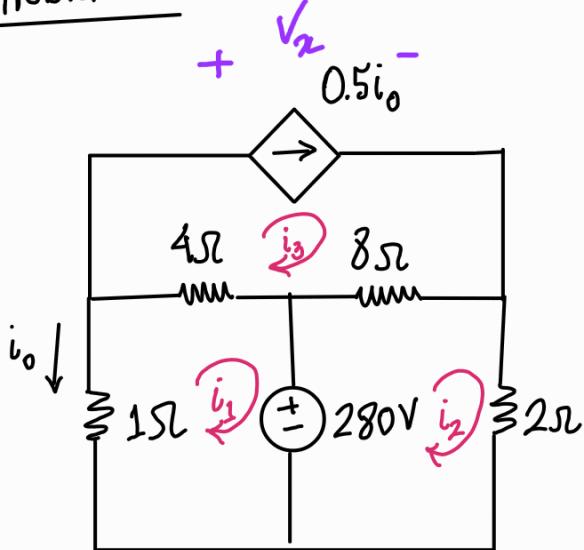

$$i_0 = -i_1 \quad \text{---} \textcircled{1}$$

Find  $i_0$  and the voltage across the  $0.5i_0$  source

$$\text{Here, } i_3 = 0.5 i_0 \Rightarrow 2i_3 = -i_1 \Rightarrow i_1 + 2i_3 = 0 \quad \text{---} \textcircled{1}$$

KVL @ 1 —

$$5i_1 - 4i_3 = -280 \quad \text{---} \textcircled{2}$$

KVL @ 2 —

$$10i_2 - 8i_3 = 280$$

$$\Rightarrow 5i_2 - 4i_3 = 140 \quad \text{---} \textcircled{3}$$

Solving  $\textcircled{1}$ ,  $\textcircled{2}$  &  $\textcircled{3}$  —

$$i_1 = -40 \text{ A}$$

$$i_2 = 44 \text{ A}$$

$$i_3 = 20 \text{ A}$$

KVL @ 3 —


$$V_x + (i_3 - i_2) \times 8 + (i_3 - i_1) \times 4 = 0$$

$$\Rightarrow V_x = -48 \text{ V}$$

But since polarity isn't given,  $V_{0.5i_0} = \pm 48 \text{ V}$

$$\text{and } i_0 = -i_1 = 40 \text{ A}$$

## Problem 6

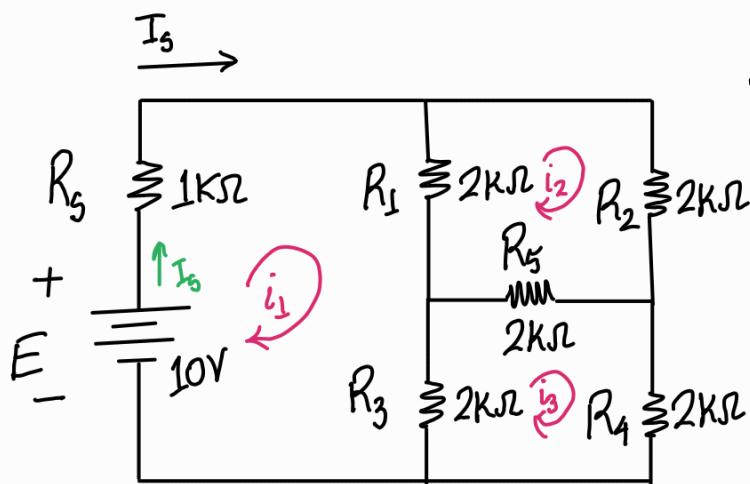

Find  $I_s$ .

KVL @ 1 —

$$5i_1 - 2i_2 - 2i_3 = 10 \quad \textcircled{i}$$

KVL @ 2 —

$$-2i_1 + 6i_2 - 2i_3 = 0$$

$$\Rightarrow -i_1 + 3i_2 - i_3 = 0 \quad \textcircled{ii}$$

KVL @ 3 —

$$-2i_1 - 2i_2 + 6i_3 = 0$$

$$\Rightarrow -i_1 - i_2 + 3i_3 = 0 \quad \textcircled{iii}$$

Solving  $\textcircled{i}, \textcircled{ii} \& \textcircled{iii}$  —


$$i_1 = 3.33 \text{ mA}$$

$$i_2 = 1.67 \text{ mA}$$

$$i_3 = 1.67 \text{ mA}$$

$$\therefore i_s = i_1 = 3.33 \text{ mA}$$

## Problem 7

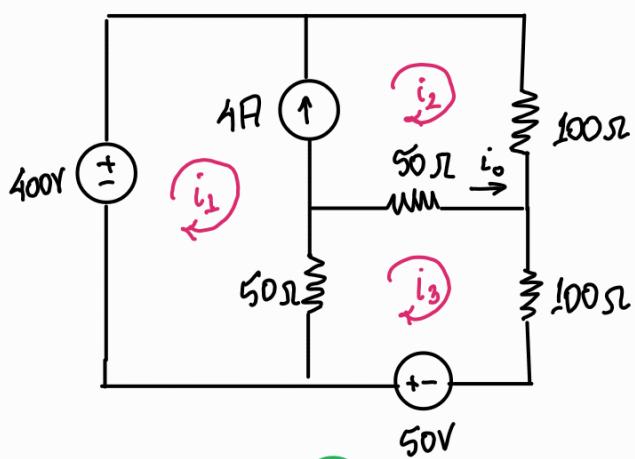

Current relation @ Supermesh 1 & 2 —

$$-i_1 + i_2 = 1 \quad \textcircled{i}$$

KVL @ supermesh 1 & 2 —

$$50i_1 + 150i_2 - 100i_3 = 400$$

$$\Rightarrow i_1 + 3i_2 - 2i_3 = 8 \quad \textcircled{ii}$$

KVL @ 3 —

$$-50i_1 - 50i_2 + 200i_3 = 50$$

$$\Rightarrow -i_1 - i_2 + 4i_3 = 1 \quad \textcircled{iii}$$

Solving  $\textcircled{i}, \textcircled{ii} \& \textcircled{iii}$  —


$$i_1 = -0.5 \text{ A}$$

$$i_2 = 3.5 \text{ A}$$

$$i_3 = 1 \text{ A}$$

$$\therefore i_o = i_3 - i_2 = -2.5 \text{ A}$$

### Problem 8

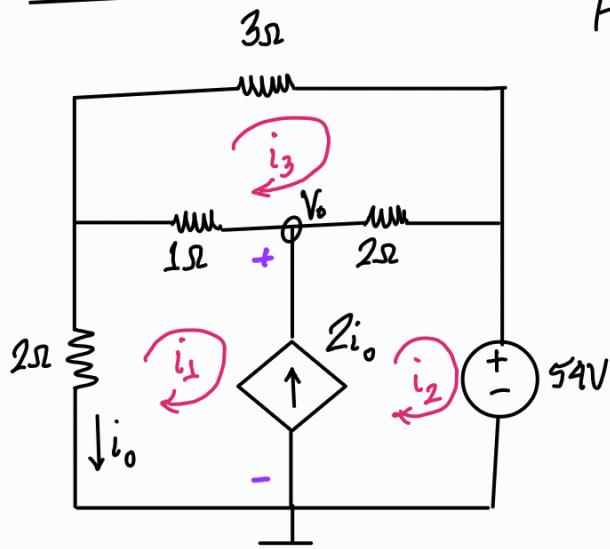

Find  $i_o$  &  $V_o$  using mesh analysis.

Current relationship @ supermesh 1,2 —

$$-i_1 + i_2 = 2i_o \quad \text{--- (i)}$$

$$\text{but } i_o = -i_1$$

$$\therefore \text{(i)} \Rightarrow i_1 + i_2 = 0 \quad \text{--- (ii)}$$

KVL @ supermesh 1,2 —

$$3i_1 + 2i_2 - 3i_3 = -54 \quad \text{--- (iii)}$$


KVL @ 3 —

$$-i_1 - 2i_2 + 6i_3 = 0 \quad \text{--- (iv)}$$

KVL @ 1 —

$$V_o = -3i_1 + i_3 = 114V$$

### Problem 9

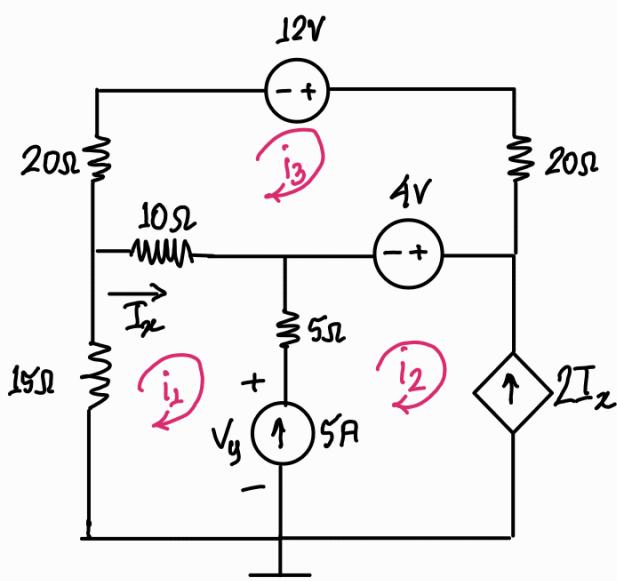

Find  $V_y$  using mesh analysis

@ 2 —

$$-i_2 = 2I_x$$

$$\text{but } I_x = i_1 - i_3$$

$$\therefore -2i_1 - i_2 + 2i_3 = 0 \quad \text{--- (i)}$$

Current relation @ supermesh 1,2 —

$$-i_1 + i_2 = 5 \quad \text{--- (ii)}$$

KVL @ 3 —

$$-10i_1 + 50i_3 = 8 \quad \text{--- (iii)}$$

KVL @ 1 —

$$V_y = -30i_1 + 5i_2 + 10i_3 = 68V$$


Solving (i), (ii) & (iii) —

$$i_1 = -1.8A$$

$$i_2 = 3.2A$$

$$i_3 = -0.2A$$

## Problem 10

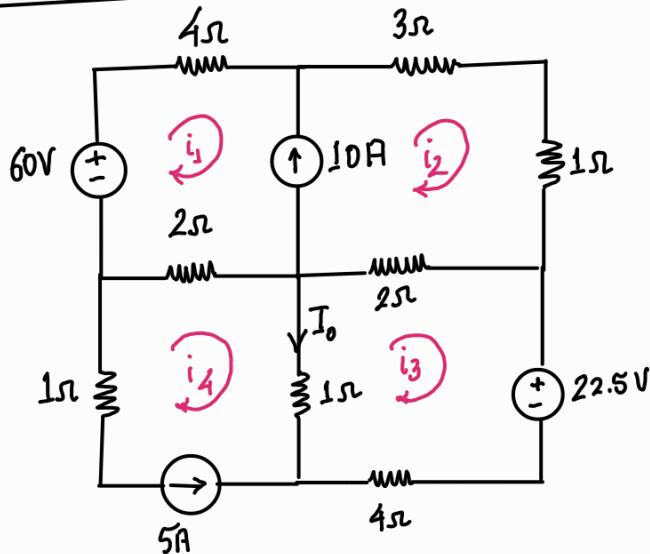

Find  $I_o$  using mesh analysis.

@ 4 —

$$i_4 = -5$$

KVL @ 3 —

$$-2i_2 + 7i_3 - i_4 = -22.5$$

$$\Rightarrow -2i_2 + 7i_3 = -27.5 \quad \text{--- (i)}$$

Current relationship @ supermesh 1,2 —

$$-i_1 + i_2 = 10 \quad \text{--- (ii)}$$

KVL @ supermesh 1,2 —

$$6i_1 + 6i_2 - 2i_3 - 2i_4 = 60$$

$$\Rightarrow 3i_1 + 3i_2 - i_3 = 25 \quad \text{--- (iii)}$$

Solving (i), (ii) & (iii) —


$$i_1 = -1.0625 \text{ A}$$

$$i_2 = 8.9375 \text{ A}$$

$$i_3 = -1.375 \text{ A}$$

$$\text{here, } I_o = i_4 - i_3 = -3.625 \text{ A}$$

## Problem 11

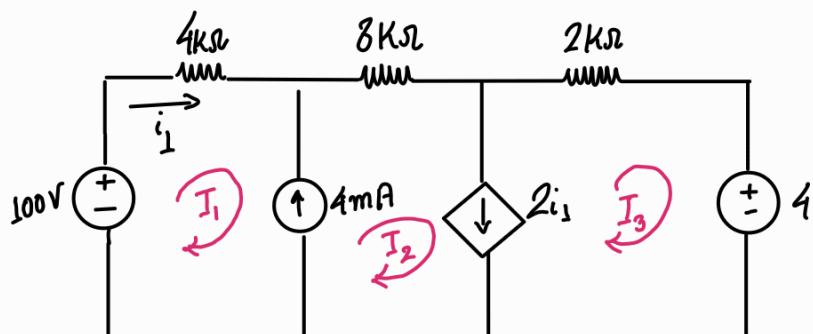

Find the mesh currents

Current relations @ supermesh 1,2,3 —

$$-I_1 + I_2 = 4 \quad \text{--- (i)}$$

$$\& I_2 - I_3 = 2i_1$$

$$\text{but } i_1 = I_1$$

$$\therefore -2I_1 + I_2 - I_3 = 0 \quad \text{--- (ii)}$$

KVL @ supermesh 1,2,3 —

$$4I_1 + 8I_2 + 2I_3 + 40 - 100 = 0$$

$$\Rightarrow 2I_1 + 4I_2 + I_3 = 30 \quad \text{--- (iii)}$$


Solving (i), (ii), (iii) —

$$I_1 = 2 \text{ mA}$$

$$I_2 = 6 \text{ mA}$$

$$I_3 = 2 \text{ mA}$$


## Problem 12

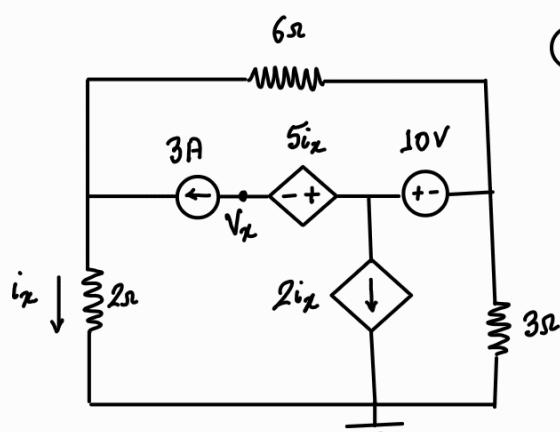

- (i) Use nodal analysis to find the voltage across the 3A source &  $i_x$
- (ii) Use mesh analysis to find  $V_a$  &  $i_x$

Answer—

Nodal analysis—

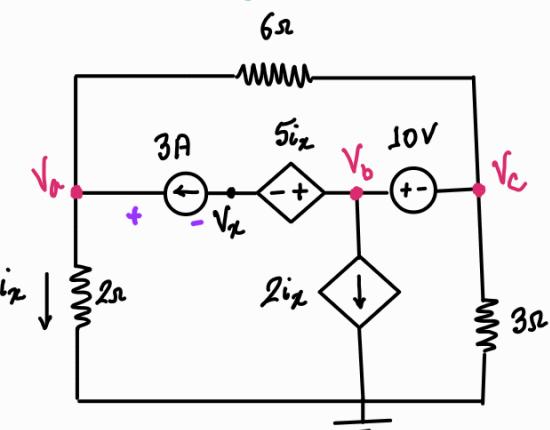

KCL @ a—

$$V_a(2^{-1} + 6^{-1}) - V_c(6^{-1}) = 3 \quad \textcircled{i}$$

Voltage relationship @ supernode b,c —

$$V_b - V_c = 10 \quad \textcircled{ii}$$

KCL @ supernode b,c —

$$3 + 2i_x + V_c(6^{-1} + 3^{-1}) - V_a(6^{-1}) = 0$$

$$\text{but } i_x = V_a \cdot 2^{-1}$$


$$\therefore 3 + V_a(1 - 6^{-1}) + V_c(6^{-1} + 3^{-1}) = 0$$

$$\Rightarrow V_a(1 - 6^{-1}) + V_c(6^{-1} + 3^{-1}) = -3 \quad \textcircled{iii}$$

Solving  $\textcircled{i}$ ,  $\textcircled{ii}$  &  $\textcircled{iii}$  —

$$V_a = 2.1176V \quad V_b = 0.1706V \quad V_c = -9.529V$$

Mesh analysis —

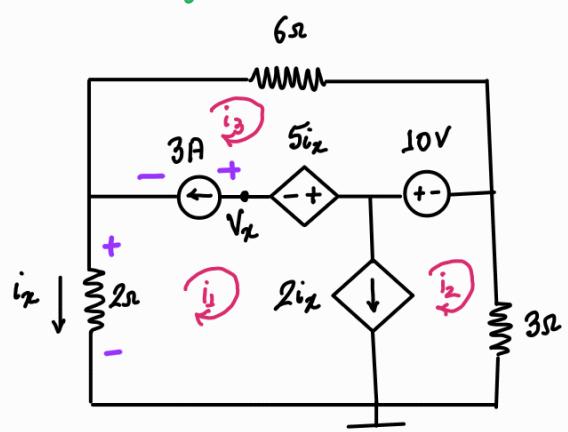

Current relationships @ supermesh 1,2,3 —

$$-i_1 + i_3 = 3 \quad \textcircled{i}$$

$$\& i_1 - i_2 = 2i_x$$

$$\text{but } i_x = -i_1$$

$$\therefore 3i_1 - i_2 = 0 \quad \textcircled{ii}$$

KVL @ supermesh 1,2,3 —

$$2i_1 + 3i_2 + 6i_3 = 0 \quad \textcircled{iii}$$

Solving  $\textcircled{i}$ ,  $\textcircled{ii}$  &  $\textcircled{iii}$  —

$$i_1 = -1.059A \quad i_2 = -3.176A \quad i_3 = 1.941A$$

$$i_x = \frac{V_a}{2} = 1.059 A$$

$$\& V_{3A} = \pm (V_a - V_b + 5i_x) \\ = \pm 6.942 V \text{ (close enough)}$$

and  $V_x = -4.823 V$  (close enough)

Answer wrong in slide

$$i_x = -i_1 = 1.059 A$$

$$V_x = V_{2A} + V_{3A}$$

$$= 2i_x + V_{3A}$$


KVL @ 3 —

$$6i_3 - 10 + 5i_x + V_{3A} = 0$$

$$\therefore V_{3A} = -6.941 V \text{ (± because no assigned polarity)}$$

$$\therefore V_x = -4.823 V$$

### Problem 13

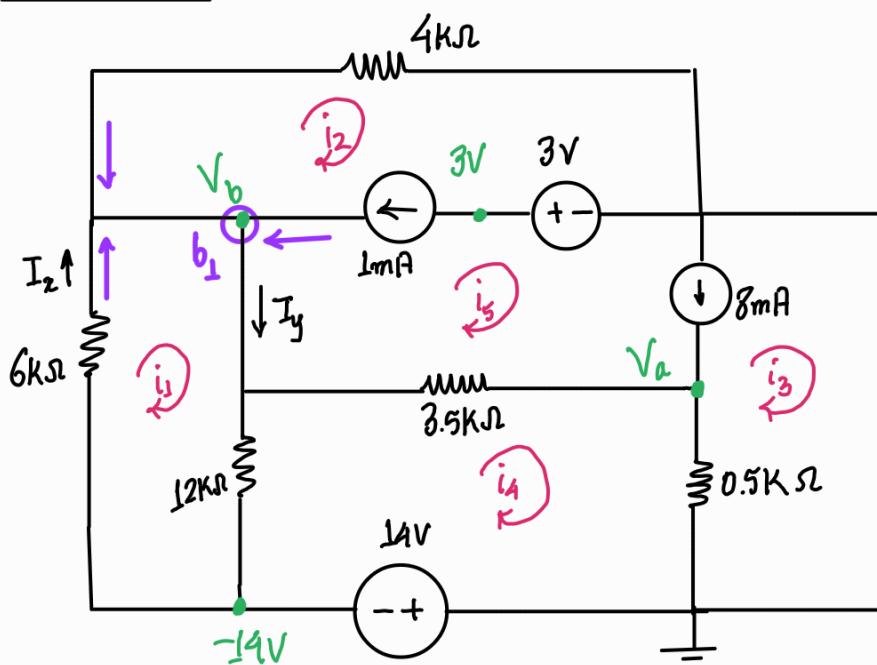

Nodal analysis —

KCL @ a —

$$V_a(0.5^{-1} + 3.5^{-1}) - V_b(3.5^{-1}) = 8 \quad \textcircled{i}$$

KCL @ b —

$$-V_a(3.5^{-1}) + V_b(4^{-1} + 3.5^{-1} + 6^{-1} + 12^{-1}) = 1 - 14(6^{-1} + 12^{-1}) \quad \textcircled{ii}$$

Find  $I_x$  &  $I_y$  using both nodal and mesh analysis

Mesh analysis —

Current relations @ supermesh 2,5,3 —

$$i_2 - i_5 = 1 \quad \textcircled{i}$$

$$\& -i_3 + i_5 = 8 \quad \textcircled{ii}$$

KVL @ supermesh 2,5,3 —

$$4i_2 + 0.5i_3 - 4i_1 + 3.5i_5 = 0 \quad \textcircled{iii}$$

KVL @ 4 —

$$-12i_1 - 0.5i_3 + 16i_4 - 3.5i_5 = -14 \quad \textcircled{iv}$$

KVL @ 1 —

$$18i_1 - 12i_4 = 0 \quad \textcircled{v}$$

$$\text{from } \textcircled{i} \rightarrow i_2 = 1 + i_5$$

$$\therefore \textcircled{ii} \rightarrow -i_3 + i_5 = 8 \quad \textcircled{1}$$

Solving ① & ② —

$$V_a = 3.25V$$

$$V_b = -2V$$

$$\therefore I_x = -\frac{-2 - (-14)}{6} \\ = -2mA$$

applying KCL @ b<sub>1</sub> —

$$I_x + 1 - \frac{V_b}{4} = I_y \Rightarrow -2 + 1 + \frac{2}{4} = I_y \\ \Rightarrow I_y = -0.5mA$$

Note — Don't do  $I_y = \frac{V_b - (-14)}{12}$

$$\textcircled{iii} \rightarrow 0.5i_3 - 4i_4 + 7.5i_5 = -4 \quad \textcircled{2}$$

$$\textcircled{iv} \rightarrow -12i_1 - 0.5i_3 + 16i_4 - 3.5i_5 = -14 \quad \textcircled{3}$$

$$\textcircled{v} \rightarrow 18i_1 - 12i_4 = 0 \quad \textcircled{4}$$

Solving ①, ②, ③ & ④ —

$$i_1 = -2mA$$

$$i_3 = -9.5mA$$

$$i_4 = -3mA$$


$$i_5 = -1.5mA$$

$$\therefore i_2 = -0.5mA$$

$$I_x = i_1 = -2mA \quad \& \quad I_y = i_1 - i_5 = -0.5mA$$

P.S. — here mesh analysis was not feasible

## Problem 14

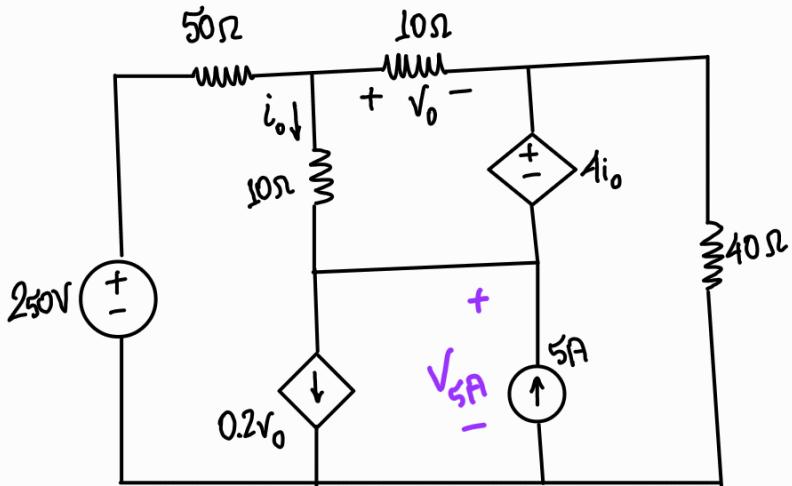

Use mesh analysis to determine  $v_0$  &  $i_0$ .  
What is voltage across the 5A source?

Current relation @ supermesh 1,2 —

$$i_1 - i_2 = 0.2v_0 - 5$$

$$\text{but } v_0 = 10i_3$$

$$\therefore i_1 - i_2 - 2i_3 = -5 \quad \textcircled{i}$$

KVL @ supermesh 1,2 —

$$60i_1 + 40i_2 - 10i_3 - 4i_0 = 250$$

$$\text{but } i_0 = i_1 - i_3$$

$$\therefore 60i_1 + 40i_2 - 10i_3 - 4i_1 + 4i_3 = 250$$

$$\Rightarrow 56i_1 + 40i_2 - 6i_3 = 250 \quad \textcircled{ii}$$

KVL @ 3 —

$$-10i_1 + 20i_3 + 4i_0 = 0$$

$$\text{but } i_0 = i_1 - i_3$$


$$\therefore -6i_1 + 16i_3 = 0 \quad \textcircled{iii}$$

Solving  $\textcircled{i}$ ,  $\textcircled{ii}$  &  $\textcircled{iii}$  —

$$i_1 = 0.7843 \text{ A}$$

$$i_2 = 5.196 \text{ A}$$

$$i_3 = 0.294 \text{ A}$$

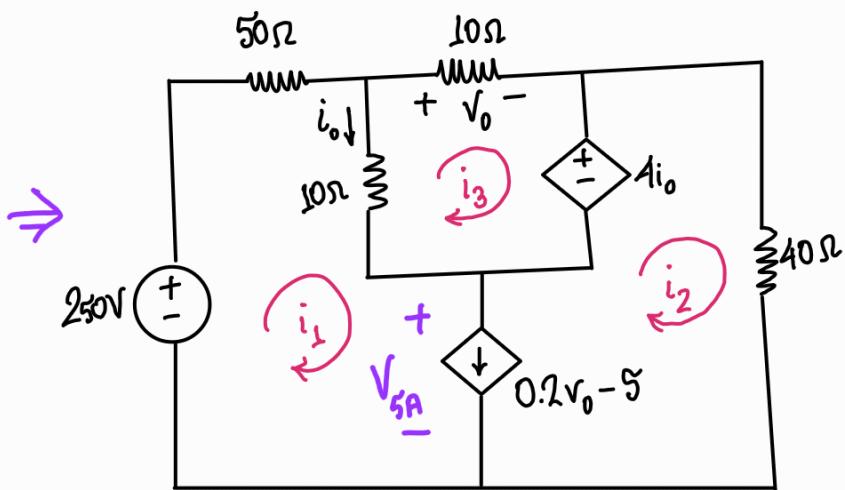

$$\therefore i_0 = i_1 - i_3 = 0.49 \text{ A}$$

$$\& v_0 = 10i_3 = 2.94 \text{ V}$$

KVL @ 1 —

$$60i_1 - 10i_3 + V_{5A} = 250$$


$$\therefore V_{5A} = 205.88 \text{ V}$$

but since polarity isn't defined,

$$V_{5A} = \pm 205.88 \text{ V}$$

P.S. — Do not combine circuits if your manipulation leads you to lose info crucial to solving the actual problem.

### Problem 15

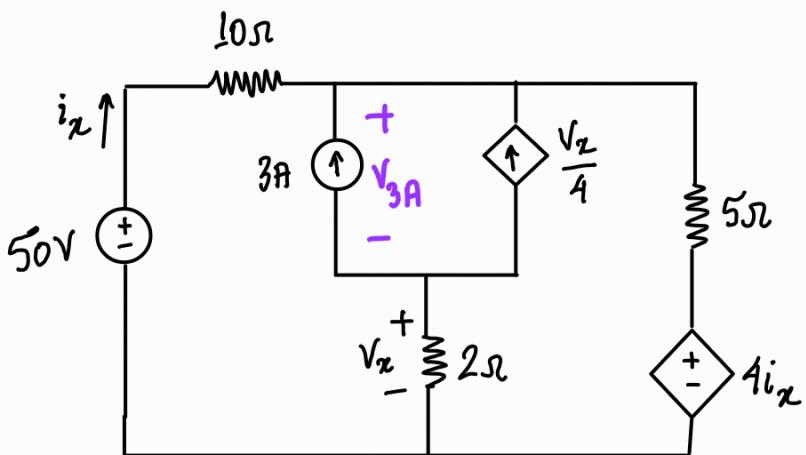

Use mesh analysis to determine  $V_x$  &  $i_x$ . What is the voltage across the 3A source?

Current relation @ supermesh 1,2 —

$$-i_1 + i_2 = 3 + \frac{V_x}{4}$$

$$\text{but } V_x = (i_1 - i_2) \times 2$$

$$\therefore -i_1 + i_2 = 3 + 0.5i_1 - 0.5i_2$$

$$\Rightarrow -1.5i_1 + 1.5i_2 = 3 \quad \text{--- (i)}$$

KVL @ supermesh 1,2 —

$$10i_1 + 5i_2 + 4i_x = 50$$


$$\text{but } i_x = i_1$$

$$\therefore 14i_1 + 5i_2 = 50 \quad \text{--- (ii)}$$

Solving (i) & (ii) —

$$i_1 = 2.105 \text{ A}$$

$$i_2 = 4.105 \text{ A}$$

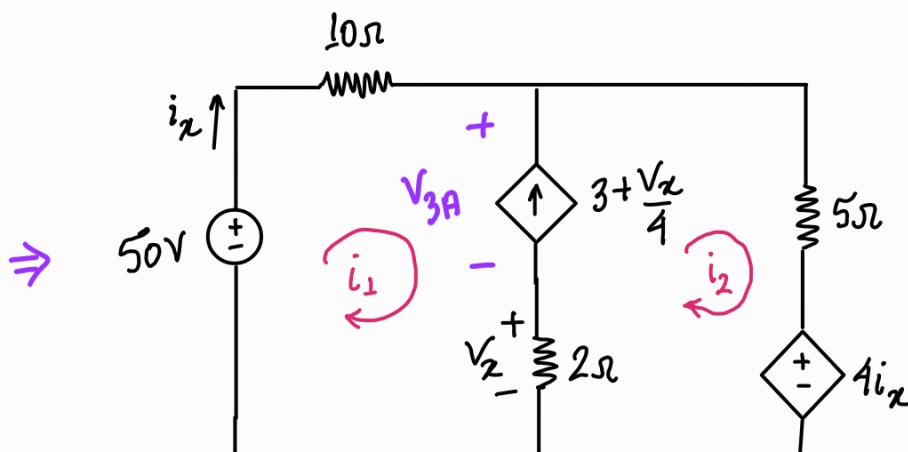

$$\therefore i_x = i_1 = 2.105 \text{ A}$$

$$V_x = (i_1 - i_2) \times 2 = -4 \text{ V}$$


KVL @ I —

$$10i_1 + V_{3A} + V_x = 50$$

$$\Rightarrow V_{3A} = 32.95 \text{ V}$$

but since polarity wasn't assigned,  $V_{3A} = \pm 32.95 \text{ V}$

### Problem 16

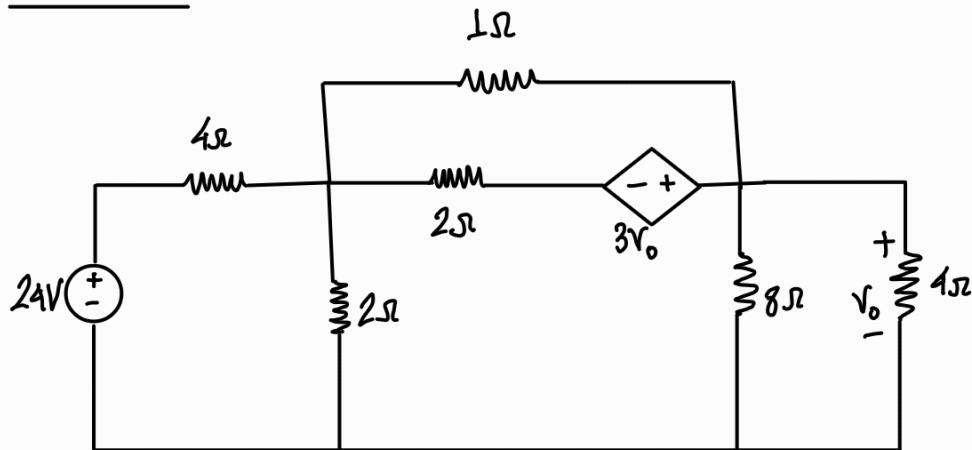


Which method of analysis will be more convenient for solving this ckt? Derive the equations for the convenient method.

$$\text{number of essential nodes} = 3 \quad \therefore \text{nodal equations} = n-1 = 2$$

$$\text{number of meshes} = 4 \quad \therefore \text{mesh equations} = m = 4$$

$\therefore$  nodal analysis will be more convenient.

Preparing the ckt for nodal analysis —

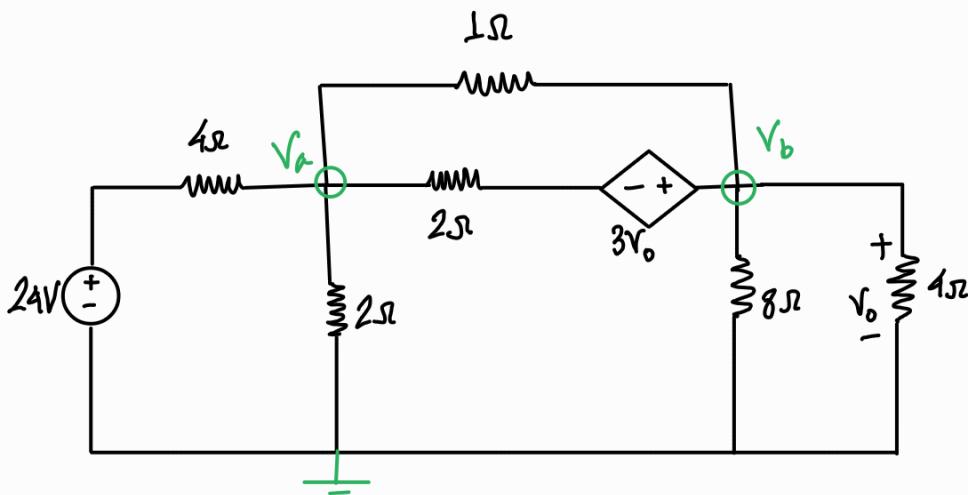

KCL @ a —

$$\frac{V_a - 24}{4} + \frac{V_a - V_b}{1} + \frac{V_a - V_b + 3V_o}{2} + \frac{V_a}{2} = 0$$

$$\Rightarrow V_a \left( \frac{1}{4} + 1^{-1} + 2^{-1} + 2^{-1} \right) - V_b \left( 1^{-1} + 2^{-1} \right) + V_o \left( \frac{3}{2} \right) = 6$$

$$\text{but } V_o = V_b$$

$$\therefore V_a \left( \frac{1}{4} + 1^{-1} + 2^{-1} + 2^{-1} \right) - V_b \left( 1^{-1} + 2^{-1} - \frac{3}{2} \right) = 6 \quad \text{--- (i)}$$

KCL @ b —

$$-V_a (1^{-1} + 2^{-1}) + V_b (1^{-1} + 2^{-1} + 8^{-1} + 1^{-1})$$

$$-\frac{3}{2} V_o = 0$$


$$\Rightarrow -V_a (1^{-1} + 2^{-1}) + V_b (1^{-1} + 2^{-1} + 4^{-1} + 8^{-1} - \frac{3}{2}) = 0$$

Solving (i) & (ii) —

$$V_a = 2.67V$$

$$V_b = 10.67V$$

### Problem 17

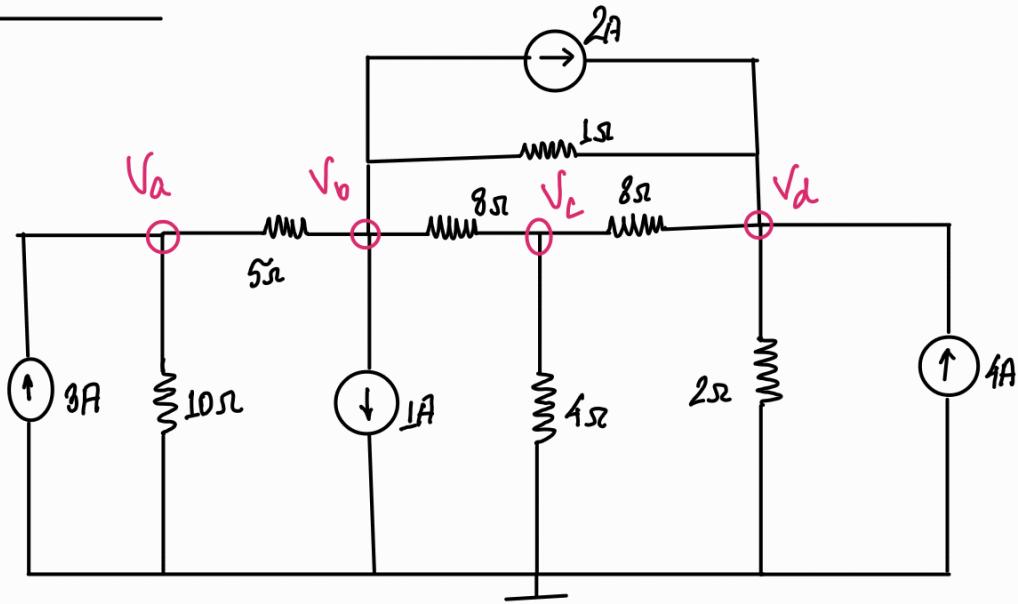

Which method of analysis will be more convenient for solving this ckt? Derive the equation for the convenient method.

# essential nodes (except ground) = 4      ∴ # of equations = 4

# meshes = 7      ∴ # of equations = 7

∴ nodal more convenient

But for mesh analysis you will have 3 mesh current values directly. So, Even when nodal is more convenient based only on numbers, mesh is also feasible. This isn't true for all cases. So maintain caution.

Comment

KCL @ a —

$$V_a(10^{-1} + 5^{-1}) - V_b(5^{-1}) = 3 \quad \text{--- i}$$

KCL @ b —

$$-V_a(5^{-1}) + V_b(5^{-1} + 8^{-1} + 1^{-1}) - V_c(8^{-1}) - V_d(1^{-1}) = -3 \quad \text{--- ii}$$

KCL @ c —


$$-V_b(8^{-1}) + V_c(8^{-1} + 8^{-1} + 4^{-1}) - V_d(8^{-1}) = 0 \quad \text{--- iii}$$

KCL @ d —

$$-V_b(1^{-1}) - V_c(8^{-1}) + V_d(1^{-1} + 8^{-1} + 2^{-1}) = 6 \quad \text{--- iv}$$

Solving i, ii, iii & iv —  $V_a = 13.897V, V_b = 5.845V, V_c = 3.348V, V_d = 7.547V$

## Problem 18

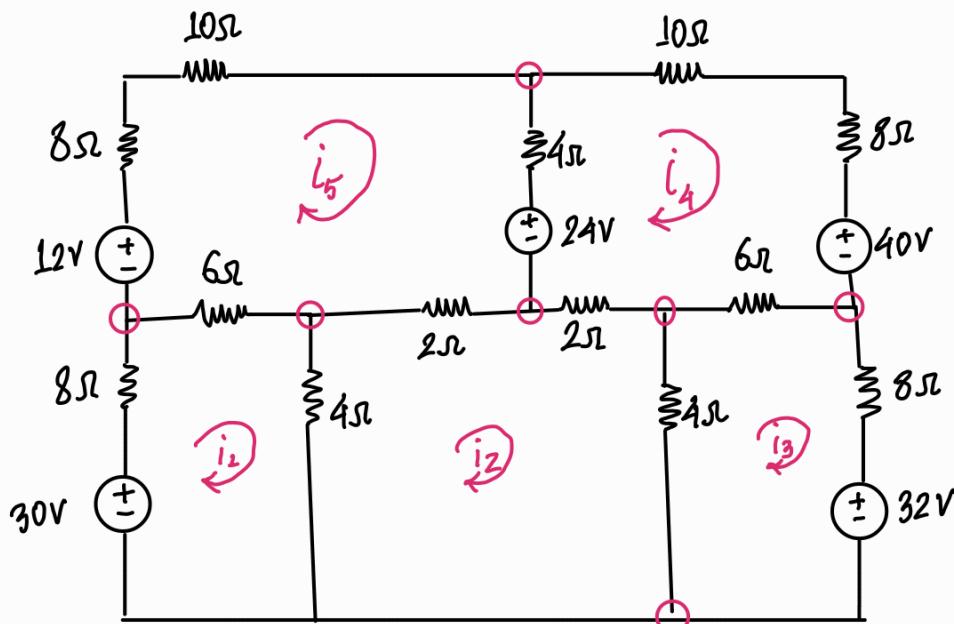

Which method of analysis will be more convenient for solving this ckt? Derive the equations for the convenient method.

$$\begin{aligned} \text{\# essential nodes} &= 7 & \therefore \text{\# nodal equations} &= 6 \\ \text{\# meshes} &= 5 & \therefore \text{\# mesh equations} &= 5 \end{aligned}$$

∴ mesh analysis will be more convenient.

KVL @ 1 —

$$18i_1 - 4i_2 - 6i_5 = 30 \quad \textcircled{i}$$

KVL @ 2 —

$$-4i_1 + 12i_2 - 4i_3 - 2i_4 - 2i_5 = 0 \quad \textcircled{ii}$$

KVL @ 3 —

$$-4i_2 + 18i_3 - 6i_4 = -32 \quad \textcircled{iii}$$

KVL @ 4 —

$$-2i_2 - 6i_3 + 30i_4 - 4i_5 = -16 \quad \textcircled{iv}$$

KVL @ 5 —

$$-6i_1 - 2i_2 - 4i_4 + 30i_5 = -12 \quad \textcircled{v}$$

Solving  $\textcircled{i}$ ,  $\textcircled{ii}$ ,  $\textcircled{iii}$ ,  $\textcircled{iv}$  &  $\textcircled{v}$  —

$$i_1 = 1.468 \text{ A}$$

$$i_2 = -0.476 \text{ A}$$

$$i_3 = -2.233 \text{ A}$$

$$i_4 = -1.049 \text{ A}$$

$$i_5 = -0.278 \text{ A}$$

Solving wasn't required.

I solved the values to check if the equations were correct and so I have included the values here.