

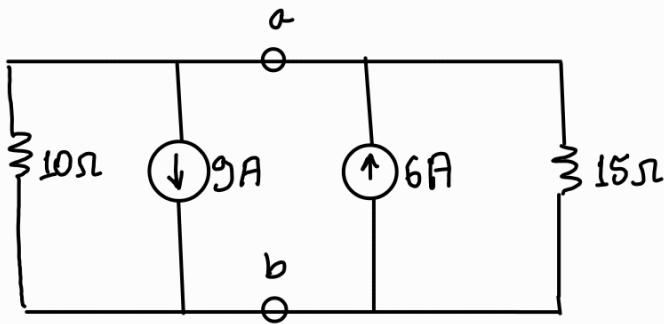



Problem 1

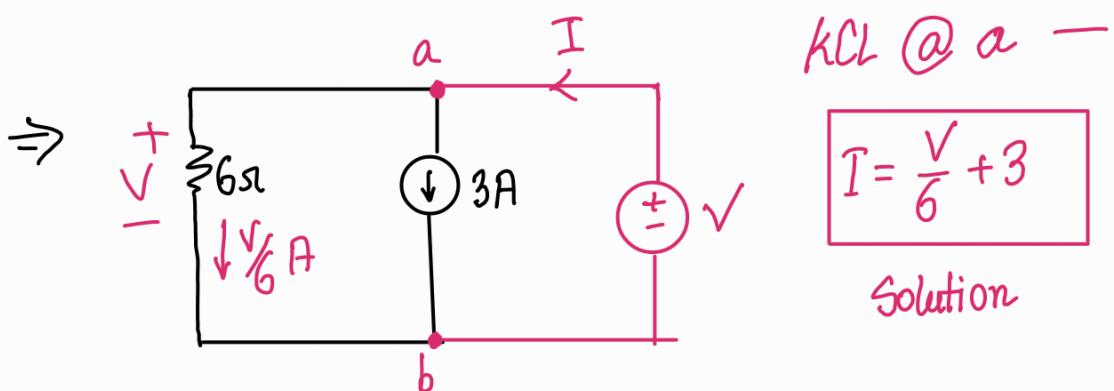


Derive I-V characteristics of the following circuit with respect to the terminals a-b

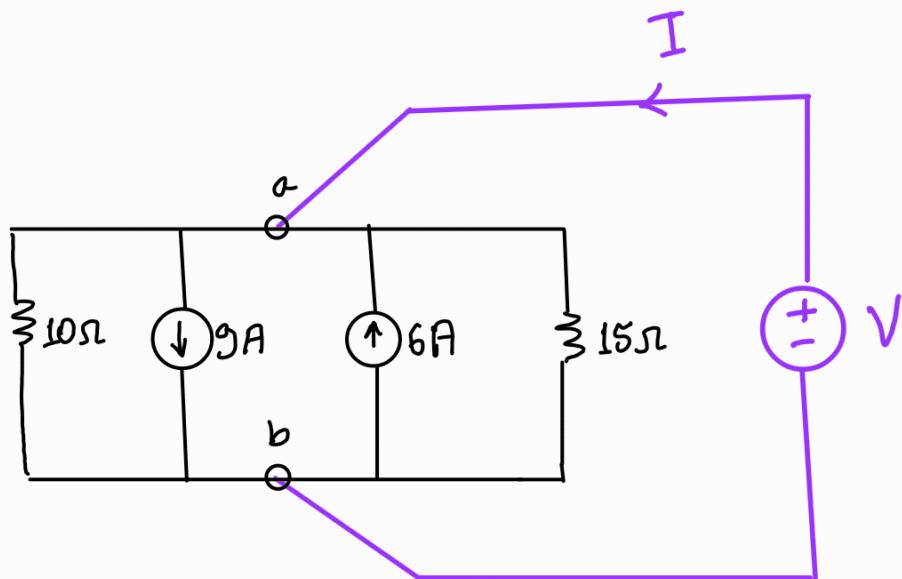

Problem 2

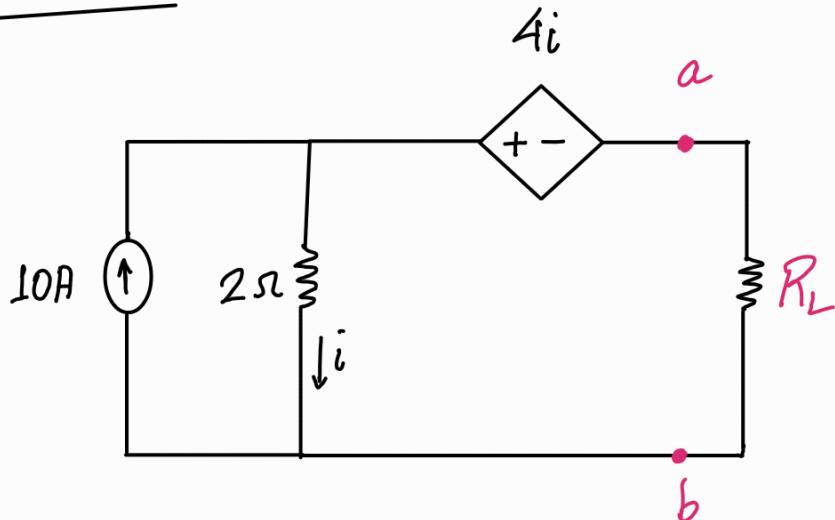

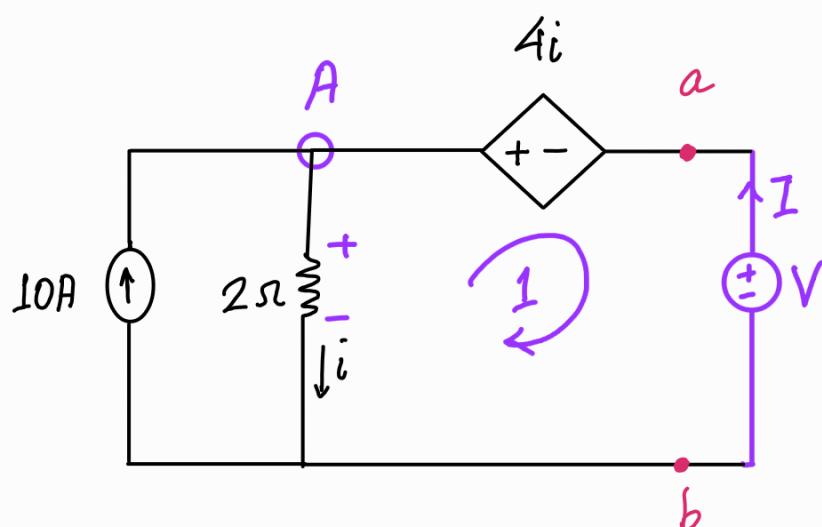Derive the $I-V$ characteristics of the portion left to the terminals $a-b$.



$$KCL @ A - 10 + I = i \quad \textcircled{i}$$

$$KVL @ I - V - 2i + 4i = 0$$


$$\Rightarrow V = -2i$$

$$\Rightarrow i = -\frac{V}{2} \quad \textcircled{ii}$$


$$\therefore \textcircled{i} \rightarrow I = -\frac{V}{2} - 10$$

↳ Solution

Problem 3

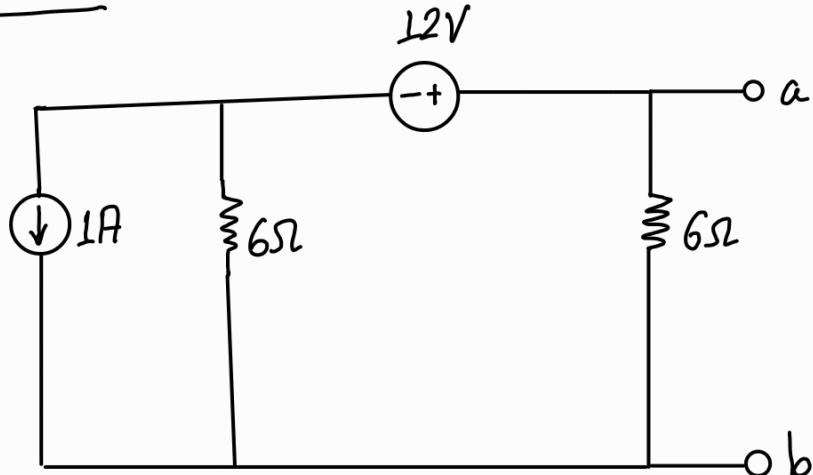

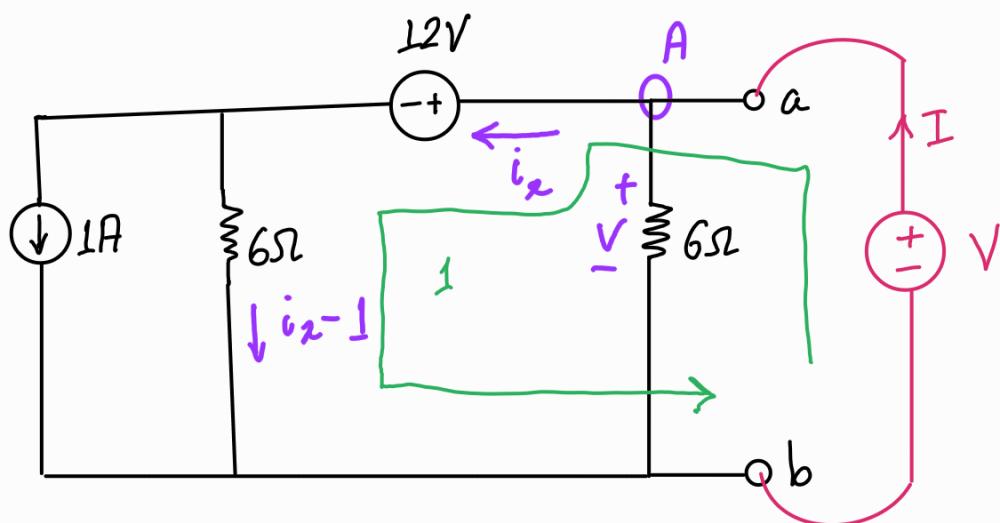From the following circuit
derive the I-V characteristics
between the terminals a-b



$$KCL \text{ at } A - I = i_x + \frac{V}{6} \quad \textcircled{i}$$

$$KVL \text{ at } 1 - 12 + 6i_x - 6 - V = 0$$

$$\Rightarrow 6i_x = V - 6$$


$$\Rightarrow i_x = \frac{V}{6} - 1$$

$$\therefore \textcircled{i} \rightarrow I = \frac{V}{6} - 1 + \frac{V}{6}$$

$$\Rightarrow I = \frac{V}{3} - 1$$

Solution

Problem 4

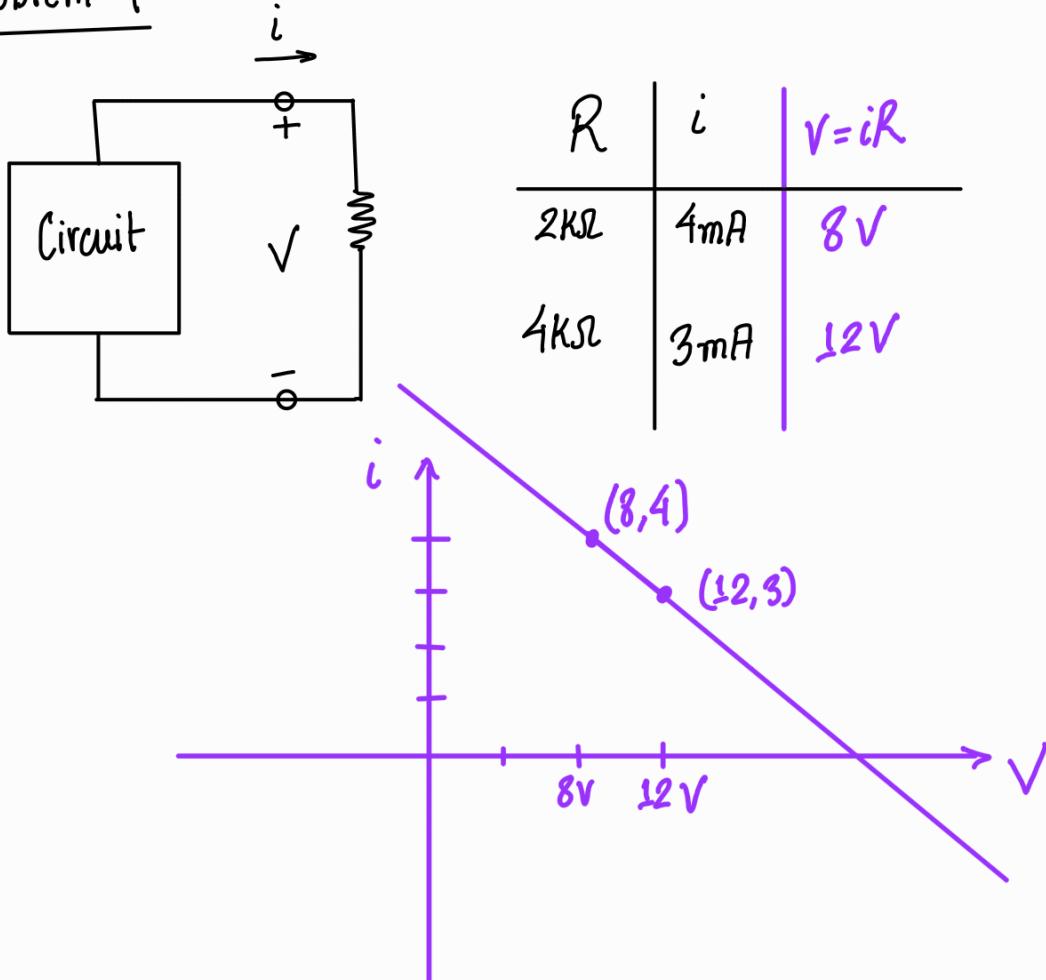


Equation from graph — $\frac{4-3}{8-12} = \frac{I-3}{V-12}$

$$\Rightarrow V-12 = -4I+12$$

$$\Rightarrow I = -\frac{V}{4} + 6$$

Now how do we find the simplest form of ckt from I-V equations?

The simplest form of ckt —

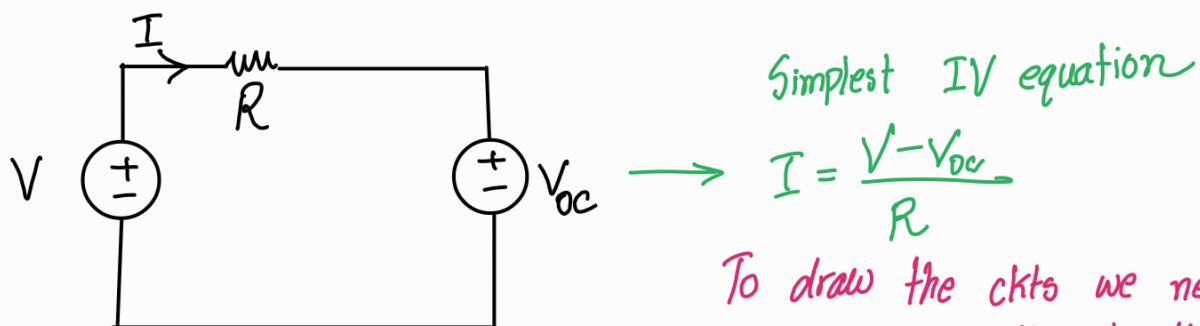

Simplest IV equation

$$I = \frac{V - V_{oc}}{R}$$


To draw the ckt's we need to bring the I-V equation to this form.

Going back to our problem —


Our IV equation $\rightarrow I = -\frac{V}{4} + 6$

$$= -\frac{\sqrt{-24}}{4}$$



\therefore ckt —

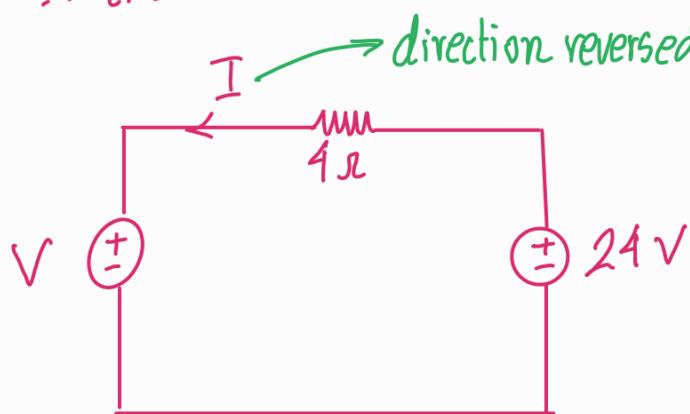


This is also correct —

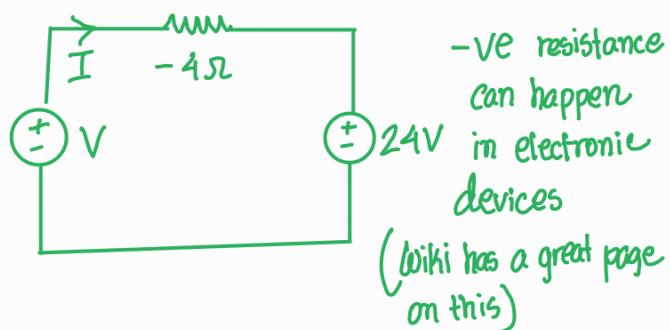

Problem 5

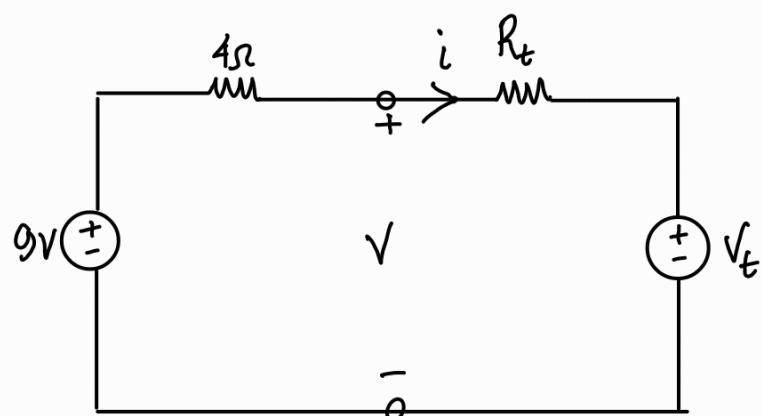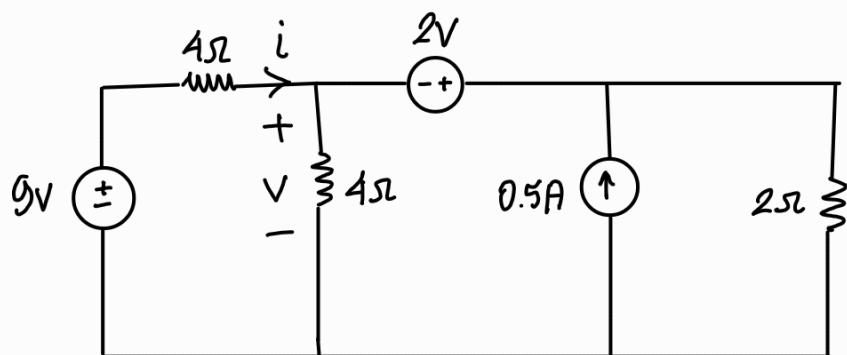

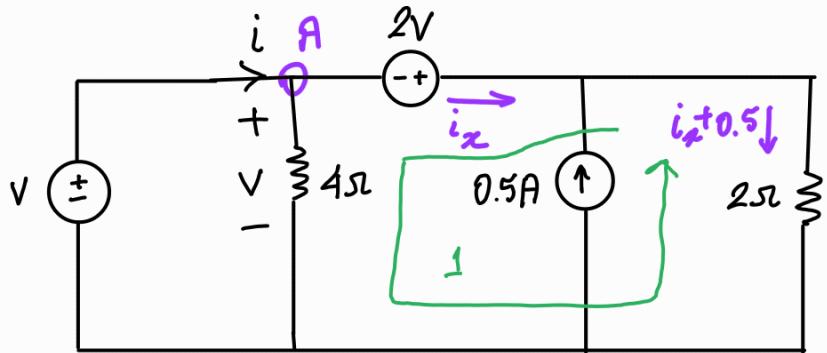Determine the value of R_t & V_t if the two circuits are equivalent to each other.



We have to at first find the I-V characteristics equation for this circuit.

$$KCL @ A \rightarrow i = \frac{V}{4} + i_x \quad \text{--- (i)}$$

$$KVL @ 1 \rightarrow V - 2i_x - 1 + 2 = 0$$

$$\Rightarrow i_x = \frac{V}{2} + \frac{1}{2}$$


$$\therefore \text{(i)} \rightarrow i = \frac{V}{4} + \frac{V}{2} + \frac{1}{2}$$

$$= \frac{3V}{4} + \frac{1}{2}$$


now we have to change it to the simplest form—

$$\begin{aligned} i &= \frac{3V + 2}{4} \\ &= \frac{V - (-\frac{2}{3})}{4/3} \end{aligned}$$


\therefore the simplest ckt —

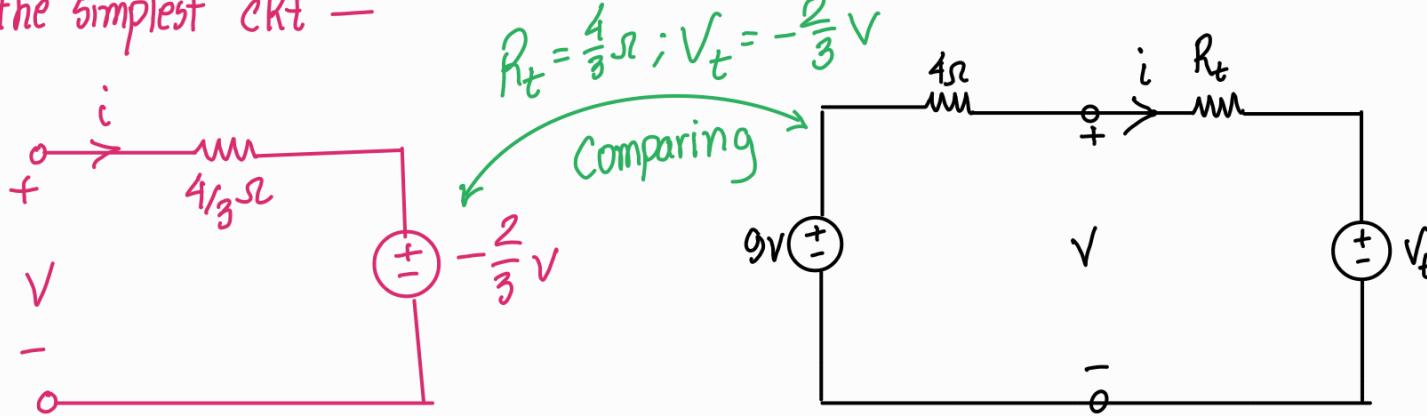


Problem 6

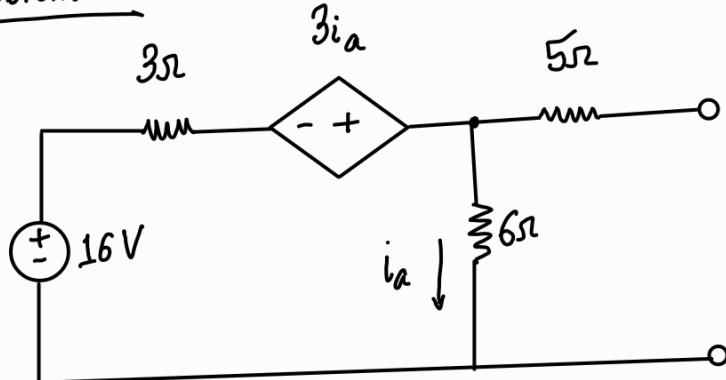

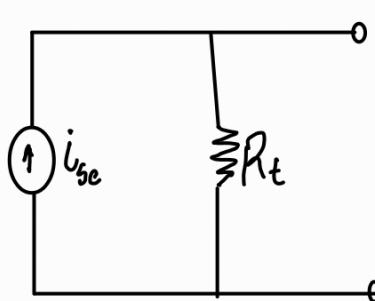Determine the value of i_{sc} and R_t if two ckt's are equivalent.



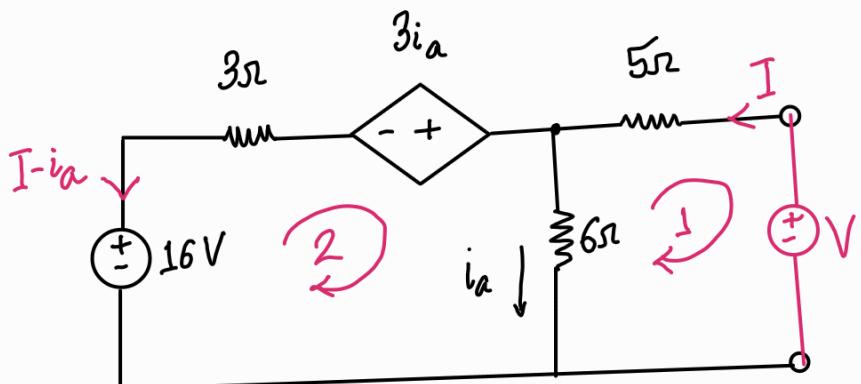Find the I-V characteristics equation for the original ckt —



$$\begin{aligned} \text{KVL @ 1} - \\ V - 6i_a - 5I = 0 \quad \textcircled{1} \end{aligned}$$

KVL @ 2 —

$$-16 - 3I + 3i_a - 3i_a + 6i_a = 0$$


$$\Rightarrow 6i_a = 16 + 3I$$

$$\textcircled{1} \Rightarrow V - 16 - 3I - 5I = 0$$

$$\Rightarrow I = \frac{V}{8} - 2$$

We cannot use our previous simplest circuit because it was in the form of voltage source.

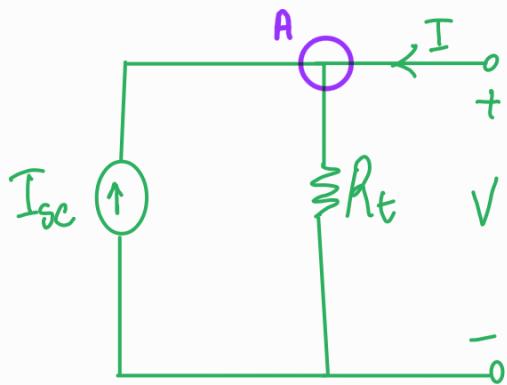Let's derive a simplest equation form for the ckt -



KCL @ A —

$$I + I_{sc} = \frac{V}{R_t}$$



$$\Rightarrow I = \frac{V}{R_t} - I_{sc} \quad \text{Comparing}$$

Now our original I-V equation — $I = \frac{V}{8} - 2$

$$I_{sc} = 2A$$


$$R_t = 8\Omega$$

Problem 7

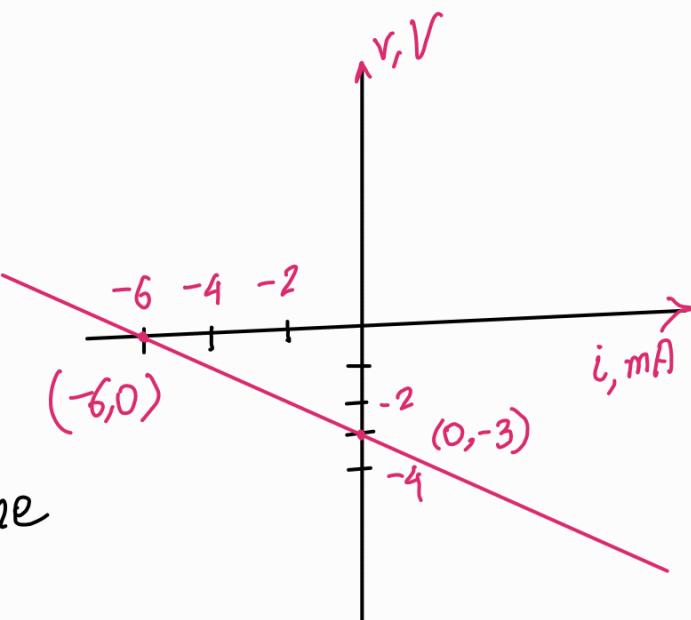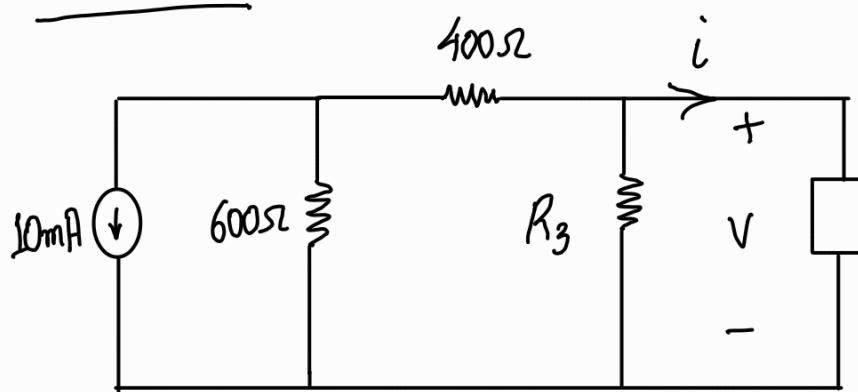

From the v-i characteristics find the value of R_3

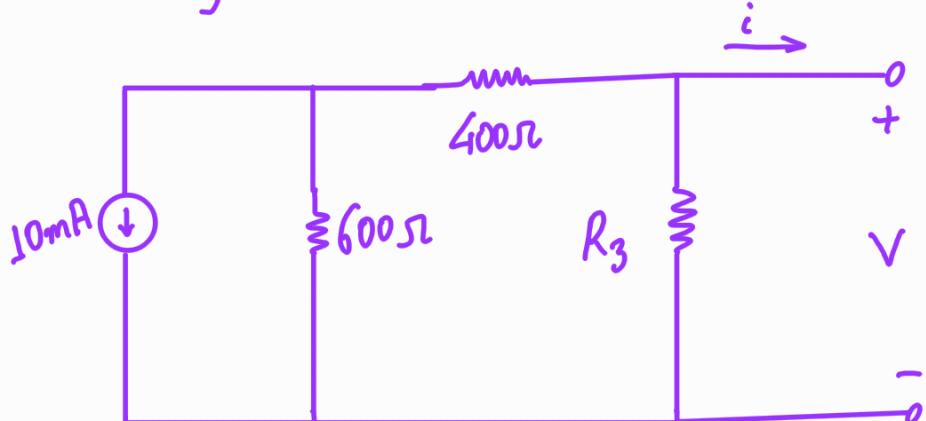Since R_3 is on the left side, we are only concerned with that part




In such problems, we will take advantage of the extreme points in the graph.

1st extreme point $\rightarrow (-6\text{mA}, 0\text{V}) \rightarrow$ short circuit


2nd extreme point $\rightarrow (0\text{mA}, -3\text{V}) \rightarrow$ open circuit

1st extreme point ckt —

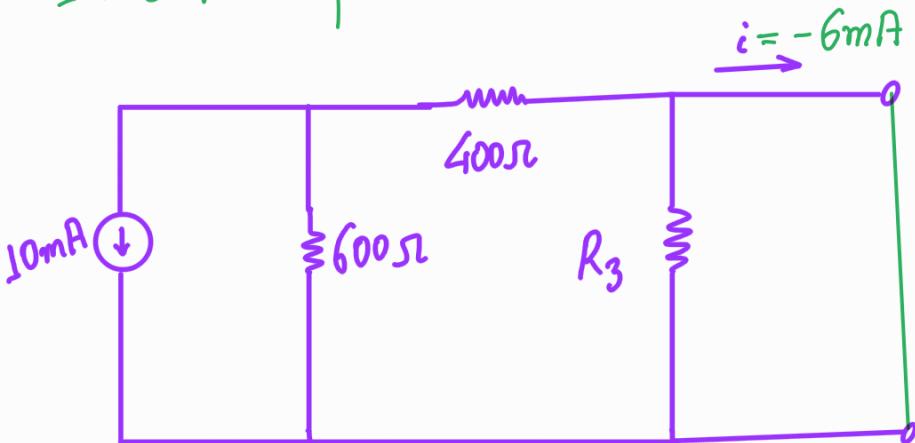

Cannot be used because we lose R_3 to a short circuit

2nd extreme point ckt —

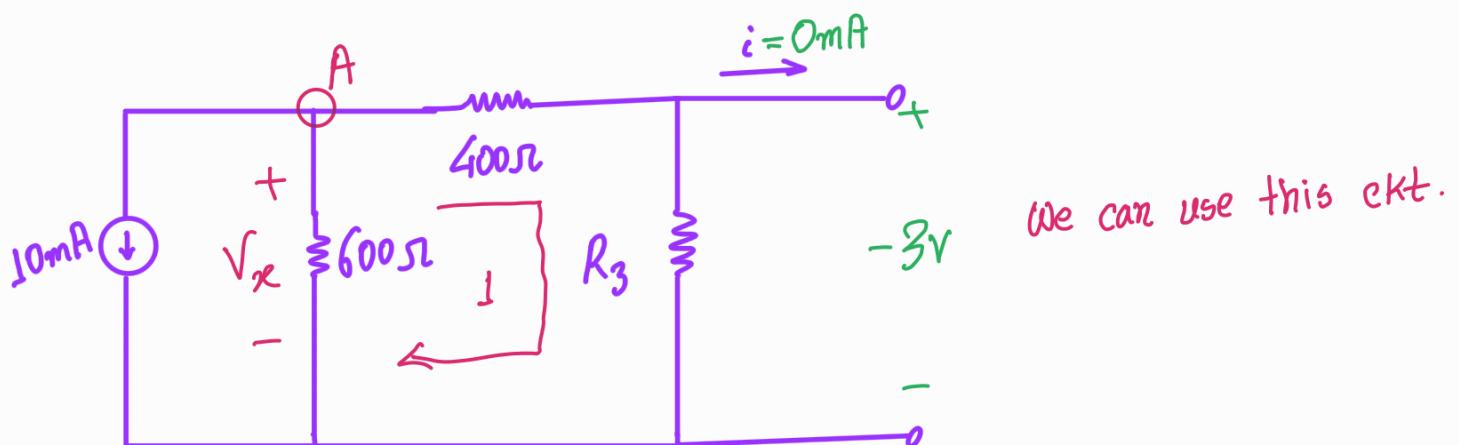

We can use this ckt.

$$\text{KCL @ } A - 10 + \frac{V_A}{600} + \frac{-3}{R_3} = 0 \quad \textcircled{i}$$

$$\text{Voltage divider in } \textcircled{i} \rightarrow -3 = \frac{R_3 V_A}{400 + R_3}$$

$$\Rightarrow -1200 - 3R_3 = R_3 V_A$$

$$\Rightarrow V_A = -\frac{1200}{R_3} - 3$$

$$\therefore \textcircled{1} \Rightarrow 10 - \frac{2}{R_3} - \frac{1}{200} - \frac{3}{R_3} = 0$$

$$\Rightarrow \frac{5}{R_3} = \frac{2 - 1}{200}$$

$$\Rightarrow R_3 = 1000 = 1 \text{ k}\Omega$$